

Bismah Noor

Batch-I Fsc

# CURRENT ELECTRICITY

@Sochbadlobymak

flow (of) electric charges

Introduction: "Electric current is net charge flowing through area per time."

→ Steady current is the constant flow of free electrons

→ Conventional current; it was assumed before the electron theory that current flows from positive terminal to negative terminal.

→ Electronic current; actual direction of current is from negative terminal to positive terminal.

→ Why is current scalar? Because it does not follow vector law of addition.

→ When do electrons flow? When free electrons present in a conductor are exposed to a potential difference, they flow.

Mathematically:

$$I = \frac{Q}{t} \text{ (C s}^{-1}\text{)}$$

where  $I$  = current,  $t$  = time  
 $Q$  = charge


SI unit

: Ampere

Drift Velocity: "The net velocity which  $e^-$ s acquire within a conductor upon connection w/ a battery is called drift velocity"

→ Why is drift velocity called as 'drift' velocity?

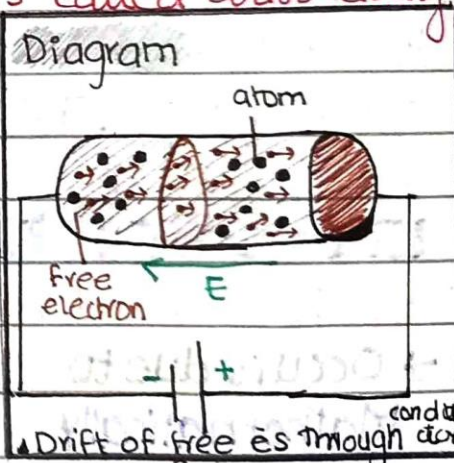When upon connection with a battery, of conductor electric field  $E$  is set up at every point within the conductor. The electrons ( $e^-$ ) acquire some path through the conductor with some drift velocity but  $e^-$ s face opposition from atoms of conductor and thus they deviate from their straight path and move along a tilted drift path.



Mathematically

$$V_d = \frac{j}{nq} \text{ where } j = \text{current density} = \frac{I}{A}$$

$$V_d = \frac{I}{nqA} \text{ or } V_d = \frac{I}{nqA}$$

only the free electrons within a conductor cause electric current in a conductor

→ Important point: In absence of battery net effect/velocity of  $e^-$ s is zero.

**iii, Ohm's Law:** "Current and voltage show a linear relationship as long as the temperature of conductor is kept constant."

→ Constant temperature is important for obeying this law as with increase in temperature, effective collisions between atoms start which offer resistance to the flow of current.

Mathematically  $V \propto I$  or  $V = IR$

→ Non Ohmic materials are those having variable slope for I versus V graph



→ Ohmic materials are those having a constant slope for I versus V graph.

→ Limitations of Ohm's law

- not applicable to insulators
- valid at only constant temperature
- not applicable on semiconductors and gaseous conductors like hydrogen

→ Graph

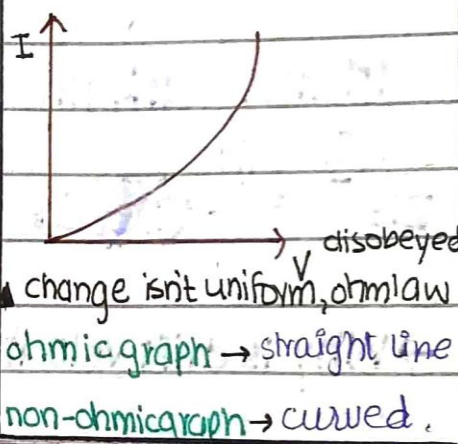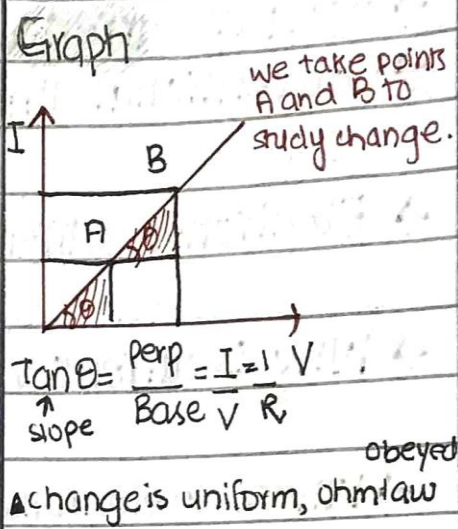We plot a graph between I and V to observe their behaviour with respect to each other and to study change. The curve tells us about resistance since  $I/V = I/R$  or  $V/I = R$



Get admission in our institute  
"SochBadloByMAK"  
For Online Classes Admission details  
Contact WhatsApp: +92 331 5014353

**iii, Electrical Resistance:** "Resistance is the opposition offered by the substance to the flow of free electrons"

→ Occurs due to collision of free electrons with atoms. This liberates heat.

Mathematically symbol's  $\Omega$   $1 \Omega = 1V/1A$  SI unit Ohm. ( $\Omega$ )

Factors affecting;

→ Length  $R \propto L$

→ Cross section A  $R \propto 1/A$

→ Nature of material

→ Temperature  $R \propto T$

REASONS

- Greater length means greater no. of atoms for collision.
- Small c.s.A means greater resistance to passage of charge
- Specific resistance varies from material to material
- Temperature increases the collisions b/w atoms.

Get admission in our institute

"SochBadloByMAK"

For Online Classes Admission details

Contact WhatsApp: +92 331 5014353

## Combined equation

$$R \propto \frac{L}{A}$$

$$R = \rho \times \frac{L}{A}$$

where  $\rho$  is (keeping  $T$  constant) called specific resistance of material

## → Specific resistance

or resistivity of a material is the resistance offered by 1m length of wire of material having an area of cross section of  $1\text{m}^2$ .

→ Resistivity of metals is very less thus they are good conductors.

→ Resistivity of insulators is very large thus they hardly conduct any current.

## ↳ effect of temperature on:

→ Resistance of conductor increases with increase in temperature due to collisions which offer hindrance to free  $e^-$ s  $\uparrow T \propto R \uparrow$

→ Resistance of an insulator decreases w/ increase in temperature. This is because the electrons which otherwise do not flow due to not being free, gain enough energy from heat to jump from their orbits and start flowing.  $\uparrow T \propto 1/R \downarrow$

↳ **Conductance**: "The reciprocal of resistance of a conductor is called conductance (G)."

Mathematically

$$G = \frac{1}{R}$$

SI unit

mho

Common unit

Siemen (S).

## → Conductance / Resistance

VS

## → Resistivity / conductivity

- These terms are general which describe the phenomenon of either conductance or resistance

- These terms are specific to the materials which offer either conductance or resistance

All materials have their specified values for these phenomenon thus when specifying conductance or resistance to a specific material, we use resistivity or conductivity

↳ **conductivity**: Reciprocal of resistivity of a conductor is called its conductivity

Mathematically

$$\sigma = \frac{1}{\rho} = \frac{L}{RA}$$

Unit

$\text{mhm}^{-1}$

or siemen meter<sup>2</sup> ( $\text{Sm}^{-1}$ )

# Temperature Coefficient of Resistance / Resistivity

- Consider a conductor having resistance  $R_0$  at  $0^\circ\text{C}$  and resistance  $R_T$  at  $T^\circ\text{C}$ .
- Change in resistance will be (final - initial)  $R_T - R_0$
- Change will depend on initial resistance and rise in temp.
  - $R_T - R_0 \propto R_0$  → Greater the initial value of resistance, greater the change.
  - $R_T - R_0 \propto T$  → Greater the rise in  $T$ , greater will be increase & change in resistance.

**Mathematically**  $R_T - R_0 = \alpha R_0 T$  ① or  $\alpha = \frac{R_T - R_0}{R_0 T}$  ②

where ' $\alpha$ ' is temperature coefficient of resistance.


- What does ' $\alpha$ ' tell us?  $\alpha$  tells us how much change in resistance will occur with respect to the original ohm resistance per degree rise in temperature. **unit of  $\alpha = \text{K}^{-1}$**
- Every conductor has its own value of ' $\alpha$ '.
- Positive and Negative temperature coefficient of R
  - Resistance of metals increases w/ temperature. They have **Positive temperature coefficient of R**. (PTC)
  - Resistance of semiconductors decreases with temperature. They have **Negative temperature coefficient of R**. (NTC)
- Temperature coefficient of 'resistivity'

Equation ① can be stated in terms of specific resistance of material as well. If specific resistance  $\rho_0$  is at  $0^\circ\text{C}$  and  $\rho_T$  is at  $T^\circ\text{C}$  then

**Mathematically**  $\rho_T = \rho_0 (1 + \alpha T)$  or  $\alpha = \frac{\rho_T - \rho_0}{\rho_0 T}$
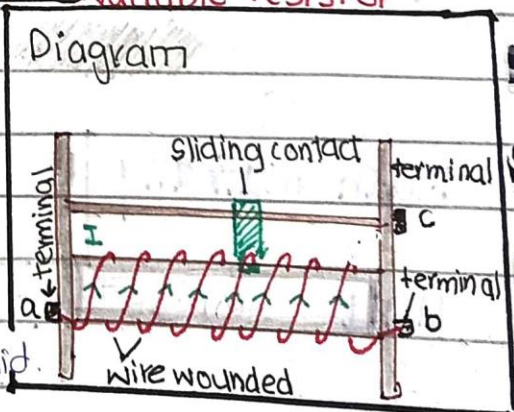
## Rheostat: Rheostat is a wire-bound variable resistor usually cylindrical in appearance.

- Symbol - its symbol is
- Construction wire is wound over some ceramic material. Rheostat has three terminals, two are fixed (a and b) and one is variable (c). A sliding contact is present which slides over the wires or solenoid.




→ **Function** Rheostat is a current controlling device. It acts as a potential divider in the circuit. If the fixed terminals are connected in the circuit it acts as a fixed resistor. If the variable terminal along with one fixed terminal are connected, it acts as variable resistor.

**Potential Divider** ∴ "Rheostat helps us to get a variable potential difference hence it acts as a potential divider."

→ **Connection in circuit** we will connect either a or b and the c terminal in the circuit. to get rheostat work like a potential divider. (series connection will be effective)

→ **Working Principle** works on the principle **Resistance  $\propto$  Length of wire**

**Working**

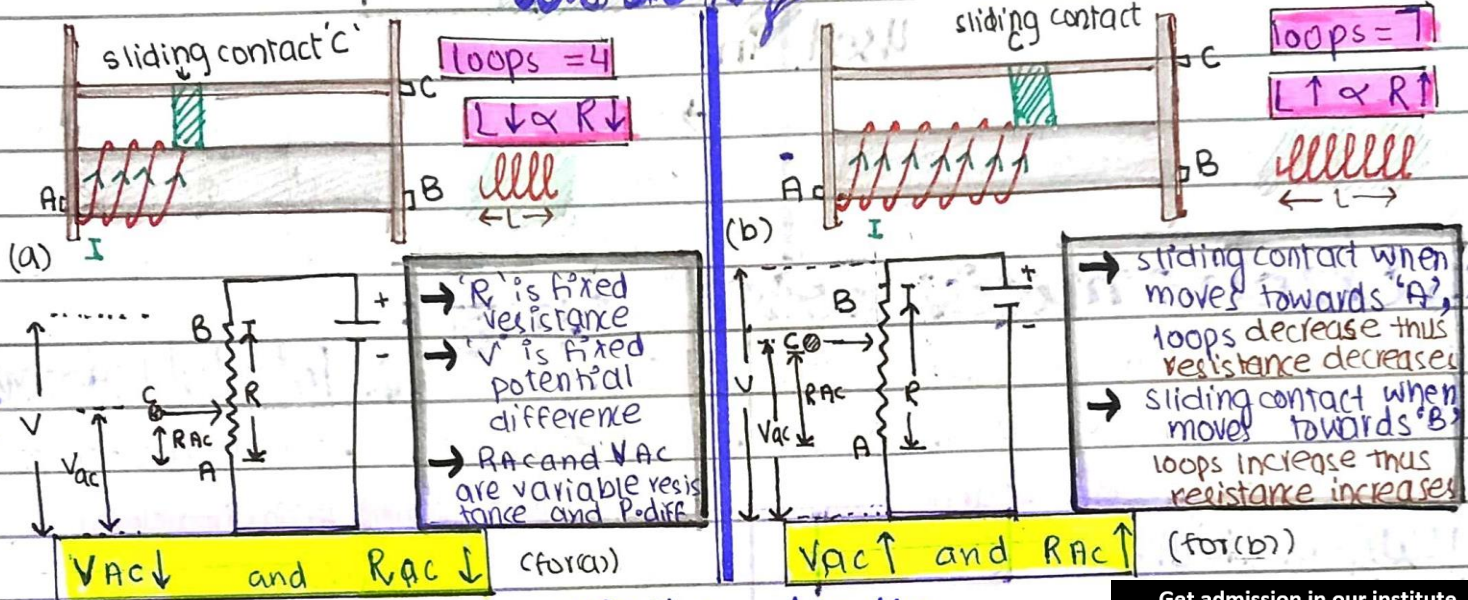

**Mathematically**

$V_{AB} = IR$

$V_{AC} = IR_{AC}$

$V_{AC} = V \times \frac{R_{AC}}{R}$

$V_{AC} = \frac{R_{AC}}{R} \times V$

(fixed potential difference of circuit)

(variable potential difference due to sliding contact c)

→ **What does ratio  $R_{AC}/R$  tell us?** This ratio tells us about what portion the variable resistance ' $R_{AC}$ ' is of the total resistance ' $R$ '. Then in order to find potential difference for that part having variable resistance ' $R_{AC}$ ' we multiply the ratio  $R_{AC}$  with total potential difference.


Get admission in our institute "SochBadloByMAK"  
 For Online Classes Admission details  
 Contact WhatsApp: +92 331 5014353

**Conclusion** ∴ Depending on the position of the sliding contact 'c' the value of fraction  $R_{AC}/R$  can be varied from 0 to 1.

**Thermistor:** "Thermistor is a temperature sensing device whose function is to exhibit change in electrical resistance with corresponding change in temperature."

Get admission in our institute  
"SochBadloByMAK"  
For Online Classes Admission details  
Contact WhatsApp: +92 331 5014353

Symbol

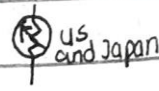

### → NTC Thermistor

### → PTC Thermistor

Increase in Temp

→ Its resistance decreases

→ Its resistance increases

Decrease in Temperature

→ Its resistance increases

→ Its resistance decreases

Mathematically

$$\uparrow R \propto \downarrow 1/T \downarrow$$

$$\uparrow R \propto T \uparrow$$

Used in

→ hair dryers, ovens, toasters, A-C  
Fire alarm, thermostats washing  
machines, freezers etc

→ automotive industry as heaters.  
Timing devices in TVs. They are  
generally used for fuse purposes.

## iii, Electromotive Force Emf :

Emf 'E' of a source equals the work done in carrying 1 coulomb of charge through the source

Mathematically

$$E = W/q$$

**PKMZ:** Emf motivates the e<sup>-</sup>s to move across the circuit. It's similar to motivating students to bunk a class. Thus to memorize, we can call emf as electron bunk force.

→ Sources: Battery, Thermocouples, generators, Radiant.

→ Unit **volt V**

## Emf vs Potential Difference

• Emf is maximum potential difference b/w battery terminals in an open circuit	• Is the difference of two points' potential in a closed circuit
• It's independent of the resistance of circuit	• It's dependent on the resistance of circuit
• Responsible for steady current	• Not responsible for <sup>steady</sup> current
• It is a <b>cause</b>	• It is an <b>effect</b>
• Greater than potential difference	• Smaller than emf
• Remains constant	• varies with resistance
• Causes electric and magnetic field.	• only causes electric field.
• Symbol <b>E</b>	• Symbol <b>V</b>

# Maximum Power Output: "Maximum

power output is obtained when load resistance equals internal resistance of the source of emf. This is also called maximum power transfer theorem.

→ Minimum power will be delivered to load when load resistance is less or greater than the source resistance.

## Mathematically

Expression can be derived in two ways

$$P_{out} = VI$$

$$P_{out} = (IR)I$$

$$P_{out} = I^2 R \quad (1)$$

$$\mathcal{E} = IR + Ir, \quad \mathcal{E} = I(r+R)$$

$$\mathcal{E}/(r+R) = I \quad (2)$$

Put eq (2) in (1),  $P_{out} = \left(\frac{\mathcal{E}}{r+R}\right)^2 \times R$

$$P_{out} = \frac{\mathcal{E}^2}{r^2 + R^2 + 2rR} \times R$$

condition  $\rightarrow R=r$

$$P_{out} = \frac{\mathcal{E}^2}{(R^2 + R^2 + 2R^2)} \times R, \quad P_{out} = \frac{\mathcal{E}^2 \times R}{4R^2}$$

$$P_{out} = \frac{\mathcal{E}^2}{4R}$$

**Important point** Both derivations are correct for exam.

→ Usually when we consider the factor 'R' to be equal to 'r', we talk on theoretical ideal basis. In actual practice, it's usually not possible to get these factors equal.

$$P_{out} = VI$$

$$P_{out} = (IR)I$$

$$P_{out} = I^2 R$$

$$\mathcal{E} = Ir + IR, \quad \mathcal{E} = I(r+R)$$

$$P_{out} = \left(\frac{\mathcal{E}}{r+R}\right)^2 \times R$$

$$P_{out} = \frac{\mathcal{E}^2}{(r+R)^2} \times R$$

$$P_{out} = \frac{\mathcal{E}^2}{r^2 + R^2 + 2rR} \times R$$

adding and subtracting  $(-2rR)$  at RHS

$$P_{out} = \frac{\mathcal{E}^2}{r^2 + R^2 + 2rR - 2rR + 2rR} \times R$$

$$P_{out} = \frac{\mathcal{E}^2}{(r-R)^2 + 4rR} \times R$$

factor  $(r-R)^2$  shows us that when they are equal, they cancel each other's effect.

$$P_{out} = \frac{\mathcal{E}^2}{(r-r)^2 + 4r^2} \times R \quad (\text{Putting } r=R)$$


$$P_{out} = \frac{\mathcal{E}^2}{4r}$$

Get admission in our institute  
"SochBadloByMAK"  
For Online Classes Admission details  
Contact WhatsApp: +92 331 5014353

**in, Thermocouples:** "Temperature sensor that generates a potential difference through temperature change is called Thermocouple"

→ Working principle / Seebeck effect

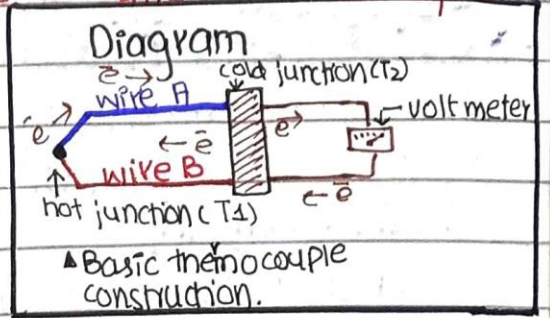Working principle of thermocouple is the Seebeck effect, which states that when two metals are joined at two ends, there is a temperature difference across the junction and a voltage is generated.



→ Types {J, K, E, T} Base metal T.c.s. {R, S, B} Noble metal thermocouples.

→ Construction two dissimilar wires 'A' and 'B' are joined at one end  $T_1$  - the "hot" junction (variable temperature) the other end  $T_2$  (cold junction) is maintained at a constant reference temperature i.e.,  $0^\circ\text{C}$

→ Reason behind using dissimilar metals Metal combination like Cu-Fe might be used. This is because due to the different nature and conductivity of metals, charges get a direction to flow when temperature gradient is applied.

→ emf generation and its direction hot and cold junction together work as an emf source. The Seebeck effect is reversible; if hot and cold junctions are interchanged, the direction of emf reverses.

usually, Hot junction → +ve terminal (high potential) and cold junction → -ve terminal (low potential)

Mathematically

$$E = \alpha T + \frac{1}{2} \beta T^2$$

and


Distance b/w metals  $\propto$  Thermo emf

→ Variation in thermo emf with temperature?

→ If junctions are in thermal equilibrium no thermo emf will be produced.

→ If junctions are at different temp (hot and cold) thermo emf will be generated and increased upon increasing temp of hot junction and maximum at

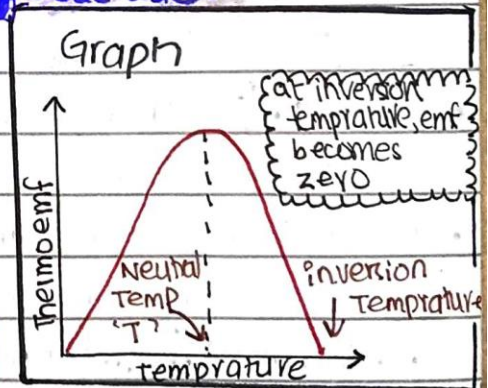neutral temperature  $T$  [value of neutral temperature depends on nature of material & is constant for a t.c.]



→ Further increase in temperature will cause decrease in thermo emf because high temperature above  $T$  will alter the nature of material used. At a certain high temperature, emf becomes zero. This is the inversion temperature.



# in, KIRCHHOFF'S LAW: Robert Kirchhoff gave two laws for

complex circuits where ohm's law can't be applied

→ **LAW (1); Kirchhoff's Current Law:** "The sum of all the currents flowing towards a junction is equal to sum of all currents moving away from it."

**Mathematically** (with respect to the diagram →)

$$(+I_1) + (+I_4) + (-I_3) + (-I_2) = 0$$


(Current moving towards junction will have +ve sign and the current moving away from junction will've negative sign)

$$I_1 + I_4 = I_3 + I_2$$

towards      away

or



$$\sum I = 0$$

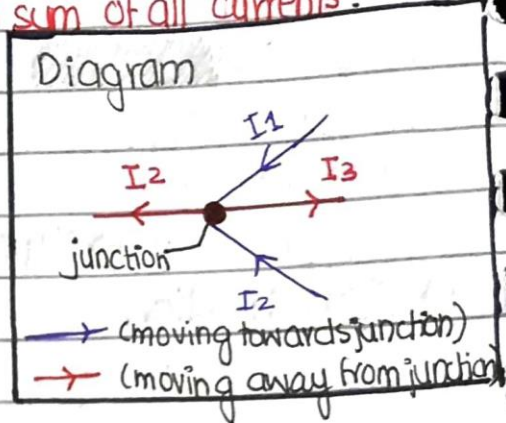


→ KCL is a manifestation of law of conservation of charge to a junction which implements; if there's no sink or source of charge at a point, the total charge flowing towards the point must be equal to the total charge flowing away from it.

→ **LAW (2); Kirchhoff's Voltage Law:** "In any closed electrical circuit, the algebraic sum of all electromotive force (emf) and voltage drops in resistor is equal to zero."

→ How to assign signs to  $\mathcal{E}$  and  $IR$  in equation? (consider the diagram →)

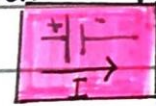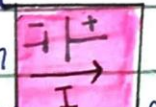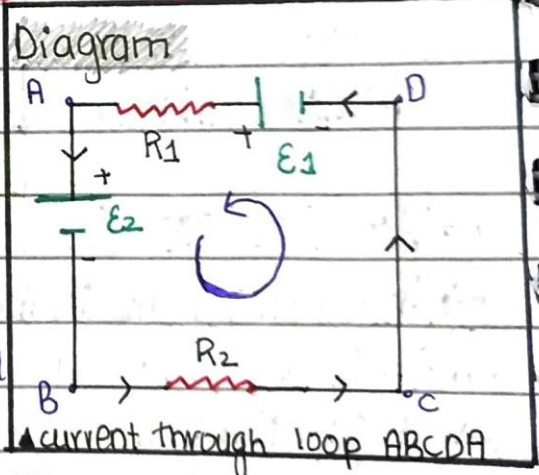- When  there will be a fall in potential represented by a -ve sign i.e.,  $-E_2$
- When  there will be a rise in potential represented by a +ve sign i.e.,  $+E_2$



• As voltage always drops due to resistance,  $IR_2$  &  $IR_1$  will be both -ve (Here resistors are traversed in the direction of current thus potential drop is -ve)

**Mathematically** Energy gained through  $\mathcal{E}_1 = \mathcal{E}_1 \Delta Q$ , Energy loss through  $\mathcal{E}_2 = -\mathcal{E}_2 \Delta Q$   
 Energy lost through  $R_1 = -IR_1 \Delta Q$ , Energy loss through  $R_2 = -IR_2 \Delta Q$

According to law of conservation of energy, total energy change must be zero so

$$E_1 \Delta Q - IR_1 \Delta Q - E_2 \Delta Q - IR_2 \Delta Q = 0$$

[take  $\Delta Q$  common]

$$E_1 - IR_1 - E_2 - IR_2 = 0$$

[ $\because \Delta Q \neq 0$ ]


$$E_1 - E_2 = IR_1 + IR_2$$

$$\sum E = \sum IR$$

Get admission in our institute  
"SochBadloByMAK"  
For Online Classes Admission details  
Contact WhatsApp: +92 331 5014353

→ KVL is a manifestation of law of conservation of Energy.  
**III, Wheatstone Bridge:** "It is basic electrical circuit which is used to measure the value of unknown resistance."

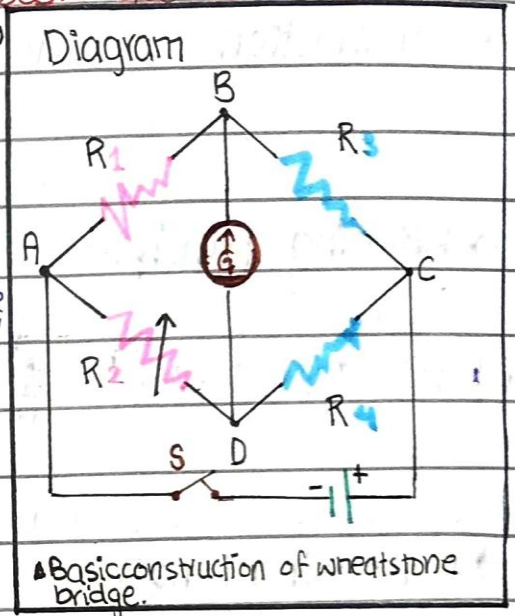→ **Construction** 4 resistances joined together value of two is fixed and known ( $R_1$  and  $R_3$ ) value of one is variable ( $R_2$ ) and known. The remaining ' $R_4$ ' is unknown. These are connected to Emf source.



→ **Working principle** when the potential at point B and D becomes equal, no current flows through the galvanometer. This is called as **null** or **balanced condition**.

→ **How is null condition achieved?** To achieve the null condition, resistances  $R_1, R_3$  and  $R_2, R_4$  should have equal ratios. As  $V \propto R$ , when ratios of resistances become equal, the ratio of potential at point B to D becomes equal. In this condition, no potential difference is present for current to flow through galvanometer and it points at 0. This is achieved by varying value of  $R_2$  (variable resistor).

**Mathematically** at null condition  $R_2 : R_4 = R_1 : R_3$

$$\text{or } \frac{R_2}{R_4} = \frac{R_1}{R_3}$$

but ' $R_4$ ' is not known to us thus,

$$\frac{R_1}{R_3} \times \frac{1}{R_2} = R_4$$

$$\boxed{\frac{R_2 \times R_3}{R_1} = R_4}$$

Grab the concept " suppose  $R_2 = 2\Omega$

and  $R_4 = 4\Omega$  ratio becomes 1:2

and  $R_1 = 6\Omega, R_3 = 12\Omega$  ratio becomes

1:2 under this condition, potential drop at B becomes equal to potential drop at D.

→ **Potentiometer**: A device used to measure or compare the potentials without drawing any current from the circuit.

→ **Drawbacks of voltmeter covered by Potentiometer** The potential difference can be measured using voltmeter but the voltmeter draws some current towards itself unless it has infinite resistance which is impossible. Thus the measurement of p.d. won't be accurate, to overcome this and to get a precise value, we use potentiometer as it draws no current towards itself and circuit current remains unchanged.


→ **Construction** consists of a resistive wire on which a terminal C can slide, a power source (known) and unknown emf source along with a galvanometer.

→ **Working principle** the potential difference across wire is directly proportional to its length.  $V \propto l$  when  $I = \text{constant}$


→ **measurement of emf**: let  $E_x$  be unknown emf of the cell. The positive terminal of  $E_{\text{known}}$  and slider are connected at same point A.

→ **Balancing length** when potential provided by  $E_x$  becomes equal to potential drop due to resistance provided by wire, the galvanometer points at zero. This is balancing length and is found by sliding the slider across A and C. Thus  $E_x = V_{AC} = \frac{l}{L} \times \mathcal{E}$

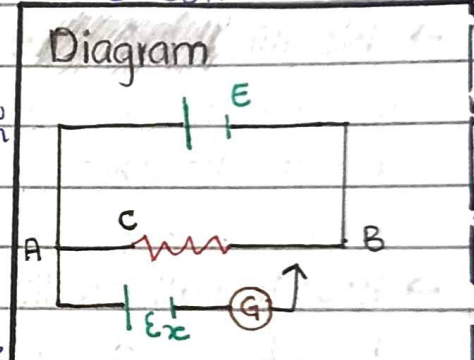→ **comparison of two cell's emf**: The upper method can also be used to compare the  $E_1$  and  $E_2$  of two cells



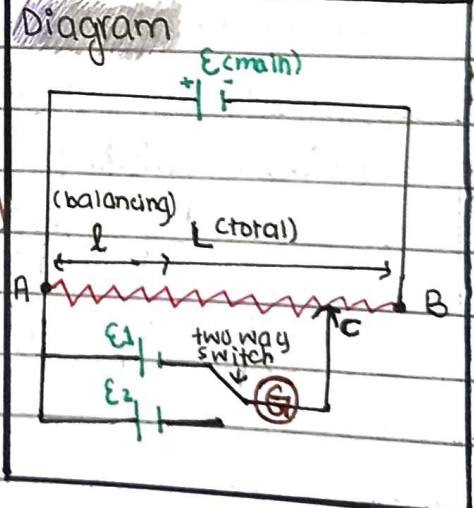- **uses of Potentiometer**
- calculate internal resistance of the cell
  - to determine emf of a cell
  - to compare emf of two cells
  - as a continuously potential divider



**Mathematically**

$$E_1 = \frac{l_1}{L} \times \mathcal{E} \text{ (main battery)}$$

$$E_2 = \frac{l_2}{L} \times \mathcal{E}$$

dividing  $E_1$  by  $E_2$

[Let  $l_2$  and  $l_1$  be balancing lengths for  $E_2$  and  $E_1$  respectively]  
 where  $\frac{l_2}{L} \times \mathcal{E} = V_{AC}$

$E_1$	$=$	$l_1$
$E_2$	$=$	$l_2$

**Get admission in our institute**

**“SochBadloByMAK”**

**For Online Classes Admission details**

**Contact WhatsApp: +92 331 5014353**