
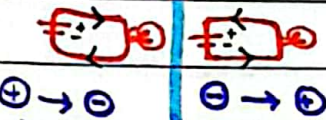


Ch: 5 Current Electricity.

→ CURRENT:

Flow

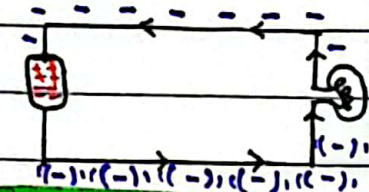


- Conventional does not exist
- Just for the shanti of our buzurgan at main
- Simple exist.
- $I = \frac{Q}{t}$
- $I = C \cdot s^{-1}$
- $I = A$

→ Measuring current:

Galvano-meter:	Ammeter:
used for measuring small currents.	used for large currents measurement.
Two terminals: (i) Red (+ve), (ii) Black (-ve).	Two terminals: (i) Red (+ve), (ii) Black (-ve).
can measure $1 \mu A$, $1 mA$ current.	can measure $1 A$, $10 A$.
will be damaged if large current is given.	will not show deflection if there is small current.


→ Conversion of (G) to (A)

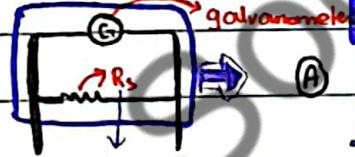we can convert a (G) to (A) by adding a small resistance shunt resistance, in parallel combination.



$R \rightarrow$ Resistance
 $s \rightarrow$ shunt.

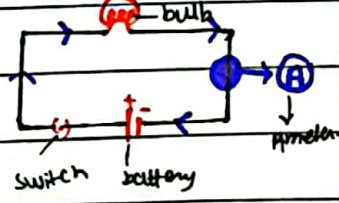In order to measure a current by using an ammeter connect (A) in circuit in series combination, wuz in series the value of current remains same.



Charges. → Potential difference:


- high potential: the point from where the charges enter.
- low potential: the point from where the charges leave the bulb.
- Potential difference causes the flow of charges.
- No charges flow when no potential difference.
- charges enter the conductor, the atoms of conductor oppose or resist the electrons (charges) coming from battery, this resistance causes the consumption of wastage of energy, so electrical energy is converted into heat & light energy.

→ Electromotive Force (EMF).

energy supplied by battery to flow +ve charges through the circuit, is potential difference. when +ve charge from H.P terminal of battery to the L.P terminal of battery the battery gives W energy to drive to the H.P point.


→ Measuring Potential Difference

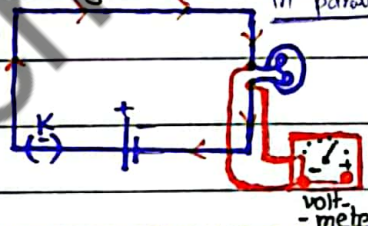- a voltmeter is used for this purpose.
- a galvanometer can be converted / modified into a voltmeter by adding a large resistance.
- Large resistance so, that no current passes through it.
- connected in parallel.




→ Measuring EMF:

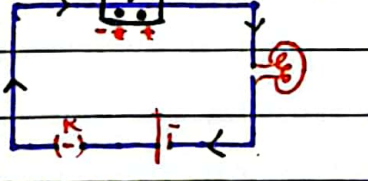- voltmeter is used
- connected directly with the terminals of battery.




→ OHM'S LAW:

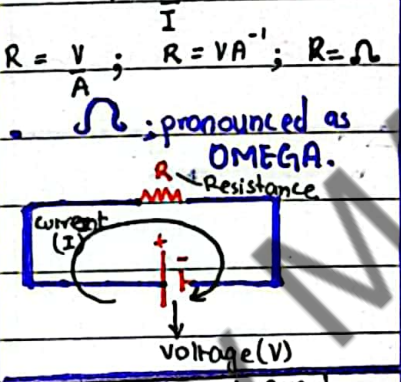- In metals (conductors) there are free electrons, and atoms, the atoms oppose the electrons.
- The opposition is the resistance.
- $I \propto V$
- $V \propto I$
- $V = RI \Rightarrow V = IR$
- Resistance is proportional to constant.
- $R = \frac{V}{I}$
- $R = \frac{V}{A}$; $R = VA^{-1}$; $R = \Omega$



→ Voltage-Current Graph:

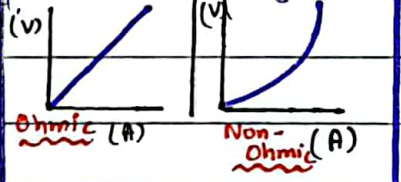- Conductors that obey Ohm's law are called Ohmic conductors.
- They have a linear graph for V-I.
- Mostly metals.
- $R = \frac{V}{I}$; constant over wide range of voltages.
- Conductors that don't obey the Ohm's law are called Non-Ohmic conductors.
- The form an irregular graph for I-V.
- Filament lamp, thermistor.
- $R = \frac{V}{I}$ changes as V changes.



→ Factors affecting resistance:

- (i) cross-sectional area
- (ii) Length
- (iii) Nature of material
- (iv) Temperature
- $R \propto L$ - (i)
- $R \propto \frac{1}{A}$ - (ii)
- Combining (i) & (ii) $R \propto \frac{L}{A} \Rightarrow R = \frac{\rho L}{A}$
- ρ ; Rho, specific resistance.
- $R = \frac{\rho L}{A}$
- $\rho = \frac{RA}{L} \Rightarrow \Omega \cdot m = \Omega m$

→ Combination of Resistors:

→ Series combination:

- Voltage drop: $V_1 + V_2 + V_3 = V$
- Current same: $I = I_1 = I_2 = I_3$
- $V = IR$
- $IR = IR_1 + IR_2 + IR_3$
- $R_e = R_1 + R_2 + R_3$
- $R_e > R_{individual}$

→ Parallel combination:

- Voltage same: $V = V_1 = V_2 = V_3$
- Current changes: $I = I_1 + I_2 + I_3$
- $I = \frac{V}{R}$
- $\frac{V}{R} = \frac{V}{R_1} + \frac{V}{R_2} + \frac{V}{R_3}$
- $\frac{1}{R_e} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$
- $R_e < R_{individual}$

→ Joule's Law:

- Energy is Vitamin.
- By electrostatic potential $V = W$
- By electric current formula $I = \frac{Q}{t}$; $Q = It$
- put (ii) in (i): $(It)V = W$; $W = VIt$

From Ohm's law: $V = IR$ - (i)

put in (i) $W = I^2 R t$

put in (ii) $W = \frac{V^2 t}{R}$

- By power formula, $P = W/t$
- $P = I^2 R$
- $P = \frac{V^2}{R}$
- $P = I^2 R$
- $P = \frac{V^2}{R}$

Electric power:

- $P = \frac{W}{t}$; $W = QV$
- $P = \frac{QV}{t}$; $Q = It$
- $P = VI$; $V = IR$
- $P = (IR)I$
- $P = I^2R$ } Unit: **Watt (W)**

Kilo-watt hour:

on commercial basis large SI units are used such as kWh, h.

$$1 \text{ kWh} = 1000 \text{ W} \times 1 \text{ h}$$

$$1000 \text{ W} \times 3600 \text{ s}$$

$$3.6 \times 10^6 \text{ Ws}$$

$$3.6 \times 10^6 \text{ J}$$

$$1 \text{ kWh} = 3.6 \text{ MJ}$$

Hazards of Electricity.

Insulation damage:

- good insulated wires should be used.
- when cables are over heated short circuit occurs.

Short circuit.

(draw backs of 11omb).

→ due to low opposition by atoms of conductors

bor e), a large amount of current passes

through the wire, in parallel combination.

this large current produces large heat &

melt the insulation, wires meet & spark occurs.

Damp Conditions:

- wet hands have moisture & it can act as electrolyte and conduct current, FIRE!!!

SAFE USE OF ELECTRICITY IN HOMES.

→ Fuse is a device which does not allow large amount of current (that can cause fire), when a large amount of current is coming, the fuse melts and breaks away. otherwise, if there is no fuse, the large currents can start the home on FIRE!!!

→ Circuit breaker, It is also a device like Fuse, it also does not allow large amount of current, the circuit breaker directly cuts the supply by pulling the metal strip to separate the contact b/w circuits. After repair the contact is restored.

Earth wire

Earth wire is basically, grounding wires. When a very very large current is supplied, a wire is grounded so the extra amount of current goes into the ground.