

Unit 18: ELECTRONICS



SBBM
NOTES
SERIES

— Chapter 18 — — Electronics —

The notes of chapter 18 electronics is divided into following categories:

- 1 Quick Revision sheet notes
- 2 Topical wise notes with detailed theory
- 3 Side boxes with detailed explanation
- 4 Short response Questions with answers (Hot Questions)
- 5 MCQs with explanation
- 6 Exercise Short Questions with MCQs
- 7 Exercise numericals



Quick revision sheet



SEMICONDUCTORS & PN JUNCTION (DIODE) - Complete Guide

SEMICONDUCTORS

Materials that have conductivity between conductors and insulators

Key Points:

- Conduct electricity partially
- Doping alters electrical properties
- Used in electronic devices



N-TYPE SEMICONDUCTOR (Donor Impurity)

- Doped with Donor Atoms (Phosphorus - 5 valence electrons)
- Donor Atoms → Add free electrons
- Majority Carriers: Electrons (Negative charge)




P-TYPE SEMICONDUCTOR (Acceptor Impurity)

- Doped with Acceptor Atoms (Boron - 3 valence electrons)
- Acceptor Atoms → Create holes
- Majority Carriers: Holes (Positive charge)



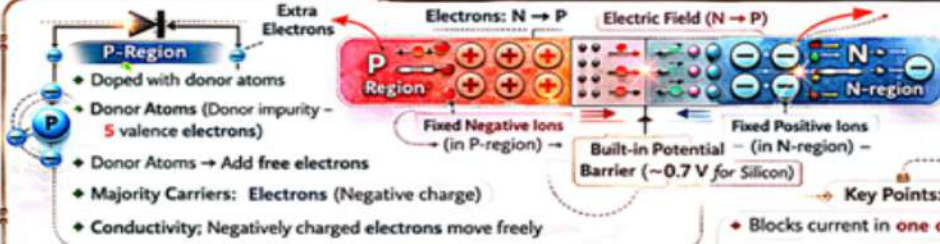PN JUNCTION (Diode) - Formation & Depletion Region



Key Points:

- Electrons diffuse from N → P
- Holes diffuse from P → N
- Fixed Positive Ions remain in N
- Fixed Negative Ions remain in P
- Electric Field forms from N to P
- Built-in Barrier (~0.7 V for Si)

Key Points:

- Blocks current in one direction
- Blocks reverse current


Acts as a Rectifier

- Allows current in one direction
- Blocks reverse current

Used in AC → DC conversion

Used in AC → DC conversion


Forward Bias (P connected to +, N to -)

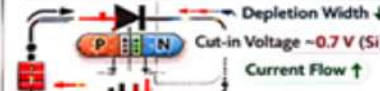

Reverse Bias (P connected to -, N to +)



I-V Curve of a Semiconductor Diode

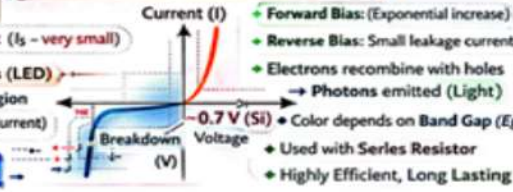

LIGHT EMITTING DIODE (LED)

- Compound Semiconductor (e.g., GaAs, GaP)
- Forward Biased PN junction
- Electrons + Holes → Recombine
- Energy Released as Photons (Visible Light)



DIGITAL ELECTRONICS

- A COMPLETE GUIDE -

Unit 18 - Electronics
OSBM One Page Revision Sheet

1. DIGITAL ELECTRONICS

Deals with Discrete Values (0 and 1) for Processing Data

IMPORTANT POINTS:

- Binary System: 0 & 1
- Uses Logic Gates
- High (1) = High Voltage
- Low (0) = Low Voltage

Switching Table

LOW (0)	HIGH (1)
0	1

(0 = Low Voltage, 1 = High Voltage)

2. UNIT OF DATA

ANALOGUE DATA
(Continuous Signal (Sound, Temperature))

DIGITAL DATA
Binary Data (0 and 1)

Units of Digital Data

- Bit = 0 or 1
- Nibble = 4 Bits
- Byte = 8 Bits
- Kilobyte (KB) = 1024 Bytes
- Megabyte (MB) = 1024 KB
- Gigabyte (GB) = 1024 MB

3. TYPES OF LOGIC GATES

Gate	Symbol	Boolean Expression	Truth Table															
AND Gate		$Y = A \cdot B$	<table border="1"> <tr><td>A</td><td>B</td><td>Y</td></tr> <tr><td>0</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>1</td><td>0</td></tr> <tr><td>1</td><td>0</td><td>0</td></tr> <tr><td>1</td><td>1</td><td>1</td></tr> </table>	A	B	Y	0	0	0	0	1	0	1	0	0	1	1	1
A	B	Y																
0	0	0																
0	1	0																
1	0	0																
1	1	1																
OR Gate		$Y = A + B$	<table border="1"> <tr><td>A</td><td>B</td><td>Y</td></tr> <tr><td>0</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>1</td></tr> </table>	A	B	Y	0	0	0	0	1	1	1	0	1	1	1	1
A	B	Y																
0	0	0																
0	1	1																
1	0	1																
1	1	1																
NOT Gate		$Y = \bar{A}$	<table border="1"> <tr><td>A</td><td>Y</td></tr> <tr><td>0</td><td>1</td></tr> <tr><td>1</td><td>0</td></tr> </table>	A	Y	0	1	1	0									
A	Y																	
0	1																	
1	0																	
NAND Gate		$Y = (A \cdot B)'$	<table border="1"> <tr><td>A</td><td>B</td><td>Y</td></tr> <tr><td>0</td><td>0</td><td>1</td></tr> <tr><td>0</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>0</td></tr> </table>	A	B	Y	0	0	1	0	1	1	1	0	1	1	1	0
A	B	Y																
0	0	1																
0	1	1																
1	0	1																
1	1	0																
NOR Gate		$Y = (A + B)'$	<table border="1"> <tr><td>A</td><td>B</td><td>Y</td></tr> <tr><td>0</td><td>0</td><td>1</td></tr> <tr><td>0</td><td>1</td><td>0</td></tr> <tr><td>1</td><td>0</td><td>0</td></tr> <tr><td>1</td><td>1</td><td>0</td></tr> </table>	A	B	Y	0	0	1	0	1	0	1	0	0	1	1	0
A	B	Y																
0	0	1																
0	1	0																
1	0	0																
1	1	0																

TRUTH TABLES

AND Gate	NOT Gate	A
A B Y	A Y	Y
0 0 1	0 1 0	
0 1 0	1 0 1	
1 0 0	1 1 0	
1 1 1		

5. TRUTH TABLES

AND Gate	NOT Gate	A
A B Y	A Y	Y
0 0 1	0 1	
0 1 1	1 0	
1 1 1	1 0	

NAND and NOR are Universal Gates

4. BOOLEAN EXPRESSIONS OF LOGIC GATES

- AND Gate: $Y = A \cdot B$
- OR Gate: $Y = A + B$
- NOT Gate: $Y = \bar{A}$
- NAND Gate: $Y = (A \cdot B)'$
- NOR Gate: $Y = (A + B)'$

7. ANALOGUE vs DIGITAL ELECTRONICS

Feature	Analogue	Digital	Examples
Signal Type	Continuous (e.g., sound)	Discrete (0 & 1)	Amplifier, Radio
Noise Effect	High	Low	Computer, Calculator
Accuracy	Less Accurate	Highly Accurate	Simple
Circuit Complexity	Complex	Simple	

6. USES OF LOGIC GATES

8. FUNDAMENTAL LOGIC GATES



DETAIL NOTES WITH SRQS AND MCQS


Semiconductors

A semiconductor is a material whose electrical conductivity falls between conductors and insulators. Their conductivity increases when temperature increases. They allow current to flow in a controlled way.

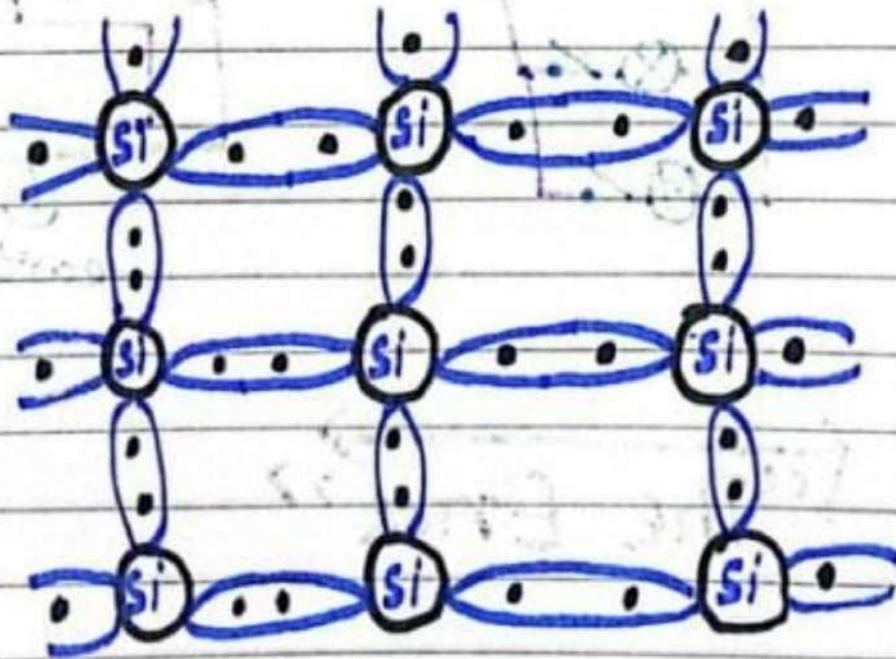Example: 1) Silicon (Si) 2) Germanium (Ge)

Explanation:

Atoms of Group IV-A of the periodic table are semiconductors. In pure silicon, atoms contain four electrons in the outer orbit. In a 2-D crystal lattice of silicon, bonds are formed by sharing of electrons – these are covalent bonds. All valence electrons of every Si atom are locked up in covalent bonds with the valence electrons of four neighbouring Si atoms.



2-D crystal lattice of silicon

Science Tidbits:

In semiconductors current is caused by both electrons and holes. If an external electric field is applied to the semiconductor, the electrons and holes move in opposite directions. Hence they both contribute to the flow of current through semiconductor material.



PKMZ – Semiconductors (Physics Kahani Mak Zabani)

Semiconductor woh material hai jiska electrical conductivity conductors aur insulators ke beech hoti hai. Jab temperature barhta hai to conductivity bhi barhti hai. Silicon aur Germanium iske main examples hain. Pure form mein yeh intrinsic hote hain, aur impurities mila do to extrinsic ban jate hain.

MCQS

1. Which of the following best describes a semiconductor?

- A) A material with zero electrical resistance
- B) A material with conductivity between conductors and insulators
- C) A material that only conducts electricity at high temperatures
- D) A material that never conducts electricity

Answer: B) A material with conductivity between conductors and insulators

Explanation: Semiconductors have electrical conductivity that falls between that of conductors (like copper) and insulators (like glass). They do not have zero resistance like superconductors, nor do they completely block current like insulators.

2. The most commonly used semiconductor material is:

- A) Germanium
- B) Carbon
- C) Silicon
- D) Gallium arsenide

Answer: C) Silicon

Explanation: Silicon is the most widely used semiconductor because it is abundantly available in the Earth's crust (as silica/sand), has a suitable band gap of 1.12 eV, and forms a stable oxide (SiO_2) that is essential in chip fabrication.

3. The energy gap (band gap) of a typical semiconductor is approximately:

- A) 0 eV

- B) 0.1–3 eV
- C) 5–10 eV
- D) Greater than 10 eV

Answer: B) 0.1–3 eV

Explanation: Semiconductors have a small forbidden energy gap of about 0.1–3 eV. This is small enough for electrons to be thermally or optically excited across it at room temperature. Insulators have gaps above 5 eV and conductors have zero gap (overlapping bands).

4. In a semiconductor, the valence band and conduction band are separated by:

- A) A large forbidden gap
- B) No gap at all
- C) A small forbidden gap
- D) An overlap

Answer: C) A small forbidden gap

Explanation: The defining feature of a semiconductor is its small forbidden gap (band gap). This distinguishes it from insulators (large gap) and conductors (no gap or overlap). The small gap allows controlled excitation of electrons.

5. Which of the following is a semiconductor?

- A) Copper
- B) Aluminium
- C) Germanium
- D) Silver

Answer: C) Germanium

Explanation: Copper, aluminium, and silver are all metals and good conductors. Germanium is a group IV element with a band gap of 0.67 eV, classifying it as a semiconductor along with silicon and gallium arsenide.

6. As temperature increases, the conductivity of a semiconductor:

- A) Decreases
- B) Increases
- C) Remains constant
- D) First increases then decreases

Answer: B) Increases

Explanation: Higher temperature provides more thermal energy to electrons, enabling more of them to jump across the small band gap into the conduction band. This increases the number of free carriers (both electrons and holes), increasing conductivity.

7. In the energy band diagram of a semiconductor at absolute zero, the conduction band is:

- A) Completely filled
- B) Partially filled
- C) Completely empty
- D) Overlapping with valence band

Answer: C) Completely empty

Explanation: At absolute zero (0 K), no thermal energy is available, so no electrons have enough energy to cross the band gap. The valence band is completely filled and the conduction band is completely empty, making the semiconductor behave like a perfect insulator.

8. Semiconductors have a crystal structure that is:

- A) Amorphous
- B) Ionic
- C) Covalent
- D) Metallic

Answer: C) Covalent

Explanation: Semiconductors like silicon and germanium form covalent crystal structures. Each atom shares its four valence electrons with four neighbouring atoms through covalent bonds, forming a regular tetrahedral lattice.

9. The property that makes semiconductors useful in electronics is:

- A) Their high conductivity
- B) Their resistance to heat
- C) The ability to control their conductivity
- D) Their magnetic properties

Answer: C) The ability to control their conductivity

Explanation: The most valuable property of semiconductors is that their conductivity can be precisely controlled through doping, temperature, light, or applied electric fields. This controllability is the foundation of all semiconductor devices like transistors and diodes.

10. Which of the following is NOT a semiconductor?

- A) Silicon
- B) Germanium
- C) Copper
- D) Gallium arsenide

Answer: C) Copper

Explanation: Copper is a metal and an excellent conductor with overlapping valence and conduction bands (no band gap). Silicon, germanium, and gallium arsenide all have small band gaps and are classified as semiconductors.

11. The valence electrons in a semiconductor are involved in:

- A) Ionic bonds
- B) Covalent bonds
- C) Metallic bonds

D) Hydrogen bonds

Answer: B) Covalent bonds

Explanation: In semiconductor crystals (e.g., silicon), each atom has four valence electrons that are shared with four neighbouring atoms to form four covalent bonds. These shared electron pairs hold the crystal together and fill the valence band completely at low temperatures.

12. Intrinsic semiconductors are:

- A) Heavily doped semiconductors
- B) Pure semiconductors with no impurities
- C) Semiconductors with donor atoms
- D) Semiconductors with acceptor atoms

Answer: B) Pure semiconductors with no impurities

Explanation: An intrinsic semiconductor is a chemically pure semiconductor with no intentionally added impurities. Its electrical properties are determined solely by the material itself. Charge carriers are generated only through thermal or optical excitation across the band gap.

13. In an intrinsic semiconductor, the number of free electrons equals:

- A) Zero
- B) The number of holes
- C) The number of protons
- D) The number of donor atoms

Answer: B) The number of holes

Explanation: In an intrinsic (pure) semiconductor, every electron that is excited to the conduction band leaves behind exactly one hole in the valence band. Therefore, free electrons and holes are always generated in equal numbers:

$$n = p = n_i$$

14. The forbidden energy gap of silicon at room temperature is approximately:

- A) 0.67 eV
- B) 1.12 eV
- C) 3.5 eV
- D) 5.0 eV

Answer: B) 1.12 eV

Explanation: Silicon has a band gap of approximately 1.12 eV at room temperature (300 K). This is large enough to make it stable at room temperature but small enough for doping and device operation. Germanium has a smaller gap of 0.67 eV.

15. The forbidden energy gap of germanium at room temperature is approximately:

- A) 0.67 eV
- B) 1.12 eV
- C) 3.5 eV
- D) 5.0 eV

Answer: A) 0.67 eV

Explanation: Germanium has a band gap of approximately 0.67 eV at room temperature. Its smaller gap compared to silicon (1.12 eV) means germanium has more thermally generated carriers at the same temperature, making it more sensitive to temperature changes.

16. Which semiconductor has a larger band gap?

- A) Germanium
- B) Silicon
- C) Indium antimonide
- D) Lead sulphide

Answer: B) Silicon

Explanation: Silicon has a band gap of 1.12 eV, which is larger

than germanium (0.67 eV), indium antimonide (~ 0.17 eV), and lead sulphide (~ 0.37 eV). The larger band gap makes silicon more thermally stable and suitable for high-temperature operation.

17. At absolute zero temperature, a pure semiconductor behaves as:

- A) A conductor
- B) A superconductor
- C) An insulator
- D) A resistor

Answer: C) An insulator

Explanation: At 0 K, all valence electrons are locked in covalent bonds. No electron has sufficient thermal energy to cross the band gap, leaving the conduction band completely empty. With no free charge carriers available, the semiconductor cannot conduct electricity and behaves as a perfect insulator.

18. Thermal energy at room temperature can excite electrons from the valence band to the conduction band because:

- A) The band gap is very large
- B) The band gap is zero
- C) The band gap is small enough
- D) Metals have large band gaps

Answer: C) The band gap is small enough

Explanation: The thermal energy available at room temperature ($kT \approx 0.026$ eV at 300 K) is comparable to the small band gap of semiconductors (~ 0.67 – 1.12 eV). A small fraction of electrons gain enough energy to be excited across this gap, creating free carriers.

19. Which type of charge carriers exist in a semiconductor?

- A) Only electrons
- B) Only holes
- C) Both electrons and holes
- D) Only protons

Answer: C) Both electrons and holes

Explanation: In a semiconductor, two types of charge carriers exist: free electrons in the conduction band (negative charge) and holes in the valence band (positive charge). Both contribute to electrical conduction. Protons are fixed in atomic nuclei and do not move through the crystal.

20. A hole in a semiconductor is best described as:

- A) A free electron
- B) The absence of an electron in the valence band
- C) A negatively charged ion
- D) A proton

Answer: B) The absence of an electron in the valence band

Explanation: A hole is the vacancy (empty state) left in the valence band when an electron is excited to the conduction band. It behaves as a positive charge carrier because when a neighbouring electron fills it, the hole appears to move in the opposite direction – equivalent to positive charge movement.

21. When an electron moves from the valence band to the conduction band, it leaves behind:

- A) A proton
- B) A neutron
- C) A hole
- D) A photon

Answer: C) A hole

Explanation: When thermal or light energy excites an electron across the band gap, the covalent bond it occupied becomes incomplete. This empty state in the valence band is called a hole. It acts as a positive charge carrier that participates in electrical conduction.

22. In an intrinsic semiconductor, the Fermi level lies:

- A) At the top of the valence band
- B) At the bottom of the conduction band
- C) Approximately in the middle of the band gap
- D) Above the conduction band

Answer: C) Approximately in the middle of the band gap

Explanation: The Fermi level represents the energy at which the probability of finding an electron is 50%. In an intrinsic semiconductor, because electrons and holes are equal in number, the Fermi level falls roughly in the middle of the forbidden gap.

23. Which of the following processes generates electron-hole pairs in a semiconductor?

- A) Doping
- B) Thermal excitation
- C) Magnetization
- D) Polarization

Answer: B) Thermal excitation

Explanation: Thermal excitation provides energy to valence electrons, allowing them to jump the band gap into the conduction band, simultaneously creating holes. Doping changes the type of carriers but doesn't generate pairs the same way. Magnetization and polarization do not generate electron-hole pairs.

24. Recombination in a semiconductor refers to:

- A) An electron joining a hole
- B) An electron leaving the conduction band for ground state
- C) A hole attracting an ion
- D) A conductor gaining electrons

Answer: A) An electron joining a hole

Explanation: Recombination is the process where a free electron in the conduction band falls into a hole in the valence band, annihilating both carriers. The energy released during recombination can be emitted as heat (phonons) or light (photons), the latter being the principle behind LEDs.

25. Semiconductors are primarily used in:

- A) Power lines
- B) Electronic devices such as diodes and transistors
- C) Electromagnets
- D) Heating elements

Answer: B) Electronic devices such as diodes and transistors

Explanation: Semiconductors form the basis of all modern electronic devices including diodes, transistors, integrated circuits, solar cells, and LEDs. Power lines use metals (conductors), electromagnets use coiled conductors, and heating elements use resistive alloys – none of which are semiconductor applications.

26. The resistivity of a semiconductor is typically in the range of:

- A) 10^{-8} to $10^{-6} \Omega \cdot m$
- B) 10^{-4} to $10^4 \Omega \cdot m$
- C) 10^8 to $10^{16} \Omega \cdot m$
- D) $10^{20} \Omega \cdot m$

Answer: B) 10^{-4} to $10^4 \Omega \cdot m$

Explanation: Semiconductors have resistivities in the range 10^{-4} to $10^4 \Omega \cdot m$, between metals (10^{-8} to $10^{-6} \Omega \cdot m$) and insulators (10^8 to $10^{16} \Omega \cdot m$). This intermediate resistivity can be precisely tuned through doping, making semiconductors versatile for device fabrication.

27. Compared to metals, semiconductors have:

- A) Lower resistivity
- B) Higher resistivity
- C) The same resistivity
- D) Zero resistivity

Answer: B) Higher resistivity

Explanation: Metals have very low resistivity ($10^{-8} \Omega \cdot m$) due to the large number of free electrons from overlapping bands. Semiconductors have far fewer free carriers at room temperature, resulting in much higher resistivity. This changes with temperature – semiconductors become more conductive as temperature rises, unlike metals.

28. The mobility of electrons in a semiconductor is:

- A) Always greater than that of holes
- B) Always less than that of holes
- C) Equal to that of holes
- D) Independent of temperature

Answer: A) Always greater than that of holes

Explanation: Electron mobility is always higher than hole mobility in semiconductors because electrons move through the conduction band (nearly empty), while holes move through the valence band (nearly full) by sequential electron hops – a slower, indirect process.

29. Which of the following best explains why semiconductors

are used in computer chips?

- A) They are cheap
- B) Their electrical properties can be precisely controlled
- C) They have very low melting points
- D) They are good heat conductors

Answer: B) Their electrical properties can be precisely controlled

Explanation: The key reason semiconductors are used in chips is that their conductivity can be precisely engineered through doping and controlled by electric fields (as in transistors). This allows billions of transistors to act as on/off switches, forming the logic gates of a processor.

30. In a semiconductor crystal, each silicon atom shares electrons with:

- A) One neighbor
- B) Two neighbors
- C) Three neighbors
- D) Four neighbors

Answer: D) Four neighbors

Explanation: Silicon is in Group IV of the periodic table and has four valence electrons. It forms four covalent bonds by sharing one electron with each of four neighbouring silicon atoms in a tetrahedral arrangement.

31. The covalent bonds in a semiconductor are formed by sharing of:

- A) One electron
- B) Two electrons
- C) Three electrons
- D) Four electrons

Answer: B) Two electrons

Explanation: Each covalent bond between two semiconductor atoms consists of two shared electrons – one from each atom. Silicon shares one of its four valence electrons with each neighbour, and each neighbour reciprocates. Each bond therefore contains two electrons.

32. Which of the following correctly lists semiconductors?

- A) Iron, copper, aluminium
- B) Silicon, germanium, gallium arsenide
- C) Sodium, potassium, lithium
- D) Neon, argon, krypton

Answer: B) Silicon, germanium, gallium arsenide

Explanation: Iron, copper, and aluminium are metals (conductors). Sodium, potassium, and lithium are alkali metals (conductors). Neon, argon, and krypton are noble gases (insulators). Silicon, germanium, and gallium arsenide all have appropriate band gaps and are classified as semiconductors.

33. As light is shone on a semiconductor, its conductivity:

- A) Decreases
- B) Remains same
- C) Increases
- D) Becomes zero

Answer: C) Increases

Explanation: When photons with energy equal to or greater than the band gap strike a semiconductor, they excite electrons from the valence band to the conduction band, creating electron-hole pairs. This increases the number of free charge carriers, increasing conductivity – a phenomenon known as photoconductivity.

34. The process by which light generates electron-hole pairs

in a semiconductor is called:

- A) Thermionic emission
- B) Photoelectric effect
- C) Photoconductivity
- D) Recombination

Answer: C) Photoconductivity

Explanation: Photoconductivity is the phenomenon where light absorption in a semiconductor generates electron-hole pairs, increasing electrical conductivity. Thermionic emission is emission of electrons from hot metals. The photoelectric effect (external) involves electrons escaping the surface. Recombination is the reverse process.

35. Compound semiconductors like gallium arsenide (GaAs) are used because:

- A) They are cheaper than silicon
- B) They have higher electron mobility and direct band gap
- C) They are more abundant
- D) They require no doping

Answer: B) They have higher electron mobility and direct band gap

Explanation: GaAs has electron mobility about 6x higher than silicon, enabling faster devices. Crucially, it has a direct band gap, meaning electrons can recombine with holes while emitting photons efficiently – essential for LEDs and laser diodes. Silicon has an indirect band gap, making optical emission inefficient.

SRQS

Q1. Define a semiconductor and give two examples.

Answer: A semiconductor is a material whose electrical conductivity lies between that of a conductor and an insulator. Examples: Silicon (Si) and Germanium (Ge).

Q2. What is an energy band gap in semiconductors?

Answer: The energy band gap (forbidden gap) is the energy difference between the top of the valence band and the bottom of the conduction band. In semiconductors, this gap is small (approx. 0.1–3 eV), allowing electrons to be thermally excited across it.

Q3. Explain why conductivity of a semiconductor increases with temperature.

Answer: As temperature rises, more electrons gain sufficient thermal energy to cross the small band gap from the valence band to the conduction band. This increases the number of free charge carriers (electrons and holes), thus increasing conductivity.

Q4. What is an intrinsic semiconductor?

Answer: An intrinsic semiconductor is a pure semiconductor with no added impurities. In it, free electrons and holes are generated solely by thermal excitation, and the number of free electrons equals the number of holes.

Q5. What is a hole in semiconductor physics?

Answer: A hole is a vacancy left in the valence band when an electron is excited to the conduction band. It behaves as a positive charge carrier and moves in the opposite direction to electrons under an electric field.

Q6. How does light affect the conductivity of a semiconductor?

Answer: When light of sufficient energy falls on a semiconductor, photons provide energy to electrons, exciting

them from the valence band to the conduction band. This creates additional electron-hole pairs, increasing conductivity – a phenomenon called photoconductivity.

Q7. State the difference between a conductor, semiconductor, and insulator in terms of energy bands.

Answer: In conductors, the valence and conduction bands overlap (no gap). In semiconductors, there is a small forbidden gap ($\sim 0.1-3$ eV). In insulators, the forbidden gap is very large (>5 eV), making electron excitation practically impossible at room temperature.

Q8. What is electron-hole recombination?

Answer: Recombination occurs when a free electron in the conduction band falls back into a hole in the valence band. The electron-hole pair is annihilated and energy is released, often as heat or light (as in LEDs).

Q9. Why is silicon more widely used than germanium in electronic devices?

Answer: Silicon has a larger band gap (1.12 eV vs 0.67 eV for Ge), making it more stable at higher temperatures. It is also more abundant, cheaper, and forms a stable oxide (SiO_2) useful in fabrication.

Q10. What is the Fermi level in an intrinsic semiconductor?

Answer: The Fermi level in an intrinsic semiconductor lies approximately at the middle of the band gap. It represents the energy level at which the probability of finding an electron is 50%, and its position indicates the balance between electrons and holes.

N and P Type Semiconductors

Types of Semiconductor

1) Intrinsic Semiconductor

Intrinsic semiconductors are in pure form and there are no impurities added.

Example: 1) Pure silicon 2) Pure germanium

2) Extrinsic Semiconductor

Extrinsic semiconductors are in impure form where impurities are doped to increase conductivity. Materials such as phosphorus (P) and aluminium (Al) are added to silicon to modify its electrical properties and make it more suitable for electronic conductivity.

Example: Adding phosphorus to silicon results in a free electron – which is impure silicon.


Types of Extrinsic Semiconductor

1) N-Type Semiconductor


N-type semiconductor is an extrinsic semiconductor formed when a pentavalent impurity is added to a pure semiconductor like silicon and germanium. The word 'N' stands for negative, indicating electrons as majority carriers.

Detail: When a pentavalent impurity (Group V-A elements) such as phosphorus is added to Si, the resulting mixture is called N-type. Four valence electrons of every phosphorus atom are locked up in covalent bonds with valence electrons of four neighbouring Si atoms. However, the 5th valence

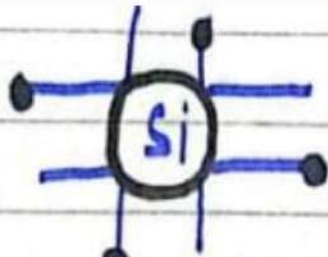electron of phosphorus atom does not find a binding electron and thus remains free to go float in the material.




four valence electrons

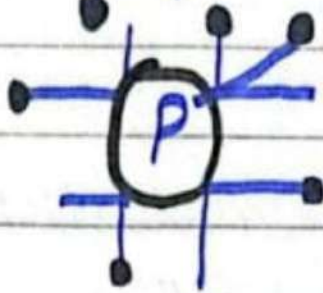

five valence electrons

Adding pentavalent impurities to Si ↓

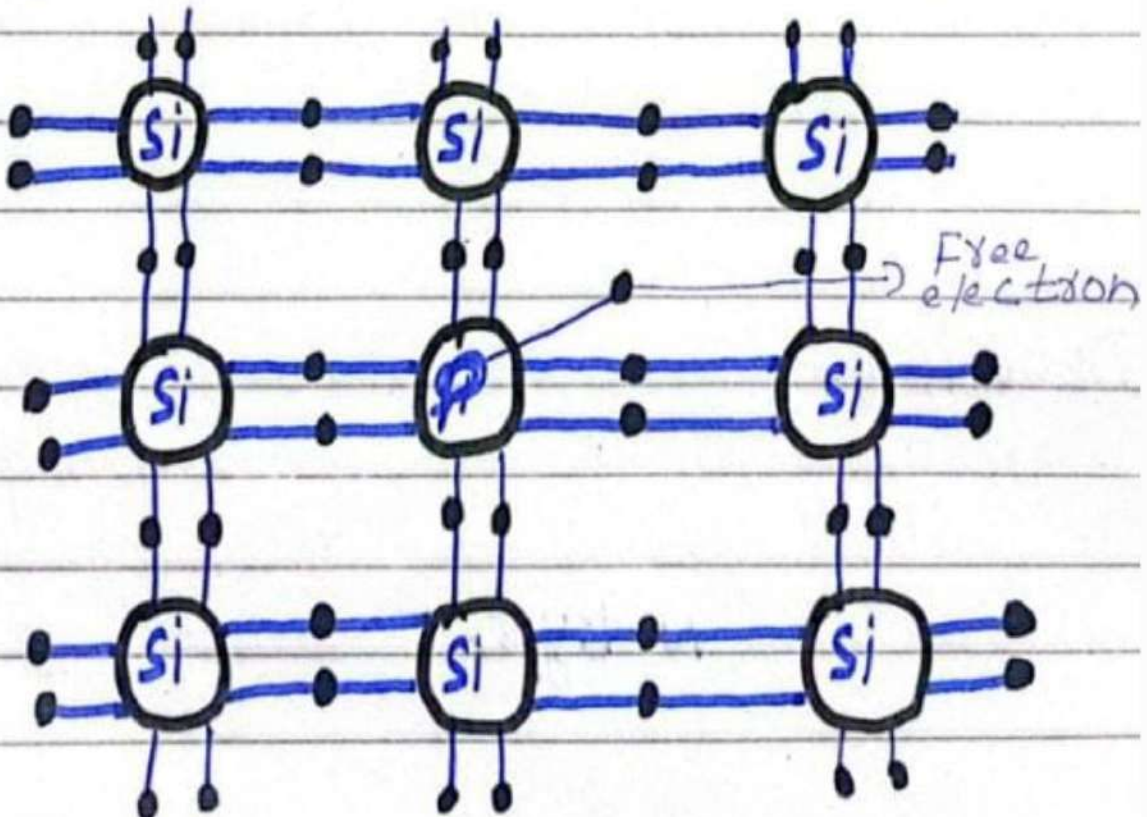

PKMZ

Silicon Chicken Story

Socho ek farm hai jahan sirf silicon chickens rehti hain.

Har chicken ke paas 4 chicks hain (jaise silicon ke 4 valence electrons).

Sab chickens apne 4-4 chicks ke saath perfectly balanced hain. System bilkul stable hai.

Ab agar hum is group mein ek duck add kar dein...

Duck thori different hai.

Us ke paas 5 chicks hain (extra one).

Ab kya hoga?

Woh 4 chicks to bonding mein use ho jayenge,

lekin 1 chick extra bach jayega

Yeh extra chick free ho kar idhar-udhar move karega.

Is wajah se system mein extra electrons ho jate hain.

Is tarah yeh ban gaya:

👉 N-Type Semiconductor

(Kyun ke negative charge yani electrons zyada ho gaye)

Aur jis process se hum ne duck add kiya usay kehte hain:

Doping Process



(Pure silicon mein impurity add karna)

2) P-Type Semiconductor

A P-type semiconductor is an extrinsic semiconductor formed when a trivalent impurity is added to a pure semiconductor like silicon or germanium. The word 'P' stands for positive, indicating holes as majority carriers.

Detail: When trivalent impurities (Group III-A elements) such as boron is added to Si, the resulting mixture is called P-

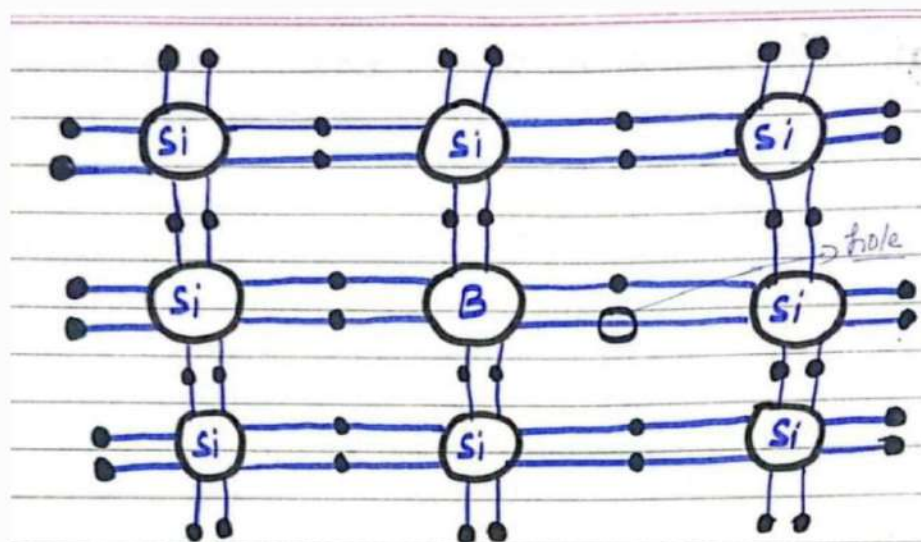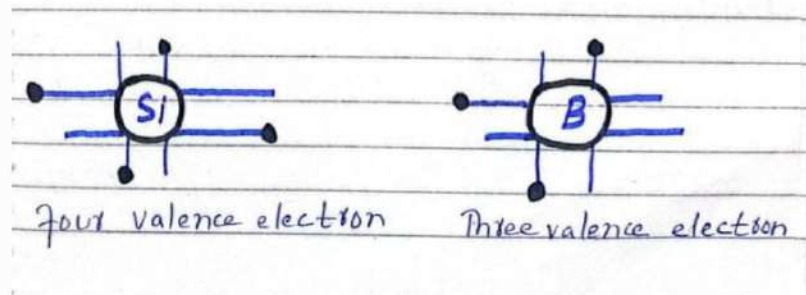type. Three valence electrons of every boron atom are locked up in covalent bonds with valence electrons of three neighbouring Si atoms. However, the fourth electron of the Si atom remains unpaired. A vacant spot called a hole is created within the covalent bond between one boron atom and a neighbouring Si atom. These holes are considered to be positive charge carriers.




Comparison of N-Type and P-Type Semiconductors:

Aspect	N-Type	P-Type
Impurity added	Pentavalent (Group V-A) e.g. Phosphorus	Trivalent (Group III-A) e.g. Boron
Majority carriers	Free electrons	Holes
Minority carriers	Holes	Free electrons
Charge of majority carrier	Negative	Positive
Extra particle	Surplus electron (5th valence e^-)	Vacant spot (hole)
Example dopant	Phosphorus (P), Arsenic (As)	Boron (B), Aluminium (Al)

PKMZ

Silicon ladki wale hain aur unhen teen shadiyan karani hai woh kahta Hai ka teen ladka lekar aana lekin rishte wale kahate Hain ki hamare pass char ladka Ham char hi ladke laenge... Aur Is Tarah Jo ek ladka rah jaega uske liye koî bahar se electron aaega... To tabhi uski shaadi ho sakti hai... Yahan bahar se electron aane se ya FIR andar ek electrons ki Khali jagha reh jai gi ..ek electron Khali ho jayega Yahan holes create honge... Yeh holes positive honge ..these holes behaves like a positive charge ...

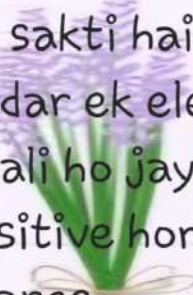

MCQs

1. A PN junction is formed by:

- A) Joining two metals
- B) Joining P-type and N-type semiconductors
- C) Doping silicon with two impurities simultaneously
- D) Exposing silicon to UV light

Answer: B) Joining P-type and N-type semiconductors

Explanation: A PN junction is created when P-type and N-type semiconductor regions are brought into intimate contact. At the interface, diffusion of majority carriers creates the depletion region and built-in electric field,

forming the fundamental structure of diodes and transistors.

2. The depletion region in a PN junction is:

- A) A region with excess charge carriers
- B) A region depleted of free charge carriers
- C) A region of high current
- D) A region with donor atoms only

Answer: B) A region depleted of free charge carriers

Explanation: The depletion region forms at the PN junction where electrons from the N-side and holes from the P-side have diffused across and recombined. This leaves behind fixed ionic charges but no mobile (free) carriers. It is 'depleted' of free electrons and holes, acting as an insulating barrier.

3. The built-in potential (contact potential) of a PN junction is caused by:

- A) External battery voltage
- B) Diffusion of carriers and formation of depletion region
- C) The crystal structure of silicon
- D) High temperature

Answer: B) Diffusion of carriers and formation of depletion region

Explanation: When the junction is formed, electrons diffuse from N to P and holes from P to N due to concentration gradients. Recombination near the junction leaves fixed positive ions (N-side) and fixed negative ions (P-side). This charge separation creates the built-in potential which opposes further diffusion.

4. The built-in potential of a silicon PN junction is approximately:

- A) 0.1 V

- B) 0.3 V
- C) 0.7 V
- D) 5 V

Answer: C) 0.7 V

Explanation: The built-in potential (contact potential) of silicon is approximately 0.7 V at room temperature. This is the voltage that must be overcome by an applied forward bias before significant current flows.

5. The built-in potential of a germanium PN junction is approximately:

- A) 0.7 V
- B) 0.3 V
- C) 1.2 V
- D) 0.0 V

Answer: B) 0.3 V

Explanation: Germanium has a smaller band gap (0.67 eV) than silicon (1.12 eV), resulting in a smaller built-in potential of approximately 0.3 V. This is why germanium diodes have a lower forward threshold voltage (~ 0.3 V) compared to silicon diodes (~ 0.7 V).

6. Forward bias of a PN junction means:

- A) Positive terminal of battery connected to N-side
- B) Positive terminal of battery connected to P-side
- C) No battery connected
- D) A.C. signal applied

Answer: B) Positive terminal of battery connected to P-side

Explanation: Forward bias is applied when the positive terminal of the external battery is connected to the P-side and the negative terminal to the N-side. This external voltage opposes the built-in potential, reducing the barrier,

narrowing the depletion region, and allowing majority carriers to flow.

7. In forward bias, the depletion region:

- A) Widens
- B) Narrows and eventually disappears
- C) Stays the same
- D) Fills with electrons

Answer: B) Narrows and eventually disappears

Explanation: When forward biased, the external electric field opposes the built-in field of the depletion region. Majority carriers are pushed toward the junction, injecting carriers and causing recombination. This narrows the depletion region until the barrier is overcome and large current flows.

8. In reverse bias, the depletion region:

- A) Narrows
- B) Widens
- C) Stays the same
- D) Disappears

Answer: B) Widens

Explanation: In reverse bias, the external field adds to the built-in field, pulling majority carriers away from the junction. This widens the depletion region and increases the potential barrier, further blocking current flow.

9. When a PN junction is forward biased, the current:

- A) Does not flow
- B) Flows easily (large current)
- C) Is very small
- D) Is alternating

Answer: B) Flows easily (large current)

Explanation: In forward bias, once the applied voltage

exceeds the threshold (0.7 V for Si), the depletion region is overcome and majority carriers flow freely across the junction. The current increases exponentially with voltage according to the diode equation.

10. When a PN junction is reverse biased, the current:

- A) Flows easily
- B) Is very large
- C) Is very small (almost zero)
- D) Alternates direction

Answer: C) Is very small (almost zero)

Explanation: Under reverse bias, the depletion region widens and the potential barrier increases, blocking majority carrier flow. Only a very small reverse saturation current (typically nanoamperes for Si) flows, due to minority carriers being swept across the junction.

11. The small current in reverse bias is due to:

- A) Majority carriers
- B) Minority carriers crossing the junction
- C) Protons moving
- D) Magnetic effects

Answer: B) Minority carriers crossing the junction

Explanation: The reverse saturation current is carried by minority carriers: thermally generated holes in the N-region and electrons in the P-region. The built-in electric field (enhanced by reverse bias) sweeps these minority carriers across the junction.

12. A PN junction acts as a:

- A) Transistor
- B) Resistor
- C) Diode (one-way valve for current)

D) Capacitor

Answer: C) Diode (one-way valve for current)

Explanation: A PN junction is the basic structure of a diode. It allows large current in forward bias (low resistance) and blocks current in reverse bias (high resistance). This asymmetric, one-directional conduction enables rectification of alternating current.

13. In the depletion region of a PN junction:

A) There are many free electrons and holes

B) There are no free charge carriers

C) Only electrons exist

D) Only holes exist

Answer: B) There are no free charge carriers

Explanation: The depletion region is named because it is depleted of mobile (free) charge carriers. Electrons and holes that diffused into this region have recombined, leaving only fixed ionic charges.

14. The electric field in the depletion region points:

A) From P-side to N-side

B) From N-side to P-side

C) Parallel to the junction

D) In all directions

Answer: B) From N-side to P-side

Explanation: The depletion region contains fixed positive ions on the N-side and fixed negative ions on the P-side. Electric field lines point from positive to negative charges, i.e., from the N-side to the P-side.

15. The process by which electrons diffuse from N-side to P-side initially is due to:

A) Electric field

- B) Concentration gradient
- C) Temperature gradient
- D) Magnetic field

Answer: B) Concentration gradient

Explanation: Initially, the N-side has a high concentration of free electrons and the P-side has a low concentration. According to Fick's Law of diffusion, particles move from regions of high concentration to low concentration. This concentration gradient drives electrons from N to P.

16. The I-V characteristic of a PN junction diode shows:

- A) Linear relationship in both directions
- B) Exponential increase in forward bias and tiny current in reverse bias
- C) Equal current in both directions
- D) No current in any direction

Answer: B) Exponential increase in forward bias and tiny current in reverse bias

Explanation: The diode's I-V curve is highly non-linear and asymmetric. In forward bias, after the threshold voltage, current increases exponentially. In reverse bias, current is approximately constant at the small reverse saturation current until breakdown.

17. Breakdown in a reverse-biased PN junction occurs at:

- A) Very low reverse voltage
- B) The threshold voltage
- C) A sufficiently high reverse voltage
- D) Any forward voltage

Answer: C) A sufficiently high reverse voltage

Explanation: Reverse breakdown occurs when the reverse voltage exceeds the breakdown voltage. At this point, the

electric field becomes strong enough to generate new electron-hole pairs (avalanche) or allow quantum tunnelling (Zener), causing a sudden large increase in reverse current.

18. Zener breakdown refers to:

- A) Avalanche multiplication of carriers
- B) Quantum tunnelling of carriers through a thin depletion region
- C) Thermal destruction of the diode
- D) Recombination of carriers

Answer: B) Quantum tunnelling of carriers through a thin depletion region

Explanation: Zener breakdown occurs in heavily doped junctions with very thin depletion regions. Under high reverse voltage, quantum mechanical tunnelling allows valence electrons to tunnel directly through the thin energy barrier into the conduction band without requiring impact ionization.

19. Avalanche breakdown in a PN junction is caused by:

- A) Tunnelling effect
- B) High-energy carriers colliding and creating new electron-hole pairs
- C) Reverse saturation current
- D) Recombination

Answer: B) High-energy carriers colliding and creating new electron-hole pairs

Explanation: Avalanche breakdown occurs when the reverse electric field accelerates minority carriers to high enough velocities that they collide with lattice atoms with sufficient energy to break covalent bonds, generating new electron-hole pairs – a rapid multiplication (avalanche) effect.

20. The knee voltage (threshold voltage) in forward bias of silicon is approximately:

- A) 0.3 V
- B) 0.7 V
- C) 1.2 V
- D) 5 V

Answer: B) 0.7 V

Explanation: The knee voltage for silicon is approximately 0.7 V. Below this voltage, negligible current flows because the built-in potential barrier hasn't been overcome. Once this threshold is exceeded, the current rises exponentially. For germanium, the knee voltage is ~ 0.3 V.

21. A PN junction is used as a rectifier because:

- A) It amplifies signals
- B) It allows current to flow in one direction only
- C) It stores charge
- D) It emits light

Answer: B) It allows current to flow in one direction only

Explanation: Rectification is the conversion of A.C. to D.C. A PN junction diode conducts easily in forward bias and blocks current in reverse bias – it is essentially a one-way switch for current. When connected to an A.C. source, it allows only one half of the cycle to pass.

22. In a forward-biased PN junction, majority carriers:

- A) Move away from the junction
- B) Cross the junction and recombine
- C) Are blocked by the depletion region
- D) Move into the depletion region and stay

Answer: B) Cross the junction and recombine

Explanation: Under forward bias, the reduced potential

barrier allows majority carriers to cross the junction: electrons from the N-side enter the P-side and holes from the P-side enter the N-side. Once they cross, they become minority carriers and eventually recombine with local majority carriers.

23. What happens to the width of the depletion region when forward bias voltage equals the built-in potential?

- A) It doubles
- B) It becomes zero (junction conducts freely)
- C) It widens
- D) It stays the same

Answer: B) It becomes zero (junction conducts freely)

Explanation: When the applied forward voltage equals the built-in potential (0.7 V for Si), the external field exactly cancels the internal field of the depletion region. The potential barrier is eliminated, the depletion region width approaches zero, and majority carriers flow freely.

24. In reverse bias, the majority carriers:

- A) Cross the junction easily
- B) Are pushed away from the junction, widening the depletion region
- C) Recombine at the junction
- D) Tunnel through the depletion region

Answer: B) Are pushed away from the junction, widening the depletion region

Explanation: Under reverse bias, the external field reinforces the built-in field. Electrons (majority carriers in N-type) are attracted toward the positive terminal and move away from the junction. Similarly, holes (majority in P-type) move away from the junction.

25. The reverse saturation current (I_0) in a PN junction diode is:

- A) Very large
- B) Zero
- C) Very small and relatively temperature-dependent
- D) Equal to the forward current

Answer: C) Very small and relatively temperature-dependent

Explanation: The reverse saturation current I_0 is extremely small (picoamperes to nanoamperes for Si) because it depends only on thermally generated minority carriers. However, I_0 approximately doubles for every 10°C rise in temperature.

26. Light-emitting diodes (LEDs) are based on:

- A) Avalanche breakdown
- B) Recombination of electrons and holes releasing photons at forward-biased PN junction
- C) Reverse bias operation
- D) Photoelectric effect

Answer: B) Recombination of electrons and holes releasing photons at forward-biased PN junction

Explanation: In a forward-biased PN junction, electrons crossing from N to P recombine with holes. In direct band gap semiconductors (like GaAs, GaN), this recombination releases energy as photons (light). The wavelength (colour) of emitted light depends on the band gap energy.

27. Photodiodes operate in:

- A) Forward bias
- B) Reverse bias
- C) Zero bias with no external voltage
- D) Both forward and reverse bias simultaneously

Answer: B) Reverse bias

Explanation: Photodiodes are operated under reverse bias. Incident light generates electron-hole pairs in the depletion region. The built-in electric field (enhanced by reverse bias) sweeps these carriers apart, creating a photocurrent proportional to light intensity.

28. The diffusion current in a PN junction flows:

- A) From N to P due to minority carriers
- B) From P to N due to majority carrier diffusion
- C) Only under external voltage
- D) Only in reverse bias

Answer: B) From P to N due to majority carrier diffusion

Explanation: Diffusion current is caused by majority carriers moving down their concentration gradients: electrons diffuse from N (high) to P (low), and holes diffuse from P (high) to N (low). The net diffusion current flows from P to N inside the junction.

29. The drift current in a PN junction is caused by:

- A) Majority carrier diffusion
- B) Minority carriers swept by the electric field in the depletion region
- C) External battery
- D) Temperature gradient

Answer: B) Minority carriers swept by the electric field in the depletion region

Explanation: Drift current is due to minority carriers being swept across the junction by the built-in electric field. Minority electrons on the P-side are swept to the N-side, and minority holes on the N-side are swept to the P-side.

30. At equilibrium (no external voltage), the net current

across a PN junction is:

- A) Maximum
- B) Equal to diffusion current
- C) Zero
- D) Equal to drift current

Answer: C) Zero

Explanation: At equilibrium, the diffusion current (majority carriers moving down concentration gradient) and drift current (minority carriers swept by built-in field) are exactly equal and opposite. The net current across the junction is therefore zero.

31. A diode in forward bias has:

- A) High resistance
- B) Low resistance
- C) Infinite resistance
- D) Variable resistance that increases with voltage

Answer: B) Low resistance

Explanation: In forward bias (above threshold voltage), the depletion region narrows, the potential barrier is reduced, and majority carriers flow freely. This results in a large current for a small voltage – the diode has low dynamic resistance.

32. A diode in reverse bias has:

- A) Low resistance
- B) High resistance
- C) Zero resistance
- D) Variable resistance that decreases with voltage

Answer: B) High resistance

Explanation: In reverse bias, the depletion region widens, forming a wide insulating barrier. Only the tiny reverse

saturation current (nanoamperes) flows. This gives the diode very high reverse resistance (megaohms), effectively blocking current.

33. In half-wave rectification using a PN junction diode:

- A) Both halves of A.C. are converted to D.C.
- B) Only one half of the A.C. cycle passes through
- C) The diode amplifies the signal
- D) The output is a pure D.C.

Answer: B) Only one half of the A.C. cycle passes through

Explanation: In a half-wave rectifier, the diode is forward biased during one half-cycle of the A.C. input (conducts, passes current) and reverse biased during the other half-cycle (blocks current). The output is a pulsating D.C. containing only positive half-cycles.

34. The depletion region in a PN junction is formed due to:

- A) External voltage
- B) Diffusion of majority carriers across the junction and recombination
- C) Movement of ions from outside
- D) Heating the semiconductor

Answer: B) Diffusion of majority carriers across the junction and recombination

Explanation: The depletion region forms spontaneously when P and N regions are joined. Majority carriers diffuse across the junction and recombine near the junction, removing free carriers from the region — leaving a zone depleted of mobile charges bounded by fixed ionic charges.

35. In a PN junction, donor ions on the N-side and acceptor ions on the P-side near the junction are:

- A) Mobile and free to move

- B) Fixed in the crystal lattice and create an electric field
- C) Neutralized by free carriers
- D) Converted to neutral atoms

Answer: B) Fixed in the crystal lattice and create an electric field

Explanation: After donor atoms on the N-side release their extra electrons, they become positive ions firmly embedded in the crystal lattice – they cannot move. Similarly, acceptor ions on the P-side are negative and fixed. These immobile fixed charges create the built-in electric field of the depletion region.

SRQs

Q1. What is a PN junction and how is it formed?

Answer: A PN junction is formed when P-type and N-type semiconductor materials are joined together. At the junction, free electrons from the N-side diffuse into the P-side and recombine with holes, leaving behind fixed positive and negative ions that create a depletion region and a built-in electric field.

Q2. Explain the formation of the depletion region.

Answer: When P and N semiconductors are joined, electrons diffuse from N-side to P-side (and holes from P to N) due to concentration gradients. Recombination near the junction removes free carriers, leaving fixed ionic charges. This carrier-depleted zone is called the depletion region. It has a built-in electric field that eventually stops further diffusion.

Q3. What is forward bias and what happens to the depletion region?

Answer: Forward bias occurs when the positive terminal of a battery is connected to the P-side and the negative terminal to the N-side. This reduces the built-in potential, narrows the depletion region, and allows majority carriers to cross the junction, resulting in a large current flow.

Q4. What is reverse bias and what happens to current flow?

Answer: Reverse bias occurs when the positive terminal is connected to the N-side and the negative terminal to the P-side. This increases the built-in potential and widens the depletion region, preventing majority carriers from crossing. Only a tiny reverse saturation current due to minority carriers flows.

Q5. Explain why a PN junction acts as a diode (rectifier).

Answer: A PN junction allows significant current flow only in forward bias (low resistance) and blocks current in reverse bias (high resistance). This one-directional conduction property allows it to convert alternating current (A.C.) to direct current (D.C.), functioning as a rectifier.

Q6. What is the built-in potential of a PN junction?

Answer: The built-in potential (contact potential) is the potential difference established across the depletion region due to the fixed ionic charges. It opposes further diffusion of majority carriers. For silicon, it is approximately 0.7 V, and for germanium, approximately 0.3 V.

Q7. Distinguish between diffusion current and drift current in a PN junction.

Answer: Diffusion current is caused by majority carriers moving from high to low concentration across the junction (electrons from N to P, holes from P to N). Drift current is caused by minority carriers swept across the junction by the

built-in electric field. At equilibrium, these two currents are equal and opposite, giving zero net current.

Q8. What is reverse breakdown in a PN junction?

Answer: Reverse breakdown occurs when the reverse voltage is large enough to cause a sudden large increase in reverse current. It can happen via Zener breakdown (quantum tunnelling in heavily doped, thin depletion region junctions) or avalanche breakdown (high-energy minority carriers collide with atoms, generating new electron-hole pairs).

Q9. How does a PN junction diode work as a half-wave rectifier?

Answer: In a half-wave rectifier, the diode is placed in series with an A.C. source and a load resistor. During the positive half-cycle, the diode is forward biased and current flows. During the negative half-cycle, the diode is reverse biased and blocks current. The output is a pulsating D.C. with only positive half-cycles.

Q10. Describe the I-V characteristics of a PN junction diode.

Answer: In forward bias, negligible current flows until the threshold voltage (~ 0.7 V for Si), after which current increases exponentially. In reverse bias, only a very small reverse saturation current flows until the breakdown voltage is reached, at which point current increases sharply. The characteristic shows the diode's rectifying property clearly.

Characteristics of Diode Under Biasing


When a diode is connected across an electric supply, then it is said to be under biasing. A diode allows current to flow in only one direction, so a diode acts as a perfect insulator for current flowing in one direction and as a perfect conductor for currents flowing through it in the other direction.

1) Forward Biased

The biasing in which the diode allows current to flow is called Forward Biased. When the positive terminal of DC source is connected to P-type and negative terminal is connected to N-type semiconductor of a PN junction, the junction is said to be in forward biased.

Detail: In this circuit, the holes in the P-side, being positively charged particles, are repelled from the positive bias terminal and driven towards the junction. Similarly, the electrons on the N-side are repelled from the negative bias terminal and driven towards the junction.

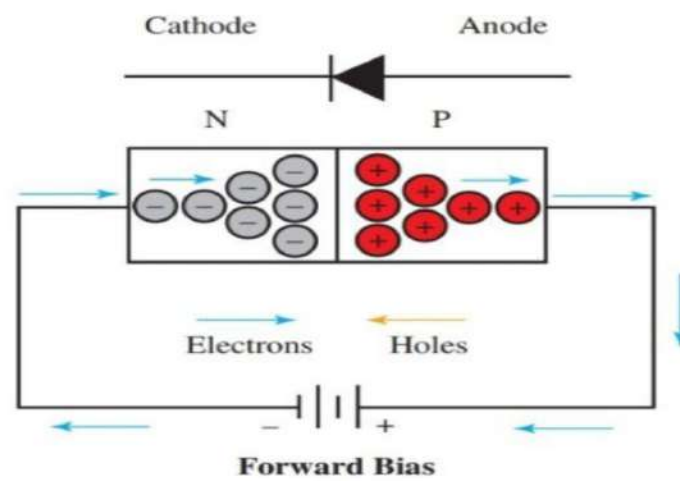The result is that the depletion region is reduced in width and the barrier potential is also reduced. Once the potential barrier is reduced by the forward voltage, a conducting path is established for flow of current. The electrons and holes combine causing the current to pass through the junction. This current is called forward current and it is of the order of a few milliamperes (mA).




2) Reverse Biased

When the negative terminal of DC source is connected to P-type and positive terminal is connected to N-type semiconductor of PN junction, the junction is said to be in reverse biased. The biasing in which current is resisted is called reverse bias. In a reverse bias, diode current is blocked.

Detail: In the reverse biased connection, holes in the N-side are forced to the left while electrons in P-side are forced to the right. This results in an empty zone around the PN junction that is free of charge carriers, creating a wider depletion region. This depletion region acts as an insulator so no current flows through the junction due to majority charge carriers.

Only a small amount of current of the order of a few microamperes (μA) flows due to minority charge carriers.

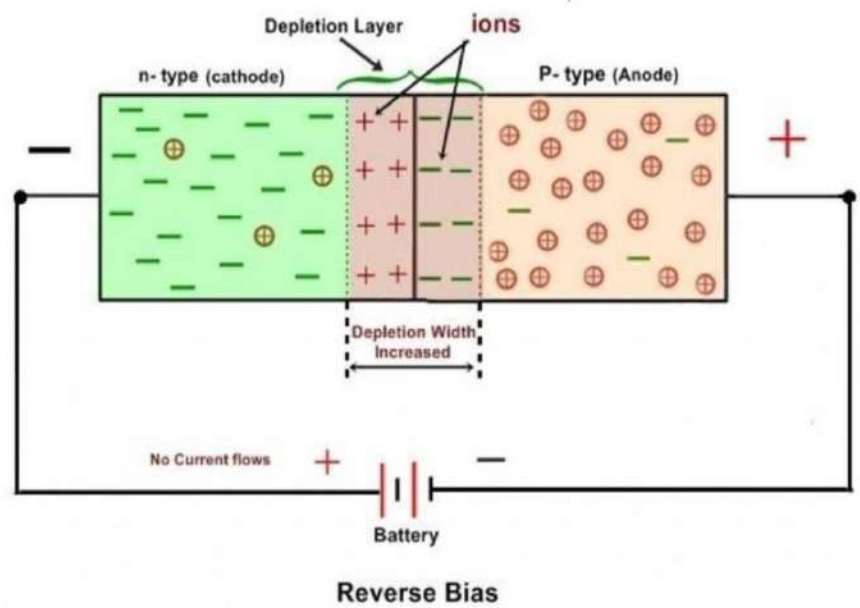The small current is known as reverse or leakage current.




I-V Characteristic Curve

In the current (I) versus voltage (V) graph for a PN junction, it can be seen that in the forward bias region, current and voltage are positive. When the forward voltage is less than V_0 , the forward current is nearly zero so the diode does not conduct. When the forward voltage is equal to V_0 , the diode starts to conduct.

In the reverse bias region, current and voltage are negative. As reverse bias voltage is raised, depletion region width increases and a point comes when the junction breaks down. This results in large flow of current.

Potential barrier: 0.3V for Germanium | 0.7V for Silicon

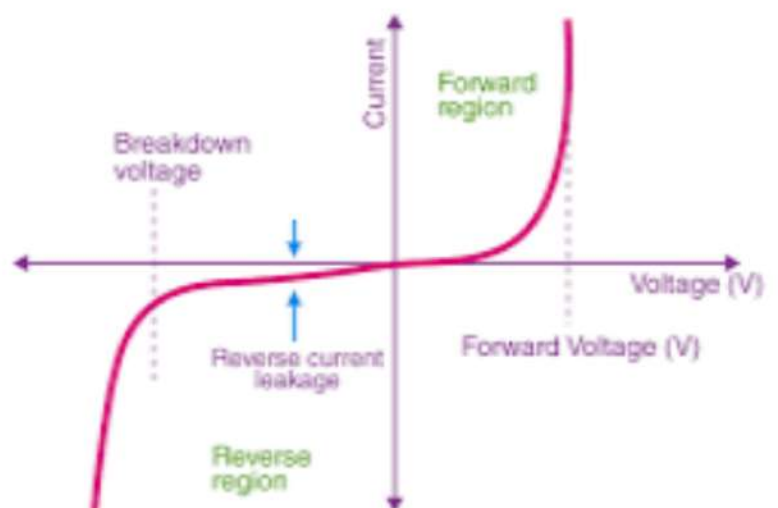

Comparison: P-Type vs N-Type in PN Junction

Property	P-Type Side	N-Type Side
Majority carriers	Holes	Electrons
Fixed ions after diffusion	Negative ions	Positive ions
Direction of electric field	Receives field	Source of field (N → P)
Potential barrier contribution	Lower potential	Higher potential

Note:

Forward bias mein positive terminal P-type se connect hota hai – current flow karta hai, depletion region choti hoti hai. Reverse bias mein negative terminal P-type se connect hota hai – current block hoti hai, depletion region bari hoti hai. Yaad rakho: Forward = current ON, Reverse = current OFF. Sirf minority carriers ki wajah se thori si leakage current aati hai.



Note:

PN Junction mein P-type aur N-type ko milaya jata hai. Junction par electrons aur holes milte hain aur recombine ho jate hain – yeh depletion region banata hai. Yeh region current flow rokta hai. Si ka barrier 0.7V aur Ge ka 0.3V hota hai. Yad rakho: PN junction sirf ek taraf current flow karne deta hai.

PKMZ:

Reverse bias

Ab dekhp hamare America wale rishtedar Hain voh chahte Hain ki Ham America Na Aaye voh hamen rokane ki puri koshish karenge lekin ab agar voh Pakistan a gaye hain to Pakistan ke sare log America chale jaenge America bhag jaenge jiski wajah se America tabarbao barbad ho jaega ...



MCQs

1. The I-V characteristic of a diode in forward bias shows:

- A) Linear increase of current with voltage
- B) Exponential increase of current after threshold voltage
- C) Constant current regardless of voltage
- D) Decreasing current with increasing voltage

Answer: B) Exponential increase of current after threshold voltage

Explanation: The forward I-V characteristic is described by the Shockley diode equation: $I = I_0(e^{(qV/kT)} - 1)$. Below the threshold voltage (~ 0.7 V for Si), negligible current flows. Once the threshold is exceeded, the current rises exponentially with voltage, giving the characteristic sharp 'knee' shape on the I-V graph.

2. The threshold (cut-in) voltage for a silicon diode is approximately:

- A) 0.1 V
- B) 0.3 V
- C) 0.7 V
- D) 1.5 V

Answer: C) 0.7 V

Explanation: The threshold voltage of a silicon diode is approximately 0.7 V. This is the forward voltage at which the depletion region potential barrier is overcome and significant current begins to flow. Germanium diodes have a lower threshold of ~ 0.3 V due to their smaller band gap.

3. The threshold (cut-in) voltage for a germanium diode is approximately:

- A) 0.7 V

- B) 1.1 V
- C) 0.3 V
- D) 0.1 V

Answer: C) 0.3 V

Explanation: Germanium has a smaller band gap (0.67 eV) than silicon (1.12 eV), resulting in a lower built-in potential and hence a lower threshold voltage of ~ 0.3 V. This makes germanium diodes more sensitive to small forward voltages but also more susceptible to leakage current at higher temperatures.

4. In the reverse bias region of an ideal diode I-V curve, the current is:

- A) Large and proportional to voltage
- B) Zero
- C) Equal to the forward current
- D) Exponentially increasing

Answer: B) Zero

Explanation: An ideal diode is a perfect one-way conductor: it passes current freely in forward bias and allows absolutely zero current in reverse bias. In reality, a very small reverse saturation current I_0 flows due to minority carriers, but the ideal model assumes this to be exactly zero for simplification.

5. The reverse saturation current I_0 in a real diode:

- A) Is very large
- B) Increases with temperature
- C) Decreases with temperature
- D) Is independent of temperature

Answer: B) Increases with temperature

Explanation: The reverse saturation current I_0 is

determined by thermally generated minority carriers. Since more minority carriers are generated at higher temperatures, I_o increases significantly with temperature – approximately doubling for every 10°C rise.

6. The dynamic (AC) resistance of a diode in forward bias is:

- A) Very high (megaohms)
- B) Very low (a few ohms)
- C) Infinite
- D) Equal to the static resistance

Answer: B) Very low (a few ohms)

Explanation: The dynamic resistance (r_d) is defined as $r_d = dV/dI$ at a given operating point. In forward bias (above threshold), the current increases steeply with a small change in voltage, giving a very low dynamic resistance (typically a few ohms).

7. The static (DC) resistance of a diode is defined as:

- A) dV/dI at the operating point
- B) V/I at the operating point
- C) The reciprocal of transconductance
- D) The slope of the I-V curve

Answer: B) V/I at the operating point

Explanation: Static (DC) resistance is simply Ohm's law applied to the operating point: $R = V/I$. It is NOT the slope of the curve (that would be dynamic resistance). Because the I-V curve is non-linear, static resistance varies with the operating point.

8. In the forward bias I-V characteristic, the 'knee' of the curve represents:

- A) The breakdown voltage
- B) The reverse saturation current

C) The threshold voltage where current starts to increase sharply

D) The maximum rated current

Answer: C) The threshold voltage where current starts to increase sharply

Explanation: The 'knee' of the forward I-V curve is the point where the curve bends sharply upward – the threshold voltage. Below the knee, the diode resistance is high and very little current flows. Above the knee, resistance drops dramatically and current increases exponentially.

9. When a diode is forward biased beyond the threshold voltage, its resistance:

A) Increases rapidly

B) Remains constant

C) Decreases to a very low value

D) Becomes infinite

Answer: C) Decreases to a very low value

Explanation: Above the threshold voltage, the depletion region narrows significantly and the built-in barrier is largely overcome. Majority carriers flow freely across the junction. The diode resistance drops to a very low value (typically a few ohms), limited mainly by the bulk resistance of the semiconductor material.

10. In reverse bias, the width of the depletion region:

A) Decreases with increasing reverse voltage

B) Increases with increasing reverse voltage

C) Remains constant

D) First increases then decreases

Answer: B) Increases with increasing reverse voltage

Explanation: As reverse bias voltage increases, majority

carriers are pulled further from the junction, removing more carriers from the junction region and widening the depletion zone. The width W of the depletion region is proportional to $\sqrt{V_{bi} + V_R}$, where V_R is the reverse voltage.

11. The Shockley diode equation is:

A) $I = I_0(e^{(qV/nkT)} + 1)$

B) $I = I_0(e^{(qV/nkT)} - 1)$

C) $I = V/R$

D) $I = I_0 \cdot V$

Answer: B) $I = I_0(e^{(qV/nkT)} - 1)$

Explanation: The Shockley equation $I = I_0(e^{(qV/nkT)} - 1)$ describes the I-V relationship of a PN junction diode, where I_0 is reverse saturation current, q is electron charge, V is applied voltage, n is the ideality factor (1-2), k is Boltzmann's constant, and T is absolute temperature.

12. The ideality factor 'n' in the diode equation is typically:

A) 0

B) Between 1 and 2

C) Greater than 10

D) Negative

Answer: B) Between 1 and 2

Explanation: The ideality factor n accounts for recombination in the depletion region. For ideal diodes with only diffusion current, $n = 1$. When recombination in the depletion region is significant, n approaches 2. Real silicon diodes typically have n between 1 and 2.

13. The thermal voltage V_T at room temperature (300 K) is approximately:

A) 0.7 V

- B) 1.12 V
- C) 26 mV
- D) 100 mV

Answer: C) 26 mV

Explanation: The thermal voltage $V_T = kT/q$, where $k = 1.38 \times 10^{-23}$ J/K, $T = 300$ K, and $q = 1.6 \times 10^{-19}$ C. Calculating:
 $V_T = (1.38 \times 10^{-23} \times 300) / (1.6 \times 10^{-19}) \approx 0.026$ V = 26 mV.

14. At large reverse bias (before breakdown), the diode current is approximately:

- A) Zero
- B) Equal to I_0 (reverse saturation current)
- C) Equal to forward current
- D) Infinitely large

Answer: B) Equal to I_0 (reverse saturation current)

Explanation: At large reverse bias, the Shockley equation gives $I \approx I_0(0 - 1) = -I_0$. The current saturates at $-I_0$ (reverse saturation current). Increasing the reverse voltage beyond a few times V_T doesn't significantly increase the current until breakdown.

15. The forward voltage drop across a conducting silicon diode is approximately:

- A) 0 V
- B) 0.3 V
- C) 0.7 V
- D) 5 V

Answer: C) 0.7 V

Explanation: When a silicon diode is forward biased and conducting current, the voltage across it is approximately constant at 0.7 V. In circuit analysis, a conducting silicon diode is often modelled as a 0.7 V battery in series with a

small resistance. For germanium, $V_F \approx 0.3 \text{ V}$.

16. In the I-V characteristic, reverse breakdown appears as:

- A) A gradual decrease in current
- B) A sudden sharp increase in reverse current at breakdown voltage
- C) A gradual increase in forward current
- D) No change in current

Answer: B) A sudden sharp increase in reverse current at breakdown voltage

Explanation: On the reverse bias portion of the I-V curve, the tiny reverse saturation current remains nearly constant until the breakdown voltage is reached. At this point, the curve shows a sharp, nearly vertical increase in reverse current – the breakdown region.

17. Which of the following correctly describes the I-V characteristics in the breakdown region?

- A) Voltage increases while current stays constant
- B) Current increases sharply while voltage remains approximately constant
- C) Both current and voltage decrease
- D) The diode stops conducting

Answer: B) Current increases sharply while voltage remains approximately constant

Explanation: In the breakdown region, large increases in current occur with very little change in voltage. The breakdown voltage V_{BR} remains relatively stable, which is exploited in Zener diodes for voltage regulation.

18. The forward characteristic of a diode shifts with temperature because:

- A) The band gap increases with temperature

- B) The threshold voltage decreases by approximately $2 \text{ mV}/^\circ\text{C}$ as temperature rises
- C) The reverse current decreases
- D) The diode melts

Answer: B) The threshold voltage decreases by approximately $2 \text{ mV}/^\circ\text{C}$ as temperature rises

Explanation: As temperature increases, more thermal energy is available, so electrons can cross the band gap more easily. The threshold voltage decreases by approximately 2 mV per $^\circ\text{C}$ ($-2 \text{ mV}/^\circ\text{C}$ for silicon). At higher temperatures, the I-V curve shifts to the left.

19. The reverse breakdown voltage of a Zener diode:

- A) Is always greater than 100 V
- B) Can be set precisely by controlling doping levels
- C) Cannot be controlled
- D) Is the same for all diodes

Answer: B) Can be set precisely by controlling doping levels

Explanation: Zener diodes are specially manufactured PN junction diodes where the doping concentration is carefully controlled to set the breakdown voltage to a precise, desired value. Higher doping creates thinner depletion regions, leading to lower Zener voltages.

20. A diode is said to be 'ideal' when:

- A) It has a threshold voltage of 0.7 V
- B) It has zero forward resistance and infinite reverse resistance
- C) It conducts in both directions equally
- D) It has a constant current in both bias conditions

Answer: B) It has zero forward resistance and infinite reverse resistance

Explanation: An ideal diode is a theoretical device that acts as a perfect switch: zero resistance (and zero voltage drop) in forward bias, and infinite resistance (zero current) in reverse bias. The ideal model simplifies circuit analysis.

21. The I-V graph of a Zener diode differs from a normal diode because:

- A) It has no forward bias characteristic
- B) It is designed to operate in the reverse breakdown region without damage
- C) It does not follow the Shockley equation
- D) It has no threshold voltage

Answer: B) It is designed to operate in the reverse breakdown region without damage

Explanation: A Zener diode has the same forward I-V characteristic as a normal diode. The key difference is that it is designed and rated to operate continuously in the reverse breakdown region without damage, maintaining a nearly constant voltage (Zener voltage V_Z) across it.

22. In a real diode, the bulk resistance causes:

- A) The I-V curve to be perfectly exponential at all currents
- B) A deviation from the ideal exponential curve at high forward currents
- C) Increased reverse current
- D) Lower threshold voltage

Answer: B) A deviation from the ideal exponential curve at high forward currents

Explanation: At high forward currents, the voltage drop across the bulk semiconductor resistance becomes significant. This causes the I-V curve to deviate from the pure exponential shape and become more linear at high

currents.

23. The junction capacitance of a reverse-biased PN junction:

- A) Decreases as reverse voltage increases
- B) Increases as reverse voltage increases
- C) Is independent of reverse voltage
- D) Is zero in reverse bias

Answer: A) Decreases as reverse voltage increases

Explanation: A reverse-biased PN junction behaves like a parallel-plate capacitor, with the depletion region as the insulating dielectric. As reverse voltage increases, the depletion width increases (plates move apart), reducing the junction capacitance: $C \propto 1/\sqrt{V_{bi} + V_R}$.

24. The diffusion capacitance is associated with:

- A) Reverse-biased diodes only
- B) Forward-biased diodes due to minority carrier charge storage
- C) The bulk resistance of the semiconductor
- D) The thermal voltage

Answer: B) Forward-biased diodes due to minority carrier charge storage

Explanation: In forward bias, minority carriers are injected across the junction and stored in the neutral regions. Any change in forward voltage changes this stored charge, which behaves like a capacitance – the diffusion capacitance. It limits the high-frequency performance of forward-biased diodes.

25. The knee of the reverse characteristic (breakdown) for a Zener diode is:

- A) The same as the forward threshold voltage

- B) Sharp, indicating a well-defined, stable breakdown voltage
- C) Gradual, indicating poor voltage regulation
- D) Not visible on the I-V curve

Answer: B) Sharp, indicating a well-defined, stable breakdown voltage

Explanation: The reverse breakdown characteristic of a Zener diode shows a very sharp, well-defined knee at the Zener voltage V_Z . The voltage across the Zener changes very little with large changes in current – the curve is nearly vertical at V_Z , making Zener diodes effective voltage regulators.

26. Comparing silicon and germanium diodes: which has better high-temperature performance?

- A) Germanium, because its threshold voltage is lower
- B) Silicon, because its larger band gap means lower reverse leakage at high temperatures
- C) Both perform equally
- D) Neither can operate above room temperature

Answer: B) Silicon, because its larger band gap means lower reverse leakage at high temperatures

Explanation: Silicon's larger band gap (1.12 eV vs 0.67 eV) means fewer minority carriers are thermally generated at any given temperature. Germanium diodes become unreliable at temperatures above $\sim 70^\circ\text{C}$ due to excessive leakage, while silicon diodes can operate reliably up to $\sim 150^\circ\text{C}$.

27. The piecewise linear model of a diode represents it as:

- A) An ideal switch only
- B) A battery (V_{th}) in series with a resistance (r_d) and an ideal switch
- C) A pure capacitor

D) A pure inductor

Answer: B) A battery (V_{th}) in series with a resistance (r_d) and an ideal switch

Explanation: The piecewise linear model approximates the diode I-V curve with straight-line segments. In forward bias above threshold: the diode is modelled as a voltage source V_{th} (~ 0.7 V for Si) in series with a small dynamic resistance r_d and an ideal switch. In reverse bias: open circuit.

28. In the forward I-V characteristic of a diode, the x-axis intercept of the linear extrapolation gives:

- A) The breakdown voltage
- B) The threshold (cut-in) voltage
- C) The reverse saturation current
- D) The dynamic resistance

Answer: B) The threshold (cut-in) voltage

Explanation: If the steep linear portion of the forward I-V curve is extrapolated back to the voltage axis (x-axis), the intercept approximates the threshold (cut-in) voltage. For silicon, this is ~ 0.7 V.

29. The I-V characteristic of a diode is measured by:

- A) Applying a fixed voltage and measuring current only at that point
- B) Varying the applied voltage from reverse to forward and plotting the corresponding current
- C) Using only an ohmmeter
- D) Measuring resistance at a single frequency

Answer: B) Varying the applied voltage from reverse to forward and plotting the corresponding current

Explanation: The complete I-V characteristic is obtained by systematically varying the applied voltage across the full

range: starting from large reverse bias, through zero bias, and increasing forward bias. The resulting plot of I vs V constitutes the characteristic curve.

30. At $V = 0$ (zero bias), the current through a PN junction diode is:

- A) Equal to I_0
- B) Maximum forward current
- C) Zero
- D) Equal to reverse breakdown current

Answer: C) Zero

Explanation: At zero bias, the Shockley equation gives $I = I_0(e^0 - 1) = I_0(1 - 1) = 0$. Physically, at equilibrium, diffusion current and drift current exactly cancel each other, resulting in zero net current.

31. The reverse saturation current I_0 is also called:

- A) Threshold current
- B) Leakage current
- C) Zener current
- D) Avalanche current

Answer: B) Leakage current

Explanation: The reverse saturation current I_0 is commonly called leakage current because it represents an unwanted small current that 'leaks' through the diode even when it is reverse biased and should ideally be blocking all current.

32. A conducting silicon diode in a circuit is best modelled as:

- A) A short circuit (wire)
- B) A 0.7 V voltage source
- C) An open circuit
- D) A 1 k Ω resistor

Answer: B) A 0.7 V voltage source

Explanation: A conducting silicon diode maintains approximately 0.7 V across its terminals when forward biased and carrying current. In circuit analysis, this constant voltage drop is best modelled as a 0.7 V voltage source with the positive terminal at the anode.

33. The forward voltage drop across a diode increases or decreases with increasing forward current?

- A) Decreases significantly
- B) Increases slightly
- C) Remains exactly constant at 0.7 V
- D) Drops to zero

Answer: B) Increases slightly

Explanation: While the forward voltage is often approximated as constant at 0.7 V, it does increase slightly with increasing current due to the bulk resistance of the semiconductor. V increases logarithmically with I , typically ranging from about 0.6 V at low currents to 0.8 V at high currents for silicon.

34. The I-V characteristic of a diode is non-linear because:

- A) The diode is made of two different materials
- B) The exponential relationship between current and voltage as described by the Shockley equation
- C) The diode has variable capacitance
- D) Ohm's law applies to diodes

Answer: B) The exponential relationship between current and voltage as described by the Shockley equation

Explanation: The Shockley equation $I = I_0(e^{(qV/nkT)} - 1)$ is exponential, not linear. The non-linearity arises from the Boltzmann distribution of carrier energies and the exponential dependence of carrier injection on applied

voltage.

35. Why is a load line used in diode circuit analysis?

- A) To determine the AC frequency response
- B) To graphically find the operating point (Q-point) by intersecting the load line with the diode I-V curve
- C) To calculate the breakdown voltage
- D) To measure the reverse saturation current

Answer: B) To graphically find the operating point (Q-point) by intersecting the load line with the diode I-V curve

Explanation: A load line is drawn on the I-V characteristic graph, representing the constraints imposed by the external circuit. The intersection of the load line with the diode I-V curve gives the operating point (Q-point), which specifies the actual current and voltage of the diode in the circuit.

36. On the I-V characteristic graph, the slope of the load line equals:

- A) The diode dynamic resistance
- B) $-1/R_{\text{load}}$ (negative reciprocal of load resistance)
- C) The threshold voltage
- D) The reverse saturation current

Answer: B) $-1/R_{\text{load}}$ (negative reciprocal of load resistance)

Explanation: The load line equation is $I = (V_S - V_D)/R$, which rearranges to $I = -(1/R)V_D + V_S/R$. This is a straight line with slope $-1/R$ (negative reciprocal of load resistance). The x-intercept is V_S and the y-intercept is V_S/R .



Q1. Describe the forward bias I-V characteristic of a silicon diode.

Answer: In forward bias, negligible current flows until the threshold voltage of ~ 0.7 V is reached (the 'knee'). Beyond this, the current increases exponentially with voltage as described by the Shockley equation. The curve rises very steeply, meaning even small increases in voltage above 0.7 V produce large increases in current. The forward voltage drop remains approximately 0.7 V during conduction.

Q2. Describe the reverse bias I-V characteristic of a diode.

Answer: In reverse bias, only a very small reverse saturation current I_0 (leakage current, \sim nA for Si) flows, due to minority carriers swept across the junction. This current remains nearly constant regardless of the reverse voltage magnitude. If the reverse voltage exceeds the breakdown voltage, the current increases sharply (breakdown region) while voltage remains approximately constant.

Q3. What is the threshold voltage of a diode and what does it represent physically?

Answer: The threshold voltage (cut-in or knee voltage) is the minimum forward voltage required for significant current to flow — approximately 0.7 V for silicon and 0.3 V for germanium. Physically, it represents the forward voltage needed to overcome the built-in potential barrier of the depletion region, allowing majority carriers to cross the junction freely.

Q4. Define dynamic resistance of a diode and explain how it varies with forward current.

Answer: Dynamic resistance $r_d = dV/dI$, the reciprocal of the slope of the I-V curve at the operating point. It is given by

$r_d = nVT/I_D$. As forward current I_D increases, r_d decreases – a diode conducting more current has lower dynamic resistance. At small currents, r_d is large; at large currents, r_d is very small (a few ohms or less).

Q5. How does temperature affect the forward I-V characteristic of a diode?

Answer: As temperature increases, the threshold voltage decreases by approximately $2 \text{ mV}/^\circ\text{C}$. This means at higher temperatures, the same forward current can flow at a lower forward voltage – the I-V curve shifts to the left. Also, the reverse saturation current I_0 approximately doubles for every 10°C rise, increasing leakage current.

Q6. What is a load line and how is it used to find the operating point of a diode circuit?

Answer: A load line is a straight line drawn on the diode I-V characteristic representing the external circuit constraints ($V_S = V_D + I \cdot R$). It has slope $-1/R$, x-intercept V_S , and y-intercept V_S/R . The intersection of the load line with the diode I-V curve gives the Q-point (operating point), which is the actual diode current and voltage in the circuit.

Q7. State the Shockley diode equation and identify each term.

Answer: $I = I_0(e^{(qV/nkT)} - 1)$, where I = diode current, I_0 = reverse saturation current, q = electron charge ($1.6 \times 10^{-19} \text{ C}$), V = applied voltage, n = ideality factor (1-2), k = Boltzmann's constant ($1.38 \times 10^{-23} \text{ J/K}$), T = absolute temperature (K). Positive V gives large forward current; negative V gives $-I_0$ (reverse saturation).

Q8. Compare the I-V characteristics of silicon and germanium diodes.

Answer: Both have qualitatively similar I-V characteristics,

but silicon has a threshold voltage of ~ 0.7 V while germanium has ~ 0.3 V. Silicon has lower reverse leakage current and better high-temperature performance due to its larger band gap. Germanium is more sensitive to small forward voltages and temperature changes.

Q9. What happens to the I-V characteristic at reverse breakdown?

Answer: At the breakdown voltage (V_{BR}), the reverse current increases sharply (nearly vertically on the I-V graph) while the voltage remains approximately constant. This is due to either avalanche multiplication (high-energy carrier impact ionization) or Zener tunnelling. In Zener diodes, this region is exploited for voltage regulation.

Q10. What is the difference between static resistance and dynamic resistance of a diode?

Answer: Static (DC) resistance = V/I at a given operating point – the ratio of total voltage to total current. Dynamic (AC) resistance = dV/dI – the ratio of a small change in voltage to the resulting small change in current, i.e., the slope of the I-V curve at that point. They differ because the I-V relationship is non-linear. Dynamic resistance is more relevant for AC signals

Light Emitting Diode (LED)

Light emitting Diode is a special type of diode that gives off light when current passes through it in the forward direction. Most diodes are made from gallium arsenide phosphide (GaAsP) and gallium Phosphide (GaP). A light-emitting diode (LED) is a type of semiconductor device that converts electrical energy into light energy. When a current passes through an LED, it emits light due to the recombination of electrons and holes in the semiconductor material.

Working of LED:

In LED, when the LED is forward biased, the potential barrier is lowered. The electrons from n-region cross this barrier and enter the p-region. These electrons fall into holes; they fall from higher energy level to lower energy level. In this process, they emit energy. This phenomenon is known as electroluminescence. LED is enclosed with a transparent cover to view emitted light.

[Diagram: LED structure showing p-type region, active region, n-type region, and emitted light – add manually]


Applications of LED:

- 1). Decorative lamps – due to their energy efficiency and color versatility.
- 2). Optical communication – for transmitting data as light signals.

3). Display devices – for screens and indicators.

4). Resistance circuits – connected in series with a resistor for current limiting.

A Light-Emitting Diode (LED)

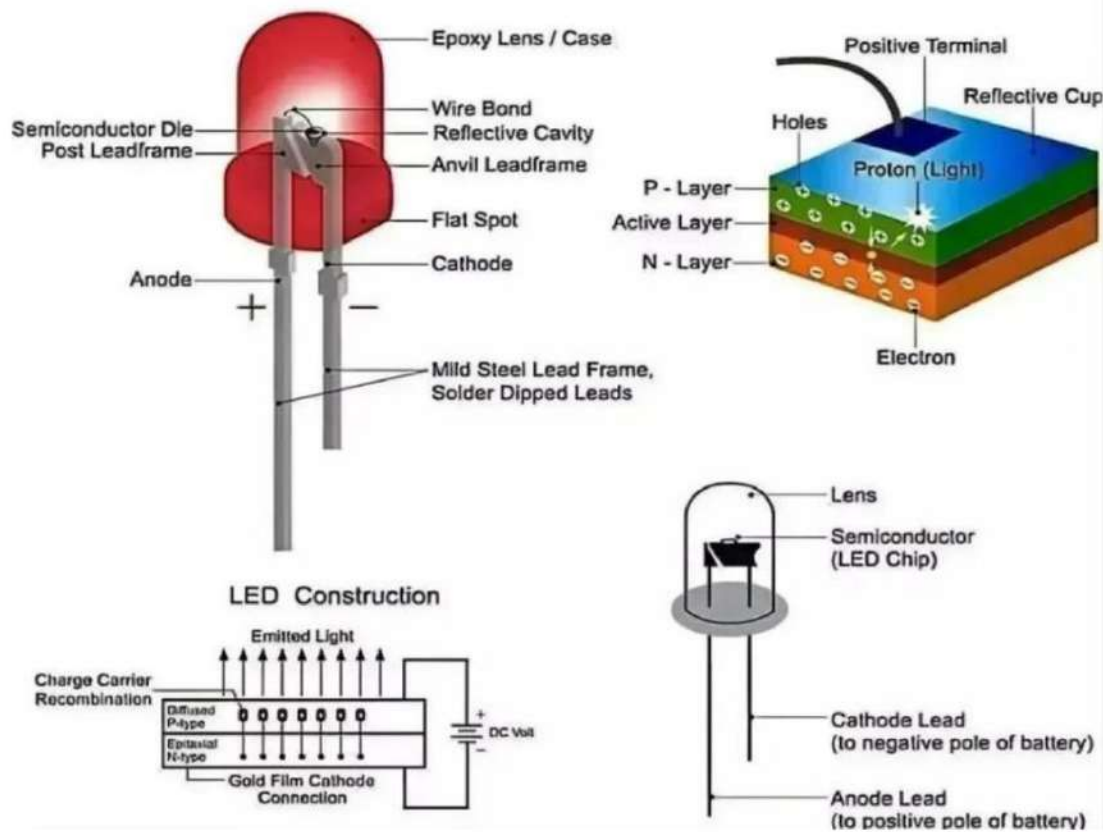

PKMZ

LED ek special diode hai jo forward bias mein light emit karta hai. Electrons n-region se p-region mein jate hain, holes ke saath recombine hote hain aur energy light ke form mein release hoti hai. GaAsP aur GaP se bana hota hai. Uses: decorative lights, screens, optical communication. Simple: current andar, light bahar.

MCQs

1. An LED emits light due to:

- A) Thermionic emission
- B) Recombination of electrons and holes releasing photons
- C) Photoelectric effect
- D) Avalanche breakdown

Answer: B) Recombination of electrons and holes releasing photons

Explanation: In a forward-biased LED, electrons from the N-region cross the junction into the P-region and recombine with holes. In direct band gap semiconductors (like GaAs, GaN, GaP), this recombination releases energy as a photon (light). The wavelength of emitted light is determined by the band gap: $E = hf = hc/\lambda$. This process is called electroluminescence.

2. The colour of light emitted by an LED depends on:

- A) The forward current through it
- B) The reverse voltage applied
- C) The band gap energy of the semiconductor material
- D) The size of the LED

Answer: C) The band gap energy of the semiconductor material

Explanation: The energy of emitted photons equals the band gap energy: $E = hf$, so $\lambda = hc/E_g$. A larger band gap produces higher-frequency light – blue or violet. A smaller band gap produces lower-frequency light – red or infrared. Different semiconductor materials (GaAs, GaN, GaP, InGaN) are used to

produce different colours.

3. LEDs are made from:

- A) Indirect band gap semiconductors like silicon
- B) Direct band gap semiconductors like GaAs and GaN
- C) Pure metals
- D) Insulating materials

Answer: B) Direct band gap semiconductors like GaAs and GaN

Explanation: LEDs require direct band gap semiconductors where electrons can recombine with holes and release energy directly as photons without needing phonon assistance. Silicon and germanium have indirect band gaps – electron-hole recombination in them produces heat rather than light, making them unsuitable for LEDs.

4. The forward voltage drop across a typical LED is:

- A) 0.3 V
- B) 0.7 V
- C) 1.5–3.5 V
- D) 12 V

Answer: C) 1.5–3.5 V

Explanation: LEDs have higher forward voltage drops than ordinary silicon diodes because they are made from materials with larger band gaps needed to emit visible light. The voltage drop corresponds to the photon energy: $V_F = E_g/q$. For red LEDs (~ 1.8 – 2.1 V), green (~ 2.0 – 2.5 V), blue (~ 2.7 – 3.5 V). The 0.7 V figure applies only to silicon diodes.

5. An LED must be connected in:

- A) Reverse bias to emit light
- B) Forward bias to emit light
- C) Either bias
- D) Zero bias

Answer: B) Forward bias to emit light

Explanation: For an LED to emit light, it must be forward biased so that majority carriers are injected across the junction and can recombine. In reverse bias, carriers are pulled away from the junction and no recombination occurs, so no light is emitted. Excessive reverse voltage can destroy the LED.

6. Which semiconductor material is used for making blue LEDs?

- A) Gallium arsenide (GaAs)
- B) Gallium phosphide (GaP)
- C) Gallium nitride (GaN)
- D) Germanium (Ge)

Answer: C) Gallium nitride (GaN)

Explanation: Gallium nitride (GaN) has a large direct band gap of ~ 3.4 eV, which corresponds to blue light wavelength (~ 450 – 475 nm). The development of high-brightness blue LEDs using GaN won the 2014 Nobel Prize in Physics. Blue LEDs are also essential for white LEDs and Blu-ray technology.

7. Which semiconductor material is commonly used for infrared LEDs?

- A) Gallium nitride (GaN)
- B) Gallium arsenide (GaAs)
- C) Silicon carbide (SiC)
- D) Zinc sulphide (ZnS)

Answer: B) Gallium arsenide (GaAs)

Explanation: Gallium arsenide (GaAs) has a direct band gap of ~ 1.42 eV, corresponding to near-infrared light (~ 870 nm wavelength). GaAs LEDs are widely used in TV remote

controls, optical fibre communication, and other infrared applications.

8. The intensity of light emitted by an LED is approximately proportional to:

- A) The square of the applied voltage
- B) The forward current through it
- C) The reverse voltage
- D) The temperature

Answer: B) The forward current through it

Explanation: The number of photons emitted per unit time is directly proportional to the number of electron-hole recombinations per unit time, which is proportional to the forward current. Doubling the current approximately doubles the light output. This linear relationship is used to control LED brightness through pulse-width modulation (PWM).

9. Compared to conventional incandescent bulbs, LEDs are:

- A) Less efficient and shorter-lasting
- B) More energy-efficient and longer-lasting
- C) Equally efficient but shorter-lasting
- D) More efficient but produce less light

Answer: B) More energy-efficient and longer-lasting

Explanation: LEDs convert electrical energy directly into light with very high efficiency (up to 50–80 lm/W), compared to incandescent bulbs (~15 lm/W). They also have much longer lifespans (typically 25,000–50,000 hours vs ~1,000 hours for incandescent). LEDs produce minimal heat waste compared to incandescent bulbs that release ~90% of energy as heat.

10. White LEDs are typically made by:

- A) Combining red, green, and blue LEDs, or coating a blue LED with phosphor

- B) Using silicon as the semiconductor
- C) Operating in reverse bias
- D) Using a very large band gap insulator

Answer: A) Combining red, green, and blue LEDs, or coating a blue LED with phosphor

Explanation: White light can be produced two ways: (1) Combining red, green, and blue LEDs whose mixed light appears white, or (2) more commonly, using a single blue LED coated with a yellow phosphor (YAG). The phosphor converts some blue light to yellow, and the combination appears white.

11. An LED is a:

- A) Passive component
- B) Active component
- C) Purely resistive device
- D) Capacitive device

Answer: B) Active component

Explanation: An LED is an active component because it converts electrical energy into another form of energy (light). Passive components only dissipate, store, or return energy without converting it to a different form. LEDs require a power source to function and are transducers converting electrical energy to radiant energy.

12. The energy of the photon emitted by an LED is:

- A) Greater than the band gap energy
- B) Equal to the band gap energy
- C) Less than the band gap energy
- D) Independent of the band gap

Answer: B) Equal to the band gap energy

Explanation: When an electron recombines with a hole, it falls from the conduction band to the valence band, losing

energy equal to the band gap energy E_g . This energy is released as a photon with $E_{\text{photon}} = E_g = hf = hc/\lambda$. Hence the photon energy equals the band gap energy, determining the wavelength and colour of emitted light.

13. A red LED typically uses:

- A) GaN
- B) GaAs or GaAsP (gallium arsenide phosphide)
- C) Silicon
- D) Germanium

Answer: B) GaAs or GaAsP (gallium arsenide phosphide)

Explanation: Red LEDs use gallium arsenide phosphide (GaAsP) or aluminium gallium arsenide (AlGaAs) with band gaps corresponding to red light wavelengths (~620–750 nm). By adjusting the phosphorus-to-arsenic ratio in GaAsP, the band gap and emission wavelength can be tuned from infrared through red and orange.

14. Why can't silicon be used to make efficient LEDs?

- A) Silicon's band gap is too large
- B) Silicon has an indirect band gap, so recombination produces heat rather than light
- C) Silicon is too expensive
- D) Silicon conducts too much current

Answer: B) Silicon has an indirect band gap, so recombination produces heat rather than light

Explanation: Silicon has an indirect band gap, meaning the conduction band minimum and valence band maximum are at different crystal momentum values. Electron-hole recombination requires a simultaneous phonon interaction to conserve momentum, making direct photon emission highly unlikely. The energy is released as heat instead.

15. LEDs in 7-segment displays are used to:

- A) Measure light intensity
- B) Display numerical digits by selectively illuminating segments
- C) Generate infrared signals
- D) Amplify electrical signals

Answer: B) Display numerical digits by selectively illuminating segments

Explanation: A 7-segment display consists of seven LED segments arranged in the shape of the digit 8. By forward biasing specific combinations of segments, any digit (0-9) and some letters can be displayed. They are widely used in digital clocks, calculators, and measuring instruments.

16. The maximum reverse voltage an LED can withstand is typically:

- A) Very high (>100 V)
- B) Very low (5 V or less)
- C) The same as for silicon diodes
- D) Equal to the forward voltage

Answer: B) Very low (5 V or less)

Explanation: LEDs have very low reverse breakdown voltages, typically only 5 V or less. This is because they are optimized for light emission (forward operation) rather than reverse voltage blocking. In AC circuits, a protective diode is often connected in reverse parallel with the LED to protect it from reverse voltage.

17. The efficiency of an LED is measured by its:

- A) Current gain
- B) Quantum efficiency (photons emitted per electron injected)

C) Voltage amplification

D) Thermal resistance

Answer: B) Quantum efficiency (photons emitted per electron injected)

Explanation: LED efficiency is characterized by quantum efficiency – the ratio of photons emitted to electron-hole pairs that recombine. Internal quantum efficiency (IQE) measures recombinations that produce photons vs those that produce heat. External quantum efficiency (EQE) also accounts for photons that actually escape the device.

18. LEDs are used in optical fibre communications because:

A) They emit X-rays for long-distance transmission

B) They can be modulated at high frequencies and emit infrared light compatible with fibre optics

C) They emit sound waves

D) They operate at very high voltages

Answer: B) They can be modulated at high frequencies and emit infrared light compatible with fibre optics

Explanation: LEDs are used as light sources in optical fibre communication because: (1) they emit infrared light at wavelengths where optical fibres have low attenuation; (2) they can be switched on and off at very high frequencies for high-speed data transmission; (3) they are compact and reliable.

19. When an LED is operated at excessively high current:

A) It emits more efficiently

B) It can overheat and be permanently damaged

C) Its colour changes to blue

D) It starts emitting UV light

Answer: B) It can overheat and be permanently damaged

Explanation: Excessive current causes excessive heat generation in the LED junction. This can degrade the semiconductor material, cause bond wire failure, or melt the encapsulant. LEDs must be operated within their rated current (typically 10–30 mA for small LEDs) using a current-limiting resistor.

20. A series resistor is connected with an LED in order to:

- A) Increase the brightness
- B) Limit the current to a safe operating level
- C) Provide reverse bias protection
- D) Increase the voltage across the LED

Answer: B) Limit the current to a safe operating level

Explanation: Since an LED is a low-resistance device in forward bias, without current limiting the current would rise to dangerous levels. A series resistor $R = (V_{\text{supply}} - V_{\text{LED}}) / I_{\text{desired}}$ limits the current to the desired safe operating value. Without it, the LED would draw excessive current and burn out immediately.

21. LEDs emit:

- A) Coherent light (laser light)
- B) Incoherent (spontaneous) light
- C) White light only
- D) X-rays

Answer: B) Incoherent (spontaneous) light

Explanation: Standard LEDs emit incoherent light through spontaneous emission — individual electron-hole recombinations emit photons at random phases and slightly different directions and frequencies. This is unlike laser diodes, which emit coherent light through stimulated emission where photons are in phase and highly directional.

22. Which of the following is an advantage of LEDs over incandescent bulbs?

- A) LEDs produce more heat
- B) LEDs have a shorter lifespan
- C) LEDs consume less power for the same light output
- D) LEDs are cheaper to manufacture

Answer: C) LEDs consume less power for the same light output

Explanation: LEDs are far more energy-efficient than incandescent bulbs. An incandescent bulb converts only about 5-10% of electrical energy into visible light, with ~90% wasted as heat. A high-quality LED can convert 40-60% or more of electrical energy into light, using 75-80% less energy for the same luminous output.

23. The principle of operation of an LED involves:

- A) Photoelectric effect
- B) Electroluminescence
- C) Thermoluminescence
- D) Bioluminescence

Answer: B) Electroluminescence

Explanation: Electroluminescence is the emission of light in response to the passage of an electric current. In an LED, the electric current drives electron-hole recombination at the forward-biased PN junction, releasing photon energy. This is distinct from thermoluminescence (heat), photoluminescence (absorbed photons), and bioluminescence (chemical reactions).

24. Organic LEDs (OLEDs) differ from conventional LEDs in that:

- A) They use inorganic semiconductors

B) They use organic (carbon-based) compounds as the emitting material

C) They do not emit visible light

D) They require reverse bias to operate

Answer: B) They use organic (carbon-based) compounds as the emitting material

Explanation: OLEDs use organic molecules or polymers as the electroluminescent material instead of inorganic crystals like GaAs or GaN. They can be made very thin and flexible, emit light across the entire surface, and are used in high-quality smartphone and TV screens.

25. A photodiode and an LED are similar in structure but different in:

A) Their semiconductor material

B) Their mode of operation: LED converts electricity to light, photodiode converts light to electricity

C) Their forward bias behaviour

D) The number of junctions they contain

Answer: B) Their mode of operation: LED converts electricity to light, photodiode converts light to electricity

Explanation: Both devices are PN junction diodes. However, they operate in opposite modes: an LED (forward biased) converts electrical energy into light through electroluminescence. A photodiode (reverse biased) converts light energy into electrical current. They are essentially reverse processes of each other.

26. The wavelength of light emitted by an LED can be calculated using:

A) $\lambda = hf$

B) $\lambda = hc/E_g$

C) $\lambda = qV/c$

D) $\lambda = E_g \times c$

Answer: B) $\lambda = hc/E_g$

Explanation: The emitted photon has energy equal to the band gap: $E_g = hf = hc/\lambda$. Rearranging: $\lambda = hc/E_g$, where $h = 6.63 \times 10^{-34} \text{ J}\cdot\text{s}$, $c = 3 \times 10^8 \text{ m/s}$, and E_g is the band gap in joules. For GaAs with $E_g = 1.42 \text{ eV}$: $\lambda = \text{approx } 873 \text{ nm}$ (infrared).

27. What limits the maximum operating frequency of an LED?

A) The band gap energy

B) The carrier lifetime – how quickly injected minority carriers recombine

C) The supply voltage

D) The size of the LED package

Answer: B) The carrier lifetime – how quickly injected minority carriers recombine

Explanation: The maximum modulation frequency of an LED is limited by the minority carrier lifetime. The LED cannot be switched faster than the carriers can recombine: $f_{\text{max}} = 1/(2\pi \cdot \tau)$. For standard LEDs, τ is on the order of nanoseconds, giving maximum frequencies of tens to hundreds of MHz.

28. LEDs used in TV remote controls emit:

A) Visible red light

B) Visible blue light

C) Infrared radiation

D) Ultraviolet radiation

Answer: C) Infrared radiation

Explanation: TV remote controls use infrared (IR) LEDs, typically made from GaAs or AlGaAs, emitting at wavelengths

around 850–950 nm – invisible to the human eye. The remote control encodes commands as pulses of IR light, which the TV's IR receiver detects.

29. The forward current rating of a typical small signal LED is approximately:

- A) 1 A
- B) 100 mA
- C) 10–30 mA
- D) 1 kA

Answer: C) 10–30 mA

Explanation: Standard small signal LEDs are rated for continuous forward currents of typically 10–30 mA. Exceeding this rating causes excessive heating and permanently damages the device. High-power LEDs can handle much higher currents but require heatsinking.

30. Green LEDs are typically made from:

- A) Pure silicon
- B) Gallium nitride (GaN) or indium gallium nitride (InGaN)
- C) Germanium
- D) Silicon carbide only

Answer: B) Gallium nitride (GaN) or indium gallium nitride (InGaN)

Explanation: Modern high-brightness green LEDs use indium gallium nitride (InGaN) or gallium nitride (GaN) with band gaps tuned to emit at ~520–560 nm (green wavelength). The indium content in InGaN adjusts the band gap – more indium gives a smaller gap and longer wavelength.

31. When designing an LED circuit with a 5 V supply and an LED with $V_F = 2$ V and $I_F = 20$ mA, the series resistor value should be:

- A) 250 ohm
- B) 100 ohm
- C) 150 ohm
- D) 350 ohm

Answer: C) 150 ohm

Explanation: Using Kirchoff's voltage law: $V_R = V_{\text{supply}} - V_{\text{LED}} = 5 - 2 = 3 \text{ V}$. The series resistance $R = V_R / I_F = 3 \text{ V} / 0.020 \text{ A} = 150 \text{ ohm}$. This resistor limits the current to 20 mA, protecting the LED from excessive current.

32. The colour of light emitted by an LED cannot be changed by:

- A) Changing the semiconductor material
- B) Changing the forward current significantly
- C) Changing the doping levels
- D) Using a different compound semiconductor

Answer: B) Changing the forward current significantly

Explanation: The colour (wavelength) of LED light is determined almost entirely by the band gap energy of the semiconductor material. This is a fixed material property. While the brightness changes with current, the colour changes only very slightly. To change colour, you must use a different semiconductor material.

SRQs

Q1. Explain the principle of operation of an LED.

Answer: An LED is a forward-biased PN junction made from a direct band gap semiconductor. When forward biased, electrons from the N-region cross the junction into the P-region and recombine with holes. The energy released during recombination equals the band gap energy and is emitted as a

photon of light. The wavelength is $\lambda = hc/E_g$. This process is electroluminescence.

Q2. Why must LEDs be made from direct band gap semiconductors?

Answer: In direct band gap semiconductors (e.g., GaAs, GaN), the conduction band minimum and valence band maximum are at the same crystal momentum. Electron-hole recombination can occur with direct photon emission. In indirect band gap semiconductors (e.g., Si, Ge), momentum conservation requires phonon participation, making photon emission unlikely – energy is released as heat instead.

Q3. How does the band gap of an LED material determine the colour of emitted light?

Answer: The energy of emitted photons equals the band gap: $E_{\text{photon}} = E_g = hf = hc/\lambda$. A larger band gap produces shorter wavelength (higher energy) light – blue/violet. A smaller band gap produces longer wavelength (lower energy) light – red/infrared. Different materials are chosen to achieve specific colours: GaN for blue, InGaN for green, GaAsP for red.

Q4. State three advantages of LEDs over conventional incandescent bulbs.

Answer: (1) Energy efficiency – LEDs convert much more electrical energy to light (~40-60%) vs incandescent bulbs (~5-10%), using 75-80% less power. (2) Longer lifespan – LEDs last 25,000-50,000 hours vs ~1,000 hours for incandescent. (3) Durability – LEDs are solid-state devices with no filament, making them more robust and resistant to vibration and shock.

Q5. What is the purpose of the series resistor in an LED

circuit?

Answer: The series resistor limits the forward current through the LED to a safe operating level. Without it, the small forward resistance of the LED would allow excessive current, causing overheating and permanent damage. The resistor value is calculated as $R = (V_{\text{supply}} - V_{\text{LED}}) / I_{\text{desired}}$, ensuring the LED operates at its rated current.

Q6. How do you calculate the wavelength of light emitted by an LED if the band gap energy is known?

Answer: Using $E_g = hf = hc/\lambda$, rearrange to $\lambda = hc/E_g$. Substitute $h = 6.63 \times 10^{-34} \text{ J}\cdot\text{s}$, $c = 3 \times 10^8 \text{ m/s}$, and convert E_g from eV to joules (multiply by 1.6×10^{-19}). For example, GaN with $E_g = 3.4 \text{ eV}$: $\lambda = (6.63 \times 10^{-34} \times 3 \times 10^8) / (3.4 \times 1.6 \times 10^{-19}) = \text{approx } 365 \text{ nm}$ (near UV/violet).

Q7. Compare LEDs and photodiodes in terms of construction and function.

Answer: Both are PN junction devices using similar semiconductor materials. Structurally, LEDs are optimized with transparent packaging to allow light out, while photodiodes have windows or lenses to allow light in. Functionally, LEDs convert electricity to light (forward biased, electroluminescence), while photodiodes convert light to electricity (reverse biased, photocurrent generation). They perform opposite energy conversions.

Q8. What is electroluminescence?

Answer: Electroluminescence is the emission of light from a material in response to an electric current or strong electric field. In an LED, the forward current drives electron-hole recombinations at the PN junction, and the released energy is emitted as photons. The wavelength (colour) of emitted

light depends on the band gap of the semiconductor material.

Q9. Why do LEDs have a higher forward voltage drop than ordinary silicon diodes?

Answer: The forward voltage drop of a diode corresponds to the band gap energy: $V_F = E_g/q$. LEDs are made from larger band gap materials needed to emit visible light with photon energies of 1.8–3.5 eV. Silicon diodes have a small band gap (~ 1.12 eV, $V_F = 0.7$ V). LED materials like GaN ($E_g = 3.4$ eV) give $V_F = 3.4$ V. Higher photon energy = higher forward voltage.

Q10. Describe two applications of LEDs.

Answer: (1) Display and indicators: LEDs are used in 7-segment displays, traffic lights, indicator lights, and large LED screens for their low power consumption, long life, and available colours. (2) Optical fibre communication: Infrared LEDs (GaAs) serve as light sources in fibre optic systems, being modulated at high frequencies to transmit data over long distances with low signal loss.

Q11. What determines the maximum safe operating current for an LED, and what happens if this is exceeded?

Answer: The maximum safe current is determined by the thermal properties of the LED – specifically, the junction's ability to dissipate heat. Exceeding the rated current (typically 10–30 mA for small LEDs) causes excessive heat at the junction, leading to degraded luminous efficiency, accelerated aging of the semiconductor material, bond wire failure, or complete destruction of the device.

Digital Electronics

Digital electronics is the branch of electronics that deals with signals which have only two states ON(1) and OFF(0). This ON/OFF switching is used to build the digital electronics circuits inside our laptop, computer, GPS system and smart phones. This is mathematically represented by binary digits 0 and 1. These are also known as Boolean variables. Boolean algebra is a formal way of describing logical operations.

Converting Analogue Data to Digital

The Analogue to Digital converter (ADC) enables microprocessors, controlled circuits like Arduinos and Raspberry. Mostly, analogue signals are converted to discrete digital signals. Such circuits are known as Analogue to Digital converters. Whereas Digital to Analogue converter (DAC) allows to convert discrete digital signal to analogue signals.

Unit of Data in Computing

As digital circuits work with binary signal which have only two discrete states, a logic '1' (High) or a logic '0' (Low). Each digit in a binary (0 or 1) is called a bit, which is an abbreviation of binary digit.

Information:

The temperature of air varies in a continuous fashion during 24 hours of a day. If we plot a graph between temperature and time, we get a continuous curve. This graph shows that temperature varies continuously with time – the air temperature does not go from 75°F to 80°F instantaneously; it takes infinite values in between.

Therefore, we say that temperature is an analogue quantity

PKMZ – Digital Electronics (Physics Kahani Mak Zabani)

Digital electronics sirf 2 states use karta hai: 0 (OFF) aur 1 (ON). Yeh binary system hai. ADC analogue signal ko digital mein convert karta hai, DAC wapas analogue mein. Har ek binary digit ko 'bit' kehte hain.

Computers, phones, GPS – sab digital hain. Simple: 0 = band, 1 = chalu.

MCQs

1. Digital electronics operates using:

- A) Continuously varying (analogue) signals
- B) Only two discrete voltage levels representing 0 and 1
- C) Signals that vary between -12 V and +12 V continuously
- D) Purely mechanical switching systems

Answer: B) Only two discrete voltage levels representing 0 and 1

Explanation: Digital electronics uses binary signals – two discrete voltage levels representing logic '0' (LOW, e.g., 0 V) and logic '1' (HIGH, e.g., 5 V or 3.3 V). All information is encoded, stored, and processed as combinations of these two states. This binary representation makes digital systems highly reliable and noise-resistant.

2. The binary number system uses a base of:

- A) 8
- B) 10
- C) 16
- D) 2

Answer: D) 2

Explanation: The binary number system (base-2) uses only two digits: 0 and 1. Each binary digit is called a 'bit'. Base-8 is octal, base-10 is decimal (everyday counting), and base-16 is hexadecimal. Binary is natural for digital electronics because transistors have two stable states (on/off) that directly represent 1 and 0.

3. In digital electronics, logic '1' (HIGH) typically corresponds to:

- A) 0 V
- B) A negative voltage
- C) A high voltage level (e.g., +5 V or +3.3 V)
- D) An alternating signal

Answer: C) A high voltage level (e.g., +5 V or +3.3 V)

Explanation: In positive logic convention, logic '1' (HIGH) corresponds to the higher of the two voltage levels – typically +5 V in older TTL logic or +3.3 V in modern CMOS. Logic '0' (LOW) corresponds to 0 V (ground). The exact voltages depend on the logic family (TTL, CMOS) but only two discrete levels are used.

4. Which of the following correctly converts binary 1010 to decimal?

- A) 5
- B) 8
- C) 10
- D) 12

Answer: C) 10

Explanation: Binary 1010 = $1 \times 2^3 + 0 \times 2^2 + 1 \times 2^1 + 0 \times 2^0 = 8 + 0 + 2 + 0 = 10$. To convert binary to decimal, multiply each bit by its positional value (power of 2, starting from 2^0 at the right) and sum all the values. The bit positions from right to left represent 1, 2, 4, 8, 16, 32 etc.

5. The decimal number 13 in binary is:

- A) 1100
- B) 1101
- C) 1011
- D) 1110

Answer: B) 1101

Explanation: $13 = 8 + 4 + 1 = 2^3 + 2^2 + 2^0$. In binary: bit

3=1, bit 2=1, bit 1=0, bit 0=1 = 1101. Method: repeatedly divide by 2 and record remainders: $13/2=6$ R1, $6/2=3$ R0, $3/2=1$ R1, $1/2=0$ R1. Reading remainders from bottom to top: 1101.

6. A bit is:

- A) A group of 8 binary digits
- B) A single binary digit (0 or 1)
- C) A decimal digit
- D) A hexadecimal digit

Answer: B) A single binary digit (0 or 1)

Explanation: A 'bit' (Binary digIT) is the fundamental unit of digital information – a single binary digit that can take the value 0 or 1. A group of 4 bits is a nibble. A group of 8 bits is a byte. Modern computers work with 64-bit words (64 bits processed simultaneously).

7. A byte consists of:

- A) 4 bits
- B) 8 bits
- C) 16 bits
- D) 2 bits

Answer: B) 8 bits

Explanation: A byte consists of 8 bits. One byte can represent $2^8 = 256$ different values (0 to 255 in decimal). Bytes are the standard unit for measuring data storage. 1 kilobyte (KB) = 1024 bytes, 1 megabyte (MB) = 1024 KB, 1 gigabyte (GB) = 1024 MB.

8. Which of the following correctly converts decimal 7 to binary?

- A) 100
- B) 110

C) 111

D) 011

Answer: C) 111

Explanation: $7 = 4 + 2 + 1 = 2^2 + 2^1 + 2^0 = 111$ in binary. All three bits are 1 because 7 is one less than 8 (2^3).

Alternatively: $7/2=3$ R1, $3/2=1$ R1, $1/2=0$ R1. Reading remainders from bottom: 111.

9. What is the maximum decimal value that can be represented by 4 binary bits?

A) 8

B) 15

C) 16

D) 31

Answer: B) 15

Explanation: With 4 bits, the maximum value is when all bits are 1: $1111 = 8+4+2+1 = 15$. Generally, n bits can represent values from 0 to $2^n - 1$. For 4 bits: $2^4 - 1 = 15$. The total number of distinct values representable by 4 bits is $2^4 = 16$ (values 0 through 15).

10. The hexadecimal number system uses base:

A) 2

B) 8

C) 10

D) 16

Answer: D) 16

Explanation: Hexadecimal (hex) is base-16, using 16 symbols: 0-9 and A-F (where A=10, B=11, C=12, D=13, E=14, F=15). One hex digit represents exactly 4 binary bits (a nibble), making hex a compact way to represent binary: an 8-bit byte = 2 hex digits. Hex is widely used in computing for memory addresses

and colour codes.

11. In Boolean algebra, the expression $A \cdot B$ (A AND B) equals 1 only when:

- A) $A=0$ and $B=0$
- B) $A=1$ and $B=0$
- C) $A=0$ and $B=1$
- D) $A=1$ and $B=1$

Answer: D) $A=1$ and $B=1$

Explanation: The AND operation gives output 1 only when ALL inputs are 1. For two inputs: $0 \cdot 0 = 0$, $0 \cdot 1 = 0$, $1 \cdot 0 = 0$, $1 \cdot 1 = 1$. This mimics series switches in a circuit – current flows only when both switches are closed. In Boolean algebra, AND is analogous to multiplication: $1 \times 1 = 1$, but $1 \times 0 = 0$ and $0 \times 0 = 0$.

12. In Boolean algebra, $A + B$ (A OR B) equals 0 only when:

- A) $A=1$ and $B=1$
- B) $A=0$ and $B=1$
- C) $A=1$ and $B=0$
- D) $A=0$ and $B=0$

Answer: D) $A=0$ and $B=0$

Explanation: The OR operation gives output 0 only when ALL inputs are 0. For two inputs: $0 + 0 = 0$, $0 + 1 = 1$, $1 + 0 = 1$, $1 + 1 = 1$ (in Boolean, not arithmetic). This mimics parallel switches – current flows when either or both switches are closed. Output is 0 only when all inputs are 0.

13. In Boolean algebra, the complement (NOT) of $A = 0$ is:

- A) 0
- B) 1
- C) 2
- D) Undefined

Answer: B) 1

Explanation: The NOT operation (complement, denoted $A\text{-bar}$ or A') inverts the input: NOT 0 = 1, NOT 1 = 0. It represents logical negation. The double complement gives back the original: NOT(NOT A) = A. In digital circuits, NOT is implemented by an inverter gate.

14. Digital systems are preferred over analogue systems because:

- A) They use more power
- B) They are less accurate
- C) They are more noise-immune and data can be perfectly reproduced
- D) They use more components

Answer: C) They are more noise-immune and data can be perfectly reproduced

Explanation: Digital signals use two discrete levels, making them highly immune to noise. Small noise disturbances do not change a '1' to a '0' as long as the noise is less than the noise margin. Analogue signals can accumulate noise at every stage. Digital data can be stored, copied, and transmitted perfectly, unlike analogue signals which degrade with each copy.

15. The term 'logic level' in digital electronics refers to:

- A) The mathematical complexity of a circuit
- B) The discrete voltage level representing a binary 0 or 1
- C) The power consumption of a gate
- D) The number of gates in a circuit

Answer: B) The discrete voltage level representing a binary 0 or 1

Explanation: A logic level is a specific voltage range corresponding to a binary digit. In TTL logic: LOW (logic 0) = 0

to 0.8 V, HIGH (logic 1) = 2 V to 5 V. Voltages between these ranges are undefined/noise regions. Different logic families (CMOS, TTL, ECL) have different voltage specifications.

16. Boolean algebra was developed by:

- A) Isaac Newton
- B) Albert Einstein
- C) George Boole
- D) Alan Turing

Answer: C) George Boole

Explanation: Boolean algebra was developed by English mathematician George Boole (1815–1864). He created an algebraic system for logical operations using 0 and 1. Claude Shannon later demonstrated that Boolean algebra could be applied to describe electronic switching circuits, forming the mathematical foundation of digital electronics.

17. Which of the following is a Boolean identity?

- A) $A + 1 = A$
- B) $A \cdot 0 = A$
- C) $A + 0 = A$
- D) $A \cdot 1 = 0$

Answer: C) $A + 0 = A$

Explanation: $A + 0 = A$ is a Boolean identity (OR with 0 leaves the value unchanged – identity law for OR). Other identities: $A \cdot 1 = A$ (identity for AND), $A + 1 = 1$ (domination for OR), $A \cdot 0 = 0$ (domination for AND). These identities are used to simplify Boolean expressions and optimize digital circuits.

18. De Morgan's first theorem states:

- A) $\overline{A + B} = \overline{A} \cdot \overline{B}$
- B) $\overline{A \cdot B} = \overline{A} + \overline{B}$
- C) $A + B = \overline{\overline{A} \cdot \overline{B}}$

D) $AB = A+B$

Answer: B) $\text{NOT}(A \text{ AND } B) = \text{NOT-A OR NOT-B}$

Explanation: De Morgan's first theorem: $\text{NOT}(A \cdot B) = \overline{A} + \overline{B}$. The complement of a product equals the sum of complements. Second theorem: $\text{NOT}(A+B) = \overline{A} \cdot \overline{B}$. The complement of a sum equals the product of complements. These theorems are powerful tools for Boolean algebra simplification and for converting between AND/OR/NOT to NAND/NOR implementations.

19. A truth table is used to:

- A) Show the physical layout of a circuit
- B) List all possible input combinations and corresponding outputs of a logic circuit
- C) Calculate the power consumption of gates
- D) Show the frequency response of a circuit

Answer: B) List all possible input combinations and corresponding outputs of a logic circuit

Explanation: A truth table exhaustively lists every possible combination of input values and the corresponding output(s) of a logic gate or circuit. For n inputs, there are 2^n rows. Truth tables are used to define, analyze, and verify logic functions. They are the fundamental tool for understanding and designing combinational logic circuits.

20. In digital circuits, a transistor is used as:

- A) An amplifier only
- B) A switch (on/off) to represent binary 1 and 0
- C) A voltage regulator
- D) A capacitor

Answer: B) A switch (on/off) to represent binary 1 and 0

Explanation: In digital circuits, transistors operate as

switches, not linear amplifiers. A transistor is either fully ON (saturated, representing logic 1) or fully OFF (cut-off, representing logic 0). Millions of such transistors in integrated circuits form the logic gates and flip-flops that make up processors, memory, and other digital systems.

21. CMOS technology is dominant in modern digital ICs because:

- A) It uses bipolar junction transistors
- B) It has very low static power consumption and high integration density
- C) It operates at higher voltages than TTL
- D) It is less reliable than TTL

Answer: B) It has very low static power consumption and high integration density

Explanation: CMOS (Complementary Metal-Oxide Semiconductor) uses pairs of complementary MOSFETs (PMOS and NMOS). In steady state, one transistor is always off, so no direct path from supply to ground exists – static power consumption is nearly zero. Only during switching is power dissipated. This enables billions of transistors on a chip without excessive heat.

22. The number of possible states of n binary bits is:

- A) n
- B) $2n$
- C) n^2
- D) 2^n

Answer: D) 2^n

Explanation: Each bit can be independently 0 or 1. For n bits, the total number of unique combinations is $2 \times 2 \times \dots \times 2$ (n times) = 2^n . For example: 1 bit = 2 states; 2 bits = 4 states;

8 bits = 256 states; 32 bits = approx 4.3 billion states. This exponential relationship is fundamental to understanding digital storage capacity.

23. Binary addition: 1 + 1 in binary equals:

- A) 2
- B) 11
- C) 10
- D) 0

Answer: C) 10

Explanation: In binary: $1 + 1 = 10$ (binary), NOT 2 (decimal). This is because binary is base-2: when the sum at any bit position reaches 2, it carries 1 to the next position. $1+1=0$ with carry 1, giving 10 in binary (which represents 2 in decimal). Binary addition rules: $0+0=0$, $0+1=1$, $1+0=1$, $1+1=10$.

24. Which logic family has the highest switching speed?

- A) CMOS
- B) TTL (standard)
- C) ECL (Emitter-Coupled Logic)
- D) RTL (Resistor-Transistor Logic)

Answer: C) ECL (Emitter-Coupled Logic)

Explanation: ECL is the fastest logic family because its transistors never enter saturation – they switch between active region states, avoiding the charge storage delay associated with saturation. ECL gate propagation delays can be as low as 0.1–1 ns. The tradeoff is very high power consumption. ECL is used in high-speed applications like supercomputers and communication equipment.

25. Noise margin in digital logic refers to:

- A) The audio noise generated by the circuit
- B) The voltage range within which a logic level is still

correctly recognized

C) The power supply noise

D) The frequency at which a gate stops working

Answer: B) The voltage range within which a logic level is still correctly recognized

Explanation: Noise margin is the maximum noise voltage that can be added to an input signal without causing incorrect logic level interpretation. A larger noise margin means the circuit tolerates more noise. CMOS has larger noise margins than TTL because it swings closer to the supply rails.

26. In a positive logic system, the more positive voltage level represents:

A) Logic 0

B) Logic 1

C) An undefined state

D) An analogue value

Answer: B) Logic 1

Explanation: In positive logic (the standard convention), the higher voltage level is logic 1 (HIGH) and the lower voltage level is logic 0 (LOW). This is the most common convention used in TTL and CMOS families. Negative logic (less common) uses the opposite convention where the lower voltage = logic 1.

27. The process of converting an analogue signal to digital is called:

A) D/A conversion

B) Modulation

C) A/D conversion (ADC)

D) Rectification

Answer: C) A/D conversion (ADC)

Explanation: Analogue-to-Digital Conversion (ADC) samples a continuous analogue signal at regular intervals (sampling) and converts each sample to a binary number representing the amplitude (quantisation). The digital data can then be processed, stored, or transmitted. D/A conversion (DAC) is the reverse process.

28. Combinational logic circuits:

- A) Have memory and depend on past inputs
- B) Produce outputs that depend only on the current inputs
- C) Only implement the AND function
- D) Require a clock signal

Answer: B) Produce outputs that depend only on the current inputs

Explanation: Combinational logic circuits produce outputs that are determined solely by the current input values – there is no memory of past states. Examples include logic gates, multiplexers, decoders, and adders. In contrast, sequential logic circuits have memory (flip-flops) and their outputs depend on both current inputs AND the current state.

29. Sequential logic circuits differ from combinational circuits in that they:

- A) Only use AND and OR gates
- B) Have memory elements and output depends on current inputs and previous state
- C) Are simpler to design
- D) Do not require power

Answer: B) Have memory elements and output depends on current inputs and previous state

Explanation: Sequential circuits incorporate memory

elements (flip-flops, latches, registers) that store the current state. The output depends on BOTH the current input AND the stored state (previous history). Clocked sequential circuits change state on clock edges. Examples include counters, registers, state machines, and memory.

30. A logic gate is a:

- A) Mechanical switch
- B) Basic building block of digital circuits that implements a Boolean function
- C) Type of transistor
- D) Power amplifier

Answer: B) Basic building block of digital circuits that implements a Boolean function

Explanation: A logic gate is an electronic circuit (usually implemented with transistors) that performs a specific Boolean logic operation on one or more binary inputs to produce a single binary output. Logic gates (AND, OR, NOT, NAND, NOR, XOR, XNOR) are the fundamental building blocks from which all digital systems are constructed.

SRQs

Q1. What is digital electronics and how does it differ from analogue electronics?

Answer: Digital electronics uses signals that take only two discrete values (logic 0 and logic 1, represented by low and high voltages). Analogue electronics uses continuously varying signals. Digital systems are more noise-immune, allow perfect data reproduction, and are easier to design and mass-produce in integrated circuits. Analogue systems better represent continuously varying physical quantities.

Q2. Convert binary 11011 to decimal.

Answer: $11011 = 1 \times 2^4 + 1 \times 2^3 + 0 \times 2^2 + 1 \times 2^1 + 1 \times 2^0 = 16 + 8 + 0 + 2 + 1 = 27$. To convert, multiply each bit by its positional value (power of 2 from right starting at 2^0) and sum the results.

Q3. Convert decimal 25 to binary.

Answer: Method (repeated division by 2): $25/2=12$ R1, $12/2=6$ R0, $6/2=3$ R0, $3/2=1$ R1, $1/2=0$ R1. Reading remainders from bottom to top: 11001. Verification: $16+8+0+0+1 = 25$.

Q4. State three advantages of digital systems over analogue systems.

Answer: (1) Noise immunity – digital signals tolerate noise without data corruption, unlike analogue signals that accumulate noise. (2) Perfect reproduction – digital data can be copied and stored without degradation. (3) Programmability – digital systems can be reprogrammed in software without changing hardware, enabling flexible, multifunctional devices like computers and smartphones.

Q5. What is Boolean algebra and why is it important in digital electronics?

Answer: Boolean algebra is a mathematical system using variables that can only take values 0 or 1, with operations AND (\cdot), OR ($+$), and NOT. It was developed by George Boole. It is fundamental to digital electronics because it provides a mathematical framework to describe, analyze, and simplify logic circuits, enabling systematic design of all digital systems.

Q6. State De Morgan's theorems and explain their significance.

Answer: First theorem: $\text{NOT}(A \text{ AND } B) = \text{NOT-}A \text{ OR NOT-}B$.

Second theorem: $\text{NOT}(A \text{ OR } B) = \text{NOT}A \text{ AND } \text{NOT}B$.

Significance: They allow any logic expression using AND/OR/NOT to be rewritten using only NAND or only NOR gates, which are universal gates. They are essential tools for simplifying logic expressions and converting between gate types.

Q7. What is a truth table? Construct the truth table for a 2-input AND gate.

Answer: A truth table lists all possible input combinations and the resulting output(s). For a 2-input AND gate: $A=0, B=0$ gives Output=0; $A=0, B=1$ gives Output=0; $A=1, B=0$ gives Output=0; $A=1, B=1$ gives Output=1. The AND output is 1 only when both inputs are 1; all other combinations give 0.

Q8. Explain why CMOS technology dominates modern digital integrated circuits.

Answer: CMOS uses complementary pairs of PMOS and NMOS transistors. In any static state, one transistor is OFF, creating no direct current path from supply to ground — static power dissipation is nearly zero. Power is only consumed during switching. This allows billions of CMOS transistors to be integrated on a single chip without generating unmanageable heat, enabling modern processors and memory.

Q9. What is a bit and what is a byte? How many values can 8 bits represent?

Answer: A bit (Binary digIT) is a single binary digit, either 0 or 1 — the smallest unit of digital information. A byte is a group of 8 bits. With 8 bits, the number of possible combinations is $2^8 = 256$, representing values from 0 to 255 in decimal. One byte can encode one ASCII character (e.g.,

the letter A = 01000001).

Q10. Distinguish between combinational and sequential logic circuits.

Answer: Combinational circuits: output depends only on current inputs; no memory; examples include logic gates, adders, multiplexers. Sequential circuits: output depends on current inputs AND previous state (memory); they contain flip-flops or latches; require a clock; examples include counters, registers, and state machines. Most practical digital systems use both types together.

Fundamental Logic Gates

Logic gates are the main building blocks of all digital logic circuits. These circuits can act as switches and convert incoming voltage into binary electrical pulses of high(1) and low(0). Digital electronic circuits used to implement binary/ logical operations are known as logic gates.

1) AND Gate

AND Gate is a gate in which its output will be '1' when all the inputs are '1'. In other situations, output of AND gate will be 0.

Boolean Expression: $X = A \cdot B$


The symbol dot (\cdot) represents AND operation.

Example: If a lamp is connected in series with a battery using two switches (A and B) as two inputs, the lamp will glow only if both the switches are closed.


Truth Table – AND Gate:

A	B	$X = A \cdot B$
0	0	0
1	0	0
0	1	0
1	1	1

Circuit symbol:

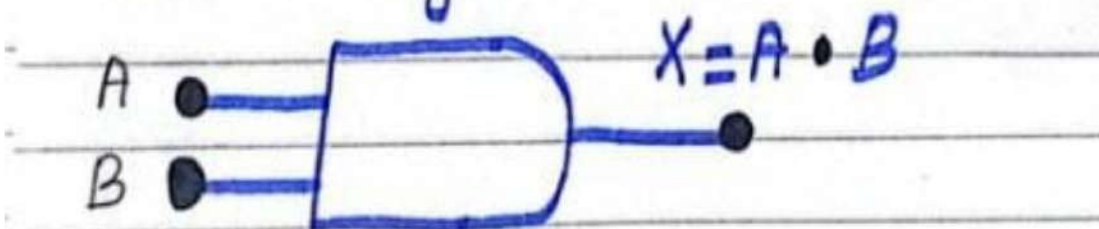

Switch depiction

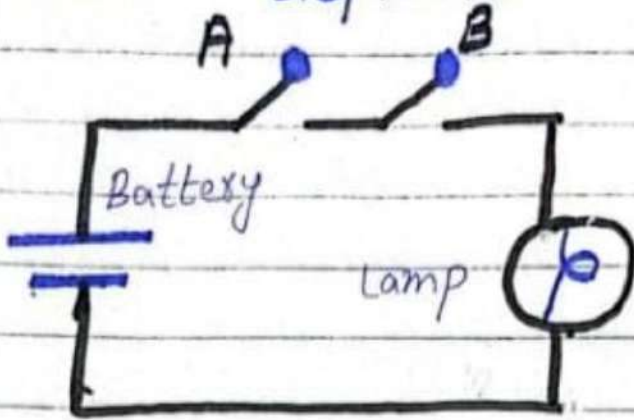

2) OR Gate

OR Gate is a gate in which its output will be 0 only when all the inputs are 0 and for all other situations, output of OR Gate will be 1.

Boolean Expression: $X = A + B$


The symbol plus (+) represents OR operation.

Example: If a lamp is connected in parallel with a battery using two switches, the lamp will glow if at least one of the switches is closed.


Truth Table – OR Gate:

A	B	$X = A + B$
0	0	0
1	0	1
0	1	1
1	1	1

Circuit symbol

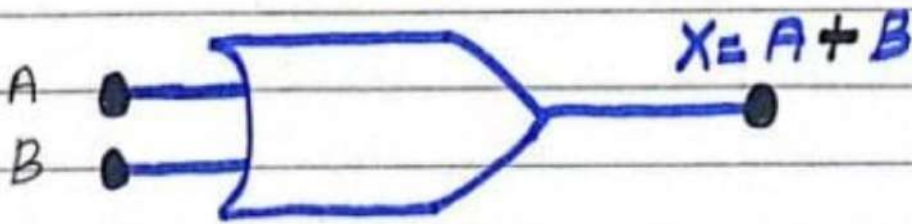

Switch depiction

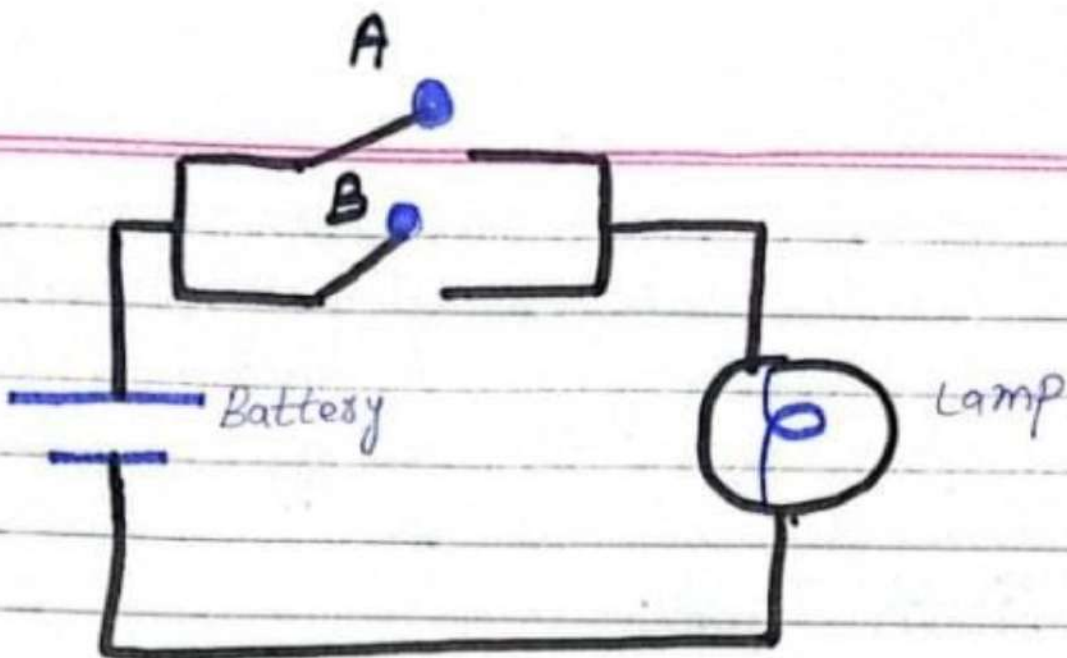

3) NOT Gate

NOT Gate is a gate in which its output will be '0' when its input is 1 and vice versa. NOT operation inverts the state of Boolean variables.

Boolean Expression: $X = \bar{A}$


The line or bar over the symbol represents the NOT operation.

Example: If a lamp is connected in parallel to a battery with switch A as input – when A is open, lamp glows; when A is closed, lamp does not glow.


Truth Table – NOT Gate:

A	$X = \bar{A}$
0	1
1	0

Circuit symbol:

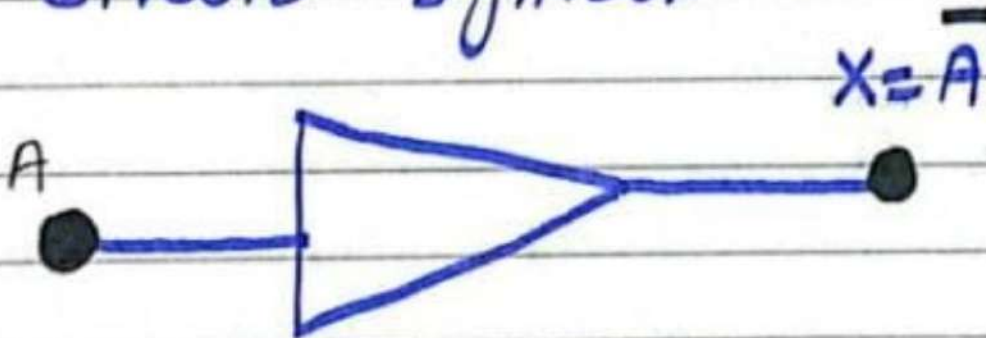

Switch depiction:

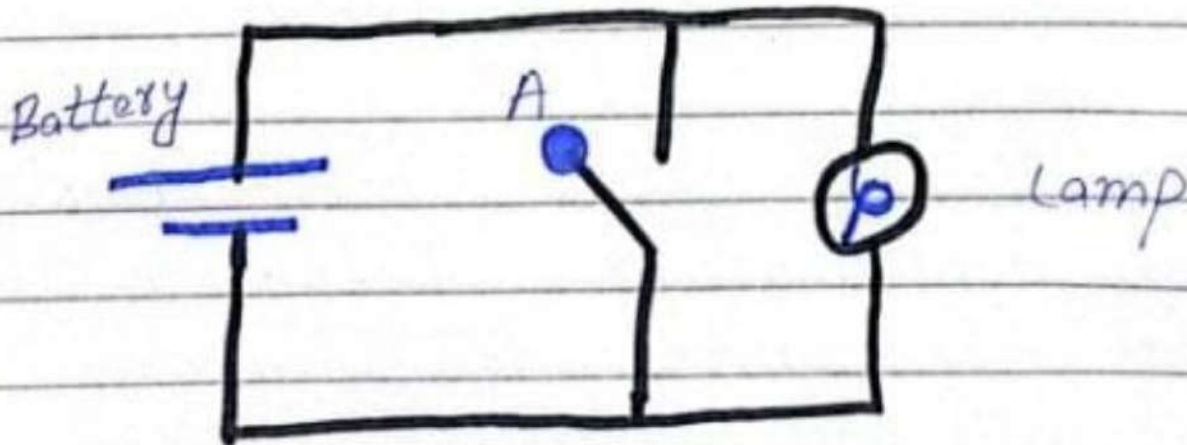

PKMZ - Fundamental Logic Gates

AND gate: dono inputs 1 hon to output 1, warna 0.
OR gate: koï bhi ek input 1 ho to output 1, sirf tab 0 jab dono 0.
NOT gate: input ulta ho jata hai - 1 ko 0, 0 ko 1. Yaad karo: AND = series circuit, OR = parallel circuit, NOT = inverter. Yeh teeno sab logic ka base hain.

Universal Logic Gates

1) NAND Gate

NAND Gate is obtained by coupling a NOT gate with an output terminal of AND Gate. NAND Gate is the reversal of AND Gate.

Boolean Expression: $X = (A \cdot B)' = \overline{A \cdot B}$

It is read as 'X equals A and B not'. NAND and NOR are called universal gates because they can generate all other logic gates using only NAND or only NOR.


Truth Table – NAND Gate:

Switch (input) AND			Lamp (output)
A	B	$A \cdot B$	$X = \overline{A \cdot B}$
1	0	0	1
0	1	0	1
0	0	0	1
1	1	1	0

Description:



Circuit Symbol

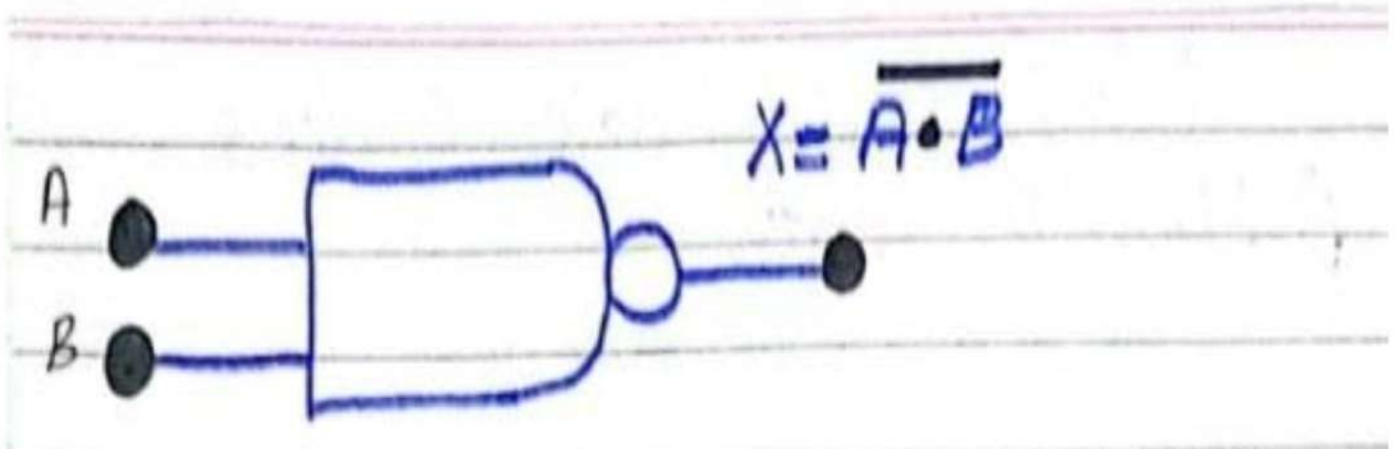

2) NOR Gate

The NOR Gate is obtained by joining the output of OR gate with the NOT Gate. The NOT Gate inverts the output of OR gate.


Boolean Expression: $X = (A + B)' = \overline{A + B}$

It is read as 'X equals A OR B NOT'.


Truth Table – NOR Gate:

switch(input)		OR GATE	Lamp (output)
A	B	$A + B$	$\overline{A + B}$
1	0	1	0
0	1	1	0
1	1	1	0
0	0	0	1

Description:

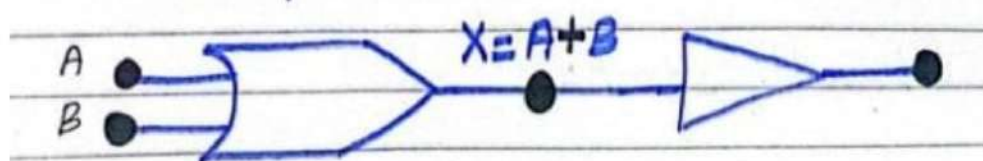

Circuit Symbol:

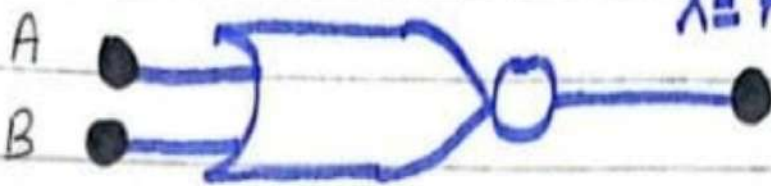

PKMZ - Universal Logic Gates (Physics Kahani Mak Zabani)

NAND = AND ka ulta. NOR = OR ka ulta. Dono universal gates hain kyunki inhi se AND, OR, NOT sab banaye ja sakte hain. NAND aur NOR mein output mein ek bubble hota hai - matlab NOT lag gaya. Yaad karo: NAND mein sirf jab dono 1 hon tab 0 aata hai, baaki sab mein 1.

MCQs

1. How many fundamental (basic) logic gates are there?

- A) 2
- B) 3
- C) 5
- D) 7

Answer: B) 3

Explanation: There are three fundamental logic gates: AND, OR, and NOT. All other logic functions can be constructed from combinations of these three. In practice, NAND and NOR are also considered universal gates because any logic function can be built from NAND gates alone or NOR gates alone, making them even more fundamental in IC manufacturing.

2. The output of a NOT gate when input is 1 is:

- A) 1
- B) 0
- C) Undefined
- D) 2

Answer: B) 0

Explanation: A NOT gate (inverter) has a single input and produces the logical complement of its input: NOT 1 = 0 and NOT 0 = 1. It is the simplest logic gate, implementing Boolean complementation. In digital circuits, it is represented by a triangle with a small circle (bubble) at the output. The bubble symbol indicates inversion.

3. The AND gate output is HIGH (1) only when:

- A) Any one input is HIGH

- B) All inputs are LOW
- C) All inputs are HIGH
- D) Any input is LOW

Answer: C) All inputs are HIGH

Explanation: The AND gate implements the Boolean AND operation. Its output is 1 ONLY when ALL inputs are 1 simultaneously. If any input is 0, the output is 0. For two inputs, truth table: $0 \cdot 0 = 0$, $0 \cdot 1 = 0$, $1 \cdot 0 = 0$, $1 \cdot 1 = 1$. The AND gate is analogous to series switches – current flows only if ALL switches are closed.

4. The OR gate output is LOW (0) only when:

- A) All inputs are HIGH
- B) Any one input is HIGH
- C) All inputs are LOW
- D) Any input is LOW

Answer: C) All inputs are LOW

Explanation: The OR gate implements the Boolean OR (+) operation. Its output is 0 ONLY when ALL inputs are 0 simultaneously. If any input is 1, the output is 1. Truth table: $0 + 0 = 0$, $0 + 1 = 1$, $1 + 0 = 1$, $1 + 1 = 1$. Analogous to parallel switches – current flows when either or both switches are closed.

5. A NAND gate is equivalent to:

- A) AND followed by OR
- B) AND followed by NOT (an inverted AND gate)
- C) OR followed by NOT
- D) Two NOT gates

Answer: B) AND followed by NOT (an inverted AND gate)

Explanation: NAND (NOT-AND) = AND gate followed by an inverter (NOT gate). Output = NOT(A AND B). For two inputs:

0 NAND 0=1, 0 NAND 1=1, 1 NAND 0=1, 1 NAND 1=0. The only way to get a 0 output from NAND is when ALL inputs are 1. NAND is universal – any logic function can be built from NAND gates alone.

6. A NOR gate is equivalent to:

- A) NOT followed by AND
- B) OR followed by NOT (an inverted OR gate)
- C) AND followed by NOT
- D) Two OR gates

Answer: B) OR followed by NOT (an inverted OR gate)

Explanation: NOR (NOT-OR) = OR gate followed by an inverter. Output = NOT(A OR B). For two inputs: 0 NOR 0=1, 0 NOR 1=0, 1 NOR 0=0, 1 NOR 1=0. The only way to get a 1 output from NOR is when ALL inputs are 0. NOR is also universal – any logic function can be implemented using only NOR gates.

7. The XOR (Exclusive OR) gate output is HIGH (1) when:

- A) All inputs are HIGH
- B) All inputs are LOW
- C) An odd number of inputs are HIGH (for 2 inputs: inputs are different)
- D) Any input is HIGH

Answer: C) An odd number of inputs are HIGH (for 2 inputs: inputs are different)

Explanation: XOR output is 1 when inputs are DIFFERENT (for 2-input XOR: one is 0 and the other is 1). Truth table: 0+0=0, 0+1=1, 1+0=1, 1+1=0. For multi-input XOR, the output is 1 when an ODD number of inputs are 1. XOR is used in binary adders (sum bit), parity checkers, and encryption circuits.

8. The XNOR gate is the complement of XOR, so it outputs 1 when:

- A) Inputs are different
- B) Inputs are the same
- C) All inputs are 0
- D) All inputs are 1

Answer: B) Inputs are the same

Explanation: XNOR (Exclusive NOR) is the complement of XOR. It outputs 1 when inputs are the SAME (both 0 or both 1). Truth table: $0 \text{ XNOR } 0 = 1$, $0 \text{ XNOR } 1 = 0$, $1 \text{ XNOR } 0 = 0$, $1 \text{ XNOR } 1 = 1$. XNOR is called an 'equality detector' – it detects when two bits are equal. It is used in comparators and error detection circuits.

9. Which gate is called a 'universal gate'?

- A) AND and OR only
- B) NAND and NOR
- C) XOR only
- D) NOT only

Answer: B) NAND and NOR

Explanation: NAND and NOR are called universal gates because ANY Boolean function can be implemented using only NAND gates or only NOR gates, without needing any other gate types. This is important in integrated circuit manufacturing: by fabricating only one type of gate, all logic functions can be realized, reducing manufacturing complexity and cost.

10. The Boolean expression for a NAND gate with inputs A and B is:

- A) $A \cdot B$
- B) $A + B$

C) $\text{NOT}(A \cdot B) = A\text{-bar} + B\text{-bar}$

D) $A \text{ XOR } B$

Answer: C) $\text{NOT}(A \cdot B) = A\text{-bar} + B\text{-bar}$

Explanation: The NAND output is the complement of the AND output: $F = \text{NOT}(A \cdot B)$. By De Morgan's theorem, this equals $A\text{-bar} + B\text{-bar}$. The NAND gate's truth table has output 0 only when $A=1$ AND $B=1$; all other combinations give output 1. This is the exact opposite (complement) of the AND gate truth table.

11. The Boolean expression for a NOR gate with inputs A and B is:

A) $A+B$

B) $\text{NOT}(A+B) = A\text{-bar} \cdot B\text{-bar}$

C) $A \cdot B$

D) $A\text{-bar} + B\text{-bar}$

Answer: B) $\text{NOT}(A+B) = A\text{-bar} \cdot B\text{-bar}$

Explanation: The NOR output is the complement of the OR output: $F = \text{NOT}(A+B)$. By De Morgan's theorem, this equals $A\text{-bar} \cdot B\text{-bar}$. The NOR gate's truth table has output 1 only when $A=0$ AND $B=0$; all other combinations give output 0. This is the exact opposite (complement) of the OR gate truth table.

12. How many rows does a truth table for a 3-input logic gate have?

A) 3

B) 6

C) 8

D) 9

Answer: C) 8

Explanation: For n inputs, the truth table has 2^n rows

representing all possible input combinations. For 3 inputs: $2^3 = 8$ rows. The rows list all combinations from 000 to 111 in binary order. For 2 inputs: 4 rows; 4 inputs: 16 rows; 8 inputs: 256 rows. The number of rows grows exponentially with the number of inputs.

13. The logic symbol for a NOT gate includes:

- A) A triangle with a bubble (circle) at the output
- B) A D-shaped symbol
- C) A curved shape
- D) A rectangle

Answer: A) A triangle with a bubble (circle) at the output

Explanation: The NOT gate (inverter) is represented by a triangle (pointing in the direction of signal flow) with a small circle (bubble) at the output. The bubble universally represents inversion in logic diagrams. The same bubble appears on the outputs of NAND and NOR gates, always indicating logical negation.

14. Implementing NOT using a NAND gate is done by:

- A) Connecting one input to logic 1
- B) Connecting both inputs together
- C) Using three NAND gates
- D) Connecting one input to logic 0

Answer: B) Connecting both inputs together

Explanation: To make a NOT gate from a NAND gate, connect both inputs to the same signal A: output = $\text{NOT}(A \cdot A) = \text{NOT}(A) = A\text{-bar}$. Truth check: when $A=0$: $\text{NOT}(0 \cdot 0) = \text{NOT}(0) = 1$; when $A=1$: $\text{NOT}(1 \cdot 1) = \text{NOT}(1) = 0$. Similarly, a NOR gate with both inputs tied together also forms a NOT gate: $\text{NOT}(A + A) = \text{NOT}(A) = A\text{-bar}$.

15. An AND gate can be constructed from NAND gates by:

- A) Using one NAND gate only
- B) Using a NAND gate followed by a NOT gate (two NAND gates)
- C) Using three NAND gates in parallel
- D) It cannot be done

Answer: B) Using a NAND gate followed by a NOT gate (two NAND gates)

Explanation: AND = NAND followed by NOT. Since NOT can be made from a NAND gate (both inputs tied together), we use 2 NAND gates: first NAND gives $\text{NOT}(A \cdot B)$, second NAND (with tied inputs) gives $\text{NOT}(\text{NOT}(A \cdot B)) = A \cdot B$. Double inversion restores the AND function.

16. An OR gate can be constructed from NAND gates using:

- A) One NAND gate
- B) Two NAND gates
- C) Three NAND gates
- D) Four NAND gates

Answer: C) Three NAND gates

Explanation: By De Morgan's theorem: $A+B = \text{NOT}(A\text{-bar} \cdot B\text{-bar})$. To implement: (1) NAND gate 1 with both inputs A gives NOT A; (2) NAND gate 2 with both inputs B gives NOT B; (3) NAND gate 3 with inputs NOT-A and NOT-B gives $\text{NOT}(\text{NOT-A} \cdot \text{NOT-B}) = A+B$. Three NAND gates implement OR.

17. The truth table for a 2-input XOR gate shows that output is 1 for how many input combinations?

- A) 1
- B) 2
- C) 3
- D) 4

Answer: B) 2

Explanation: XOR truth table: $0 \text{ XOR } 0=0$, $0 \text{ XOR } 1=1$, $1 \text{ XOR } 0=1$, $1 \text{ XOR } 1=0$. The output is 1 for exactly 2 out of 4 combinations: $(A=0, B=1)$ and $(A=1, B=0)$ – the cases where inputs are DIFFERENT. This is half of all possible input combinations, reflecting XOR's property as a 'difference detector'.

18. A half adder circuit adds two 1-bit binary numbers and produces:

- A) Only a sum bit
- B) A sum bit and a carry bit
- C) Only a carry bit
- D) A 4-bit output

Answer: B) A sum bit and a carry bit

Explanation: A half adder adds two single-bit binary inputs (A and B) and produces two outputs: Sum = $A \text{ XOR } B$ and Carry = $A \cdot B$ (AND of inputs). The 'carry' represents the overflow into the next bit position when $1+1=10$ (binary). It is called 'half' adder because it cannot handle an input carry from a previous bit – that requires a full adder.

19. The sum output of a half adder is implemented using:

- A) An AND gate
- B) A NOR gate
- C) An XOR gate
- D) A NAND gate

Answer: C) An XOR gate

Explanation: The sum of two 1-bit numbers A and B follows XOR logic: $0+0=0$ (sum=0), $0+1=1$ (sum=1), $1+0=1$ (sum=1), $1+1=10$ (sum=0, carry=1). The sum bit matches the XOR truth table exactly. The carry bit matches AND truth table. Hence: Sum = $A \text{ XOR } B$, Carry = $A \cdot B$.

20. Which gate can detect when two bits are equal?

- A) XOR
- B) XNOR
- C) NAND
- D) NOR

Answer: B) XNOR

Explanation: XNOR (equivalence gate) outputs 1 when both inputs are the SAME (equal): $0 \text{ XNOR } 0 = 1$, $1 \text{ XNOR } 1 = 1$. It outputs 0 when inputs differ. XOR does the opposite – it detects inequality. XNOR is used in digital comparators to check if two binary words are equal, comparing corresponding bits and ANDing all results.

21. In positive logic, the logic symbol with a curved input and a flat output represents:

- A) AND gate
- B) OR gate
- C) NOT gate
- D) NAND gate

Answer: B) OR gate

Explanation: The OR gate has a distinctive curved (arc-shaped) input side and a pointed output side. The AND gate has a flat input side and a curved (D-shaped) output. NOT has a triangle with a bubble. NAND and NOR have the AND/OR shapes respectively with an output bubble. These standardized symbols allow circuit diagrams to be understood universally.

22. The output of a 3-input AND gate is 1 only when:

- A) At least one input is 1
- B) Exactly two inputs are 1
- C) All three inputs are 1

D) At least two inputs are 1

Answer: C) All three inputs are 1

Explanation: The AND function always requires ALL inputs to be 1 for the output to be 1, regardless of the number of inputs. For a 3-input AND: $A \cdot B \cdot C = 1$ only when $A=1$ AND $B=1$ AND $C=1$. All other 7 combinations give output 0.

23. The output of a 3-input NOR gate is 1 only when:

A) All inputs are 1

B) All inputs are 0

C) At least one input is 1

D) Exactly two inputs are 1

Answer: B) All inputs are 0

Explanation: A 3-input NOR gate: output = $\text{NOT}(A+B+C)$. The OR of three inputs is 0 only when ALL three are 0. $\text{NOT}(0)=1$. For any other combination where at least one input is 1, the OR gives 1, and $\text{NOT}(1)=0$. So NOR output is 1 only when ALL inputs are 0.

24. Propagation delay in a logic gate refers to:

A) The time to manufacture the gate

B) The time delay between a change in input and the corresponding change in output

C) The power consumed during switching

D) The number of gate inputs

Answer: B) The time delay between a change in input and the corresponding change in output

Explanation: Propagation delay is the time it takes for a change in input to produce a corresponding change in output. It arises because transistors don't switch instantaneously and there are parasitic capacitances to charge/discharge. Typical propagation delays: CMOS $\sim 1-10$ ns, ECL < 1 ns.

Minimising propagation delay is essential for high-speed digital circuits.

25. Fan-out of a logic gate refers to:

- A) The number of inputs a gate can accept
- B) The maximum number of gate inputs that can be connected to (driven by) one gate output
- C) The power supply voltage
- D) The switching frequency

Answer: B) The maximum number of gate inputs that can be connected to (driven by) one gate output

Explanation: Fan-out is the number of gate inputs that a single gate output can drive while maintaining valid logic levels. If too many gates are connected to one output, the driving gate cannot supply/sink enough current, causing the output voltage to deviate outside the valid logic level range. Typical TTL fan-out is 10; CMOS fan-out can be much higher.

26. A logic gate with n inputs implements a Boolean function of:

- A) 1 variable
- B) n variables
- C) $2n$ variables
- D) n squared variables

Answer: B) n variables

Explanation: A logic gate with n inputs takes n binary input variables and produces one binary output. The output is a Boolean function of those n input variables. For example, a 3-input NAND gate computes $F(A, B, C) = \text{NOT}(A \cdot B \cdot C)$. The truth table has 2^n rows representing all possible combinations of the n binary variables.

27. The bubble (small circle) on a logic gate symbol

represents:

- A) Power input
- B) Clock input
- C) Logical inversion (NOT)
- D) An analogue input

Answer: C) Logical inversion (NOT)

Explanation: A small circle (bubble) in a logic gate symbol universally represents logical inversion (NOT operation) at that point. It can appear at inputs or outputs. Examples: a bubble at the output of an AND gate turns it into a NAND gate; a bubble at the output of an OR gate turns it into NOR. The bubble is a standard IEEE logic symbol notation.

28. To verify the correct operation of a logic gate, one would use:

- A) An oscilloscope only
- B) A truth table to check all input-output combinations
- C) Only a voltmeter
- D) A frequency counter

Answer: B) A truth table to check all input-output combinations

Explanation: To completely verify a logic gate, all 2^n input combinations must be tested and the output for each compared against the expected truth table. This ensures the gate correctly implements its logic function for every possible input. In practice, logic analysers and simulation tools automate this verification.

29. Which Boolean expression represents a 2-input XOR gate?

- A) $A+B$
- B) $A \cdot B$
- C) $A \text{ XOR } B = A\text{-bar} \cdot B + A \cdot B\text{-bar}$

D) $\text{NOT}(A \cdot B)$

Answer: C) $A \text{ XOR } B = \bar{A} \cdot B + A \cdot \bar{B}$

Explanation: XOR can be expressed as $A \text{ XOR } B = \bar{A} \cdot B + A \cdot \bar{B}$. This means: (NOT A AND B) OR (A AND NOT B) – output is 1 when A is 0 and B is 1, OR when A is 1 and B is 0. This is precisely 'inputs are different'.

30. Implementing a logic circuit using only NAND gates demonstrates that NAND is:

- A) Limited to two-input functions
- B) A universal gate
- C) Only useful for AND functions
- D) Less efficient than AND/OR/NOT

Answer: B) A universal gate

Explanation: NAND being universal means it can implement any Boolean function. Proof: NOT can be made from NAND (tie inputs). $\text{AND} = \text{NAND} + \text{NOT}(\text{NAND})$. $\text{OR} = \text{NAND}(\text{NOT } A, \text{NOT } B)$ by De Morgan's. Since NOT, AND, and OR are complete, NAND alone can implement ANY logic function.

31. The output of an AND gate with three inputs A, B, C where $A=1, B=0, C=1$ is:

- A) 1
- B) 0
- C) Depends on order
- D) Undefined

Answer: B) 0

Explanation: For a 3-input AND gate: $F = A \cdot B \cdot C = 1 \cdot 0 \cdot 1 = 0$. The AND function requires ALL inputs to be 1 simultaneously. Since $B=0$, the output is 0, regardless of the values of A and C. Even one LOW input forces the AND output LOW.

32. What is the output of a NOR gate with inputs $A=0, B=0$?

- A) 0
- B) 1
- C) Depends on supply voltage
- D) 0.5

Answer: B) 1

Explanation: NOR gate: $F = \text{NOT}(A+B) = \text{NOT}(0+0) = \text{NOT}(0) = 1$. The NOR gate's output is 1 ONLY when ALL inputs are 0. Since $A=0$ and $B=0$, the OR of inputs is 0, and $\text{NOT}(0) = 1$. All other input combinations (where at least one input is 1) give NOR output = 0.

33. The NOT gate is also known as:

- A) Buffer
- B) Inverter
- C) Multiplexer
- D) Encoder

Answer: B) Inverter

Explanation: The NOT gate is called an 'inverter' because it inverts (complements) its input: 0 becomes 1 and 1 becomes 0. The term 'inverter' emphasizes its function of turning a signal upside-down. A buffer is a different circuit that maintains the same logic level (1 to 1, 0 to 0) but provides current amplification without inversion.

SRQs

Q1. Describe the operation of a 2-input AND gate with a truth table.

Answer: An AND gate outputs 1 only when ALL inputs are 1. Boolean expression: $F = A.B$. Truth table: $(A=0, B=0)$ gives $F=0$; $(A=0, B=1)$ gives $F=0$; $(A=1, B=0)$ gives $F=0$; $(A=1, B=1)$ gives $F=1$. The output is HIGH for only 1 of 4 input

combinations.

Q2. Describe the operation of a 2-input OR gate with a truth table.

Answer: An OR gate outputs 1 when ANY input is 1. Boolean expression: $F = A+B$. Truth table: (A=0,B=0) gives F=0; (A=0,B=1) gives F=1; (A=1,B=0) gives F=1; (A=1,B=1) gives F=1. The output is LOW only when ALL inputs are 0.

Q3. Explain why NAND and NOR gates are called universal gates.

Answer: NAND and NOR are universal because any Boolean function can be implemented using only NAND gates (or only NOR gates), without needing any other gate type. Using NAND: NOT is made by tying both inputs together; AND = NAND followed by a NOT-NAND; OR = NAND with inverted inputs. Since NOT, AND, and OR is a complete set, NAND alone is sufficient for any logic circuit.

Q4. Write the truth table for a 2-input NAND gate and state its Boolean expression.

Answer: Boolean expression: $F = \text{NOT}(A \cdot B) = \bar{A} + \bar{B}$. Truth table: (0,0) gives 1; (0,1) gives 1; (1,0) gives 1; (1,1) gives 0. The output is 0 ONLY when both inputs are 1 – the opposite of an AND gate. NAND is the complement of AND.

Q5. Explain the operation of an XOR gate and give one application.

Answer: XOR (Exclusive OR) outputs 1 when inputs are DIFFERENT. Boolean expression: $F = A \text{ XOR } B = \bar{A} \cdot B + A \cdot \bar{B}$. Truth table: (0,0) gives 0; (0,1) gives 1; (1,0) gives 1; (1,1) gives 0. Application: Binary addition – in a half adder, the Sum bit = A XOR B. XOR is also used in parity checkers and simple encryption.

Q6. How can a NOT gate be constructed using a NAND gate? Explain with Boolean algebra.

Answer: Connect both inputs of a NAND gate to the same signal A . Output = NOT($A \cdot A$). By the idempotent law of Boolean algebra: $A \cdot A = A$. Therefore output = NOT(A) = \bar{A} . Verification: when $A=0$: NOT($0 \cdot 0$) = NOT(0) = 1; when $A=1$: NOT($1 \cdot 1$) = NOT(1) = 0. A NAND gate with tied inputs acts as an inverter (NOT gate).

Q7. Construct a truth table for a circuit with output $F = A \cdot B + C$ (where A, B, C are inputs).

Answer: With 3 inputs there are $2^3 = 8$ rows. Evaluating $F = A \cdot B + C$: (000) gives 0; (001) gives 1; (010) gives 0; (011) gives 1; (100) gives 0; (101) gives 1; (110) gives 1; (111) gives 1. $F=1$ for inputs: 001, 011, 101, 110, 111.

Q8. What is propagation delay and why is it important in digital circuits?

Answer: Propagation delay is the time between a change at a gate's input and the resulting change at its output. It arises from transistor switching times and parasitic capacitances. It is important because it limits the maximum clock frequency of a digital circuit – data must settle before the next clock edge. In complex circuits, different signal paths have different delays, potentially causing timing errors (glitches) if not managed properly.

Q9. Describe how a half adder is constructed from basic logic gates.

Answer: A half adder adds two 1-bit binary inputs (A, B) and produces Sum and Carry outputs. Sum = $A \text{ XOR } B$ (XOR gate – sum is 1 when inputs differ). Carry = $A \cdot B$ (AND gate – carry is 1 only when both inputs are 1, since $1+1=10$ in binary). The

circuit requires one XOR gate and one AND gate connected to the same two inputs.

Q10. State the logic gate corresponding to each of the following Boolean operations: AND, OR, NOT, NAND, NOR, XOR.

Answer: AND gate: $F=A \cdot B$ (output 1 only when all inputs are 1). OR gate: $F=A+B$ (output 1 when any input is 1). NOT gate (inverter): $F=A\text{-bar}$ (output is complement of input). NAND gate: $F=\text{NOT}(A \cdot B)$ (complement of AND). NOR gate: $F=\text{NOT}(A+B)$ (complement of OR). XOR gate: $F=A \text{ XOR } B$ (output 1 when inputs are different).

Q11. How many input combinations must be tested to fully verify a 4-input logic gate, and why?


Answer: A 4-input gate has $2^4 = 16$ possible input combinations (from 0000 to 1111 in binary). All 16 must be tested because the output may differ for each unique combination, and the only way to completely specify and verify a combinational logic function is to check every row of its truth table. Missing even one combination could leave a fault undetected.

Uses of Logic Gates

Burglar Alarm

A burglar alarm system is an electronic security arrangement used to detect unauthorized entry into a building or house. The system works with the help of sensors, logic gates, and an alarm device. Sensors are installed on doors, windows, and important areas. These sensors continuously monitor movement or opening. When someone tries to enter, the sensor produces an electrical signal. This signal is sent to a logic gate circuit. The logic gate processes the input according to Boolean logic. If the condition becomes true, the gate produces an output signal. This output activates a siren, bell, or light alarm.

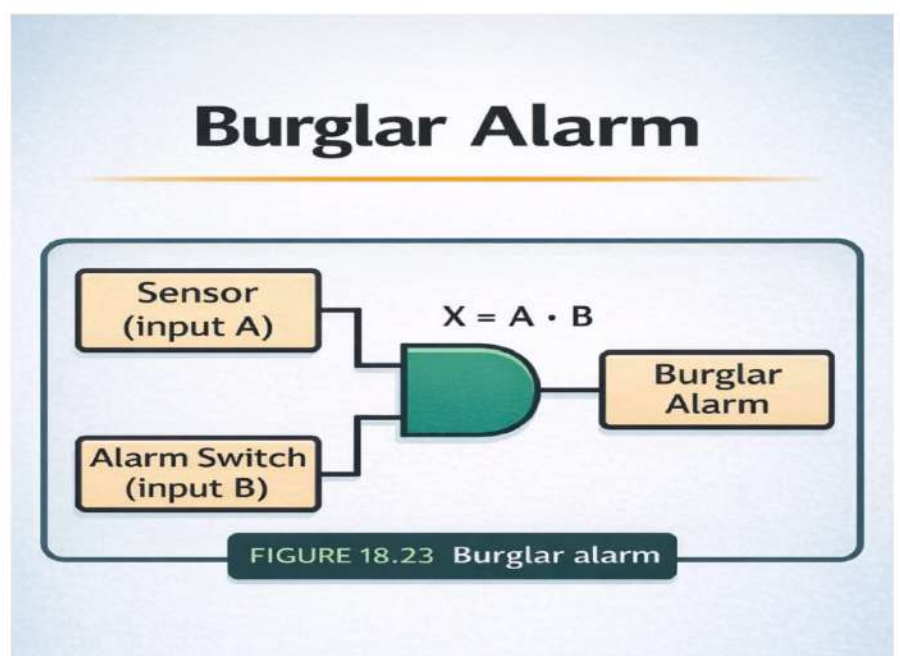In most burglar alarm circuits, an OR gate is used because an OR gate produces an output of 1 when any one of its inputs is 1. This means that if any one sensor detects intrusion, the alarm will activate. The system does not need multiple signals at the same time – it responds instantly to danger.



Example: Person sensor (Input A) and Alarm switch (Input B) are connected to an AND gate. If both sensor gives 1 and alarm switch gives 1, then output = 1 and alarm rings: $X = A \cdot B$.

Fire Extinguisher System

Before (no fire)

Buzzer is silent because the output of NAND gate A is 0. Input of the NAND gate is input 1 and input 2.

Charges flow from high potential and flow in a path where resistance is lower as it have pathway of thermistor, but thermistor has high resistance because it has low temperature (cool) therefore charges flow from another path which is input 1 (input of NAND gate 1 A) so, the input is high value 1.

Input 2 (input NAND A gate) which is the output of NAND (B) gate.

Input's of NAND B gate is 3 and 4.

Input 3 of NAND gate B is connected to lower potential so, they have a value of input 3.

Input 4 of NAND gate B is connected to a path of thermistor which don't have any flow of charges so, it's input 4 is 0.

Output of NAND gate B is 1.

Output of the NAND gate B is the input 2 of NAND gate A so, the input 2 is 1.

As the input 1 is 1 and input 2 of NAND gate A is also 1 so, the output of NAND gate A is 0 which means there is no fire and not the activation of buzzer.

Condition of the Thermistor

The circuit uses an NTC (Negative Temperature Coefficient) thermistor.

In normal room temperature (no fire), the temperature is low.

For an NTC thermistor:

Low temperature \rightarrow High resistance

Because of high resistance, very little current flows through the thermistor.

Flow of Charges

Electric charges always move from high potential to low potential. However, since the thermistor has high resistance, it restricts the flow of current. Therefore, the voltage level at the connected input does not change significantly.

Inputs of NAND Gate B

Input 3 of NAND Gate B is connected to low potential (logic 0).

Input 4 is connected through the thermistor. Since the thermistor has high resistance (no fire), the current does not flow properly, and this input also remains at logic 0.

Inputs of NAND Gate A

Input 1 of NAND Gate A is connected to high potential (logic 1).

Input 2 of NAND Gate A is the output of NAND Gate B.

Condition of the Buzzer

The buzzer is connected to the output of NAND Gate A.

Since the output is 0 (low), the buzzer remains OFF.

Final Result (No Fire)

Thermistor has high resistance → Logic does not change → Final output is 0 → Buzzer

After (fire)

Buzzer is active.

In this case, flow of charges from high potential is flow from their and acquire the path of thermistor.

Because, thermistor have lower resistance than other due to their increase in the temperature so, charges flow from thermistor.

As the input 1 of NAND gate is connected to path of charges, so, charges doesn't flow to their high resistance.

So, the input 1 of NAND gate A is 0.

Whereas input 2 (NAND gate A) is the output of NAND gate B.

Input 3 (NAND gate B) is connected to lower potential so, their input value is 0.

Input 4 (NAND gate B) is connected to the path of thermistor (path of flow of charges) so, their input 4 is 1.

Which becomes the output of NAND gate B is 1.

The output of NAND gate B is 1, which is the input of NAND gate A.

So, input 2 is 1.

Which becomes the output of NAND gate A is 1 resulting in the activating of buzzer.

1 = (higher ON) , 0 = (lower , OFF)

Effect of Fire on Thermistor

When fire occurs, temperature increases.

For an NTC thermistor:

High temperature → Low resistance

Now the thermistor allows more current to flow.

Flow of Charges

Since resistance decreases, current flows easily through the thermistor.

This changes the voltage level at the connected input of the NAND gate.

Inputs of NAND Gate B

Input 3 remains connected to low potential (0).

Input 4 now receives current because the thermistor resistance is low.

Therefore, Input 4 becomes logic 1.

However, in a properly designed fire alarm circuit, the change in thermistor resistance ultimately causes one of the inputs of NAND Gate A to become 0, resulting in output 1.


Condition of the Buzzer

When the final output becomes 1 (high), the buzzer is activated.

Thus, the buzzer turns ON and produces an alarm sound.

Final Result (Fire Condition)

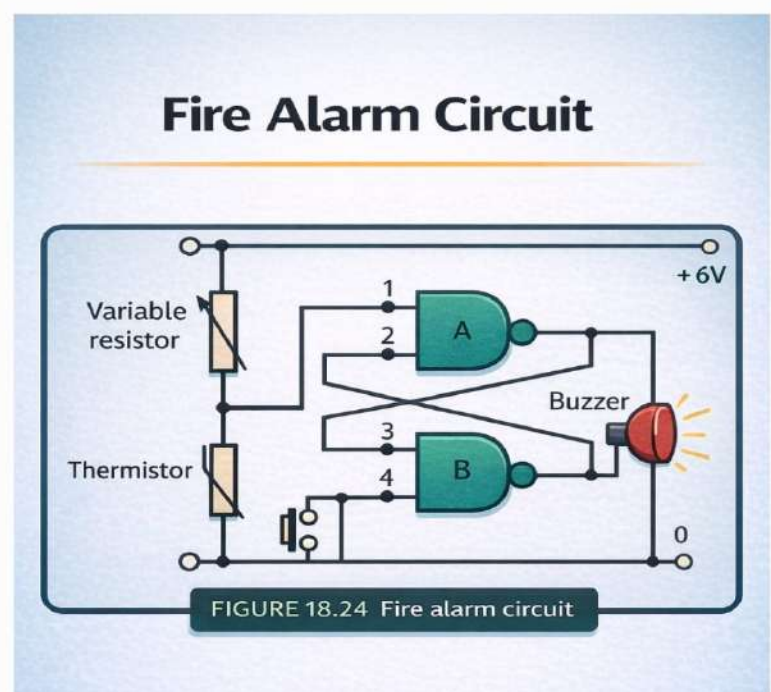Thermistor resistance decreases → Logic level changes → Final output becomes 1 → Buzzer ON



Aspect	Burglar Alarm	Fire Alarm
Purpose	Detect unauthorized entry	Detect smoke/heat/fire
Common gate used	OR gate	AND gate
Sensors	Motion/door sensors	Smoke & heat sensors
Output activates	Siren or bell	Alarm + sprinkler
Why that gate?	Any one sensor = alert	Both sensors must confirm fire

Information:

Fire Alarm Circuits and Smoke Sensors are a part of the security systems which help in detecting or preventing damage. Installing Fire Alarm Systems and Smoke Sensors in commercial buildings like offices, hospitals, schools, shopping malls and other public places is compulsory.



PKMZ – Uses of Logic Gates (Physics Kahani Mak Zabani)


Burglar alarm mein AND gate use hota hai – koi bhi ek sensor activate ho to alarm bajega. Fire alarm mein OR gate use hota hai – smoke sensor aur heat sensor dono 1 hon tab hi alarm bajega (false alarm se bachne ke liye). Dono systems mein sensors input hain aur alarm output hai. Logic gates buildings ko smart banate hain.



Analogue Electronics


Analogue electronics deals with continuous signals that change smoothly with time. The voltage or current can take

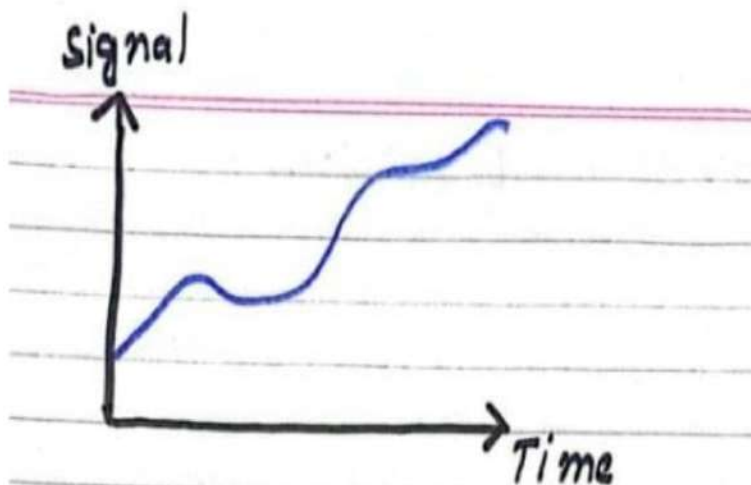infinite values within a range, representing real-world quantities like sound, light, and temperature. Analogue circuits use resistors, capacitors, diodes, and transistors to process signals. Devices such as radios, microphones, and amplifiers rely on analogue systems. They provide natural and detailed representation of information but are sensitive to noise and interference.



Digital Electronics

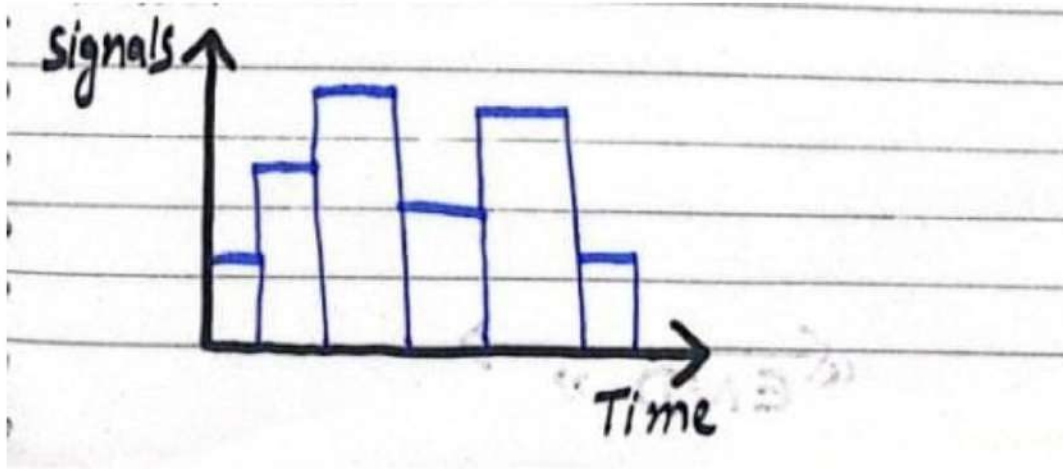Digital electronics works with discrete signals, mainly 0 and 1, representing LOW and HIGH voltage levels. These systems process information in binary form, making them suitable for computers and modern devices. Digital circuits use logic gates, microprocessors, and memory units. Digital signals are reliable and less affected by noise, and data can be stored, transmitted, and copied easily.



Aspect	Analogue Electronics	Digital Electronics
Signal type	Continuous (smooth)	Discrete (0 and 1 only)
Signal shape	Smooth curve / sine wave	Square/step wave
Noise immunity	Low — easily distorted	High — resists noise
Data storage	Difficult	Easy — binary form
Components	Resistors, capacitors, transistors	Logic gates, microprocessors
Processing speed	Real-time but slower	Very fast
Accuracy	High resolution naturally	Depends on bit resolution
Applications	Radio, amplifier, microphone	Computers, phones, calculators
Examples	FM radio, vinyl records, analog watch	Smartphones, digital watch, GPS
Advantages	Natural representation, real-time	Noise resistant, programmable
Disadvantages	Sensitive to noise, hard to store	Needs ADC conversion, complex

MCQs

- The AND gate gives HIGH output when
 - A) Any one input is HIGH
 - B) All inputs are HIGH
 - C) All inputs are LOW
 - D) Any one input is LOW

Correct Option: B

Explanation: AND gate performs logical multiplication. The output becomes 1 only when every input is 1; otherwise output is 0.

- The OR gate gives LOW output when
 - A) All inputs are LOW
 - B) Any one input is HIGH
 - C) All inputs are HIGH
 - D) Two inputs are HIGH

Correct Option: A

Explanation: OR gate performs logical addition. Output is 0 only when all inputs are 0.

- A NOT gate is also called
 - A) Buffer
 - B) Inverter
 - C) Converter
 - D) Amplifier

Correct Option: B

Explanation: NOT gate inverts the input signal. If input is 1 output becomes 0, and if input is 0 output becomes 1.

- NAND gate is called universal gate because
 - A) It is simple
 - B) It uses less power

C) It can make any logic circuit

D) It has two inputs

Correct Option: C

Explanation: Using only NAND gates, we can design AND, OR, and NOT gates. Therefore it is called a universal gate.

● Which gate gives HIGH output when inputs are different?

A) AND

B) OR

C) XOR

D) NOR

Correct Option: C

Explanation: XOR gate produces output 1 when inputs are unlike (0,1 or 1,0).

● Logic gates operate on

A) Continuous signals

B) Mechanical signals

C) Binary signals

D) Sound waves

Correct Option: C

Explanation: Logic gates work with digital signals represented by two levels: 0 and 1.

In digital circuits, HIGH level usually represents

A) 0

B) 1

C) -1

D) Infinity

Correct Option: B

Explanation: In binary system, HIGH voltage corresponds to logic 1.

● The output of NAND gate is LOW when

- A) All inputs are HIGH
- B) Any input is LOW
- C) All inputs are LOW
- D) One input is HIGH

Correct Option: A

Explanation: NAND is NOT-AND. When AND output is 1 (all inputs 1), NAND output becomes 0.

XOR gate is mainly used in

- A) Rectifiers
- B) Adders
- C) Amplifiers
- D) Transformers

Correct Option: B

Explanation: XOR gate is used in half and full adders to perform binary addition.

Universal gates are

- A) AND, OR
- B) NAND, NOR
- C) XOR, XNOR
- D) NOT only

Correct Option: B

Explanation: Both NAND and NOR gates can be used to implement all other basic gates.

Logic gates are made using

- A) Resistors only
- B) Capacitors only
- C) Transistors
- D) Inductors

Correct Option: C

Explanation: Transistors act as electronic switches in digital

circuits to build logic gates.

● In Boolean algebra, multiplication represents

- A) OR
- B) AND
- C) NOT
- D) XOR

Correct Option: B

Explanation: Logical multiplication corresponds to AND operation.

● Digital calculator works on

- A) Analogue system
- B) Logic gates
- C) Mechanical gears
- D) Hydraulic system

Correct Option: B

Explanation: Calculators process binary data using digital logic circuits.

● A buffer gate is used to

- A) Invert signal
- B) Increase signal strength
- C) Decrease voltage
- D) Block signal

Correct Option: B

Explanation: Buffer strengthens or isolates signals without changing their logic level.

● A 2-input AND gate has how many input combinations?

- A) 2
- B) 3
- C) 4
- D) 5

Correct Option: C

Explanation: Two inputs can form $2^2 = 4$ combinations (00, 01, 10, 11).

● Burglar alarm system is used for

- A) Cooling
- B) Security
- C) Lighting
- D) Heating

Correct Option: B

Explanation: Burglar alarms detect unauthorized entry and provide security by activating an alert.

● A simple burglar alarm can be made using

- A) AND gate
- B) NAND gate
- C) NOT gate
- D) XOR gate

Correct Option: B

Explanation: NAND gate is commonly used because it activates alarm when both inputs meet a specific condition.

● The sensor in burglar alarm detects

- A) Motion or opening
- B) Heat only
- C) Sound only
- D) Light only

Correct Option: A

Explanation: Sensors detect door opening, motion, or disturbance to trigger the alarm.

● Output device in burglar alarm is usually

- A) Fan
- B) Bulb

C) Siren

D) Motor

Correct Option: C

Explanation: A siren or buzzer produces sound to alert people during intrusion.

● Burglar alarm works on

A) Analogue signals

B) Digital logic

C) Hydraulic power

D) Steam power

Correct Option: B

Explanation: It uses binary conditions (door open/closed) processed by logic gates.

● A broken wire in alarm circuit

A) Activates alarm

B) Stops alarm

C) Charges battery

D) Reduces noise

Correct Option: A

Explanation: Breaking the circuit changes logic condition and triggers the alarm for safety.

● Digital electronics deals with

A) Continuous signals

B) Binary signals

C) Sound waves

D) Heat energy

Correct Option: B

Explanation: Digital electronics processes signals in discrete form (0 and 1).

● Analogue signals vary

- A) Discretely
- B) In steps
- C) Continuously
- D) Digitally

Correct Option: C

Explanation: Analogue signals change smoothly over time and can take infinite values.

- Example of digital device

- A) Mercury thermometer
- B) Digital clock
- C) Microphone
- D) Speaker

Correct Option: B

Explanation: Digital clock displays time in numerical digits using binary logic.

- Example of analogue device

- A) Calculator
- B) Computer
- C) Mercury thermometer
- D) Smartphone

Correct Option: C

Explanation: Mercury thermometer shows continuous temperature variation.

- Digital system is less affected by

- A) Noise
- B) Voltage
- C) Current
- D) Resistance

Correct Option: A

Explanation: Digital signals have clear levels (0 and 1), so

small noise does not affect them easily.

- In digital system, data is represented by

- A) Waves
- B) 0 and 1
- C) Graph
- D) Frequency

Correct Option: B

Explanation: Digital electronics uses binary number system.

- Analogue electronics is used in

- A) Amplifiers
- B) Counters
- C) Flip flops
- D) Logic gates

Correct Option: A

Explanation: Amplifiers process continuous signals, which are analogue in nature.

- Digital signals have

- A) Infinite values
- B) Two levels
- C) Continuous variation
- D) Random values

Correct Option: B

Explanation: Digital signals have only two distinct levels: HIGH and LOW.

- Digital electronics is preferred because it is

- A) Less reliable
- B) Noisy
- C) More reliable
- D) Continuous

Correct Option: C

Explanation: Digital systems are more reliable, accurate, and easier to store and process.

SRQs

1. What is a logic gate?

Answer: A logic gate is an electronic circuit that performs a basic logical operation on one or more binary inputs to produce a single output. It works on two voltage levels representing 0 and 1. Logic gates are the building blocks of digital electronics and are made using transistors.

2. Why is AND gate called a decision-making gate?

Answer: AND gate produces HIGH output only when all inputs are HIGH. This means it checks multiple conditions at the same time. If even one condition is false (0), the output becomes 0. Therefore, it is used where all required conditions must be satisfied.

3. Explain the working of OR gate.

Answer: OR gate gives HIGH output if any one of its inputs is HIGH. It performs logical addition in Boolean algebra. The output becomes LOW only when all inputs are LOW. It is used when at least one condition must be true.

4. What is the function of NOT gate?

Answer: NOT gate inverts the input signal. If input is 1, output becomes 0; if input is 0, output becomes 1. It is also

called an inverter. It is used to reverse logic conditions in digital circuits.

5. Why is NAND gate called a universal gate?

Answer: NAND gate is called universal because all other basic gates (AND, OR, NOT) can be constructed using only NAND gates. This makes it very important in digital circuit design.

6. What is meant by universal gate?

Answer: A universal gate is a logic gate that can be used to implement any Boolean function without using other types of gates. NAND and NOR gates are examples because they can form all other gates.

7. Define Boolean algebra.

Answer: Boolean algebra is a mathematical system used to analyze and simplify digital logic circuits. It works with binary numbers 0 and 1 and includes operations like AND, OR, and NOT.

8. What is the role of transistors in logic gates?

Answer: Transistors act as electronic switches in logic gates. They control the flow of current based on input signals. By switching ON and OFF, they produce binary outputs required for digital circuits.

9. What is XOR gate and where is it used?

Answer: XOR gate gives HIGH output when inputs are different. It is mainly used in binary addition circuits like half adders and full adders because it performs sum operation without carry.

10. What is a buffer gate?

Answer: A buffer gate passes the input to output without changing its logic level. It strengthens weak signals and provides isolation between circuits to prevent loading effects.

11. What is a burglar alarm system?

Answer: A burglar alarm system is an electronic security system designed to detect unauthorized entry. It uses sensors and logic circuits to activate a siren or buzzer when intrusion occurs.

12. How does a simple burglar alarm work?

Answer: A simple burglar alarm uses a switch on a door or window. When the door opens, the circuit condition changes. The logic gate detects this change and activates the alarm sound.

13. What is the function of sensor in burglar alarm?

Answer: The sensor detects changes such as motion, door opening, or vibration. It converts physical movement into electrical signals that are processed by logic circuits.

14. Why are logic gates used in burglar alarms?

Answer: Logic gates process binary conditions such as door open (1) or closed (0). They decide when to activate the alarm based on specific logical combinations.

15. What happens when the alarm circuit wire breaks?

Answer: When the wire breaks, the circuit condition changes. This change is detected as an intrusion, and the alarm is activated to ensure safety.

16. What is meant by digital electronics?

Answer: Digital electronics deals with circuits that process discrete signals, usually represented by 0 and 1. It is used in computers, calculators, and digital clocks.

17. What is analogue electronics?

Answer: Analogue electronics deals with continuous signals that vary smoothly over time. Examples include amplifiers and radio circuits.

18. Give one difference between digital and analogue signals.

Answer: Digital signals have only two levels (0 and 1), while analogue signals vary continuously and can have infinite values between minimum and maximum.

19. Why is digital system more reliable than analogue?

Answer: Digital systems are less affected by noise because small disturbances do not change the logic level easily. Therefore, they provide more accurate and stable results.

20. What is noise in electronics?

Answer: Noise is an unwanted disturbance that affects signals in a circuit. Analogue signals are more affected by noise compared to digital signals.

21. What is ADC?

Answer: ADC stands for Analog to Digital Converter. It converts continuous analogue signals into digital form so they can be processed by digital systems.

22. What is the importance of logic gates in computers?

Answer: Logic gates perform arithmetic and logical operations inside the computer. They form processors and memory units that handle data processing.

23. What is binary number system?

Answer: Binary number system uses only two digits, 0 and 1. It is the basis of digital electronics because electronic circuits operate in two states.

24. Why is XOR gate important in adders?

Answer: XOR gate produces sum output in binary addition when inputs are different. It ensures correct addition without carry in half adders.

25. What is the main advantage of digital electronics?

Answer: Digital electronics provides high accuracy, easy storage of data, and better resistance to noise. It is also easier to design and maintain.

26. Give one disadvantage of analogue electronics.

Answer: Analogue systems are more affected by noise and signal distortion, which reduces accuracy.

27. What is NOR gate?

Answer: NOR gate is a combination of OR gate followed by NOT gate. It produces HIGH output only when all inputs are LOW.

28. How is digital clock different from analogue clock electronically?

Answer: A digital clock uses binary logic circuits to display time numerically, while an analogue clock uses continuous mechanical or electrical motion.

29. What is the role of siren in burglar alarm?

Answer: Siren acts as output device. When triggered, it produces loud sound to alert people about unauthorized entry.

30. Why are transistors preferred in digital circuits?

Answer: Transistors switch quickly between ON and OFF states, consume less power, and are reliable, making them suitable for digital circuits.

31. What is logic level?

Answer: Logic level refers to voltage level representing binary values. HIGH level represents 1 and LOW level represents 0.

32. What is meant by input combination?

Answer: Input combination refers to all possible arrangements of 0s and 1s at the inputs of a logic gate.

33. Why is digital data easy to store?

Answer: Digital data is stored as binary numbers, which can

be easily saved in memory devices without signal loss.

34. What is the function of AND gate in security system?

Answer: AND gate ensures alarm activates only when all required security conditions are met.

35. What is continuous signal?

Answer: A continuous signal is one that changes smoothly over time and can take infinite values within a range.

36. What is discrete signal?

Answer: A discrete signal has specific separate values, usually 0 and 1 in digital electronics.

37. Why is digital electronics used in mobile phones?

Answer: Mobile phones process data in binary form using digital circuits, providing accurate communication and storage.

38. What is logic circuit?

Answer: A logic circuit is a combination of logic gates designed to perform a specific logical function.

39. Why is analogue amplifier not used in digital logic?

Answer: Amplifiers work with continuous signals, while digital logic requires discrete binary signals.

40. What is security system?

Answer: A security system is an arrangement of electronic devices designed to detect and prevent unauthorized access.

41. How does motion detector work in alarm?

Answer: Motion detector senses movement and converts it into electrical signals that activate the alarm circuit.

42. What is logic 0?

Answer: Logic 0 represents LOW voltage level in digital electronics.

43. What is logic 1?

Answer: Logic 1 represents HIGH voltage level in digital electronics.

44. What is main application of NAND gate?

Answer: NAND gate is widely used in digital circuit design because it can replace other gates and simplify circuits.

45. What is difference between accuracy of digital and

analogue systems?

Answer: Digital systems are more accurate because they use fixed binary levels, while analogue systems may suffer from distortion.

46. What is flip-flop?

Answer: Flip-flop is a digital memory element made of logic gates that stores one bit of data.

47. Why are digital systems easy to program?

Answer: Digital systems operate on binary logic, which can be controlled and programmed easily using logical instructions

48. What is logical addition?

Answer: Logical addition is OR operation in Boolean algebra where output is 1 if any input is 1.

49. What is logical multiplication?

Answer: Logical multiplication is AND operation where output is 1 only if all inputs are 1.

50. Why is burglar alarm important in modern homes?

Answer: Burglar alarm provides safety by detecting intrusion instantly and alerting people, reducing risk of theft and increasing security.

Short Response Questions:

- How do N-type materials and forward biasing affect semiconductor devices?

Answer:

N-type material has extra electrons that increase the flow of current.

Forward bias lowers the barrier and allows charge carriers to move easily across the junction.

Both help the semiconductor device to conduct electricity more efficiently.

- Why are pentavalent impurities called donors and trivalent impurities acceptors?

Pentavalent impurities has five outer electrons and give one extra electron to the crystal so they are donors.

Trivalent impurities lack one electron and create a hole by accepting an electron, so they are called acceptors.

- How do relays improve electrical systems? Give examples.
Relays improve electrical systems by using a small current to control a much larger current safely.

They protect delicate control circuits from high power loads and allow automatic switching.

For example, relays are used in car starters, home appliances, and industrial machines.

- How does the three terminals of a transistor work together to amplify signals?

The emitter supplies charge carriers, the base controls their movement, and the collector collects them to form the output current.

A small input current at the base controls a larger current between the collector and emitter.

This process increases the strength of the signal, so the transistor works as an amplifier.

- Why is one end of a transistor highly doped and another the smallest in size?

One region of a transistor (the emitter) is heavily doped to supply a large number of charge carriers.

The base is very thin and lightly doped so that most of these carriers pass through without recombining.

This difference helps the transistor amplify current efficiently.

- What does the arrow in a transistor symbol represent, and why is it important?

The arrow in a transistor symbol shows the direction of conventional current through the emitter.

It also helps to identify whether the transistor is NPN (arrow out) or PNP (arrow in) type.

It is important because it shows how the transistor should be connected and biased in a circuit.

- Explain the normal biasing of an NPN transistor. what

happens if it is reversed?

In normal biasing, the **base-emitter junction** is forward biased and the **base-collector junction** is reverse biased. This allows electrons to flow from the **emitter** to the collector, so the **transistor** works as an **amplifier**.

If the **biasing is reversed**, the transistor will not conduct properly and will not **amplify the signal**.

■ **How does biasing (forward or reverse) change the depletion region in a diode?**

In **forward bias**, the depletion region becomes **narrower**, allowing charge carriers to cross the junction easily and **current to flow**.

In **reverse bias**, the depletion region becomes **wider**, which blocks the flow of **majority carriers**.

■ **Why does n-type or p-type material have zero net charge?**

N-type and **P-type** materials stay neutral overall.

The extra electrons or holes are balanced by opposite charges of impurity atoms.

So, there is no total charge in the material.

■ **Why are NAND and NOR gates are called universal gates?**

NAND and **NOR** gates are called universal gates because they can be used to make any other logic gate like **AND**, **OR** or **NOT**. This means any digital circuit can be built using only **NAND** or only **NOR** gates.

■ **For a NOR gate how do you determine the output for different inputs?**

A NOR gate gives an output 1 only when all inputs are 0.

If any input is 1, the output becomes 0.

So, for two inputs, only (0,0) gives output 1, and all other combinations give 0.

EXERCISE MCQS

1. The approximate potential barrier for germanium and silicon transistors are respectively?

Options:

- A. 0.3 V and 0.7 V
- B. 0.7 V and 0.3 V
- C. 0.7 V and 0.5 V
- D. 0.5 V and 0.7 V

Correct option: A. 0.3 V and 0.7 V

Explanation: The potential barrier is the minimum voltage required to overcome the depletion layer of a PN junction. In germanium it is about 0.3 V, while in silicon it is about 0.7 V.

2. The current ratio of beta (β) is:

Options:

- A. I_C / I_E
- B. I_B / I_C
- C. I_E / I_B
- D. I_C / I_B

Correct option: D. I_C / I_B

Explanation: Beta (β) is the current gain in common-emitter configuration and is defined as the ratio of collector current to base current.

3. Which of the following relation is correct for a transistor?

Options:

- A. $I_C = I_B + I_E$
- B. $I_B = I_C + I_E$
- C. $I_E = I_C + I_B$
- D. $I_E = I_C - I_B$

Correct option: C. $I_E = I_C + I_B$

Explanation: According to Kirchhoff's Current Law, emitter current is equal to the sum of collector and base currents.

4. The heavily doped region of the transistor is:

Options:

- A. Emitter
- B. Collector
- C. Base
- D. All of these

Correct option: A. Emitter

Explanation: The emitter is heavily doped to inject a large number of charge carriers. The base is lightly doped and thin, while the collector is moderately doped.

5. A transistor has _____ PN junctions.

Options:

- A. 1
- B. 2
- C. 3
- D. 4

Correct option: B. 2

Explanation: A bipolar junction transistor has three regions forming two PN junctions: emitter-base and collector-base.

6. If $I_E = 1$ mA and $I_C = 0.25$ mA then the value of I_B will be:

Options:

- A. 0.75 mA
- B. 0.95 mA
- C. 0.65 mA
- D. 0.85 mA

Correct option: A. 0.75 mA

Explanation: Using $I_E = I_C + I_B \rightarrow I_B = 1 - 0.25 = 0.75$ mA.

7. If the gain β of an NPN transistor is 200 and its collector current is 4 mA, the value of base current will be:

Options:

A. 20 μ A

B. 25 μ A

C. 30 μ A

D. 35 μ A

Correct option: A. 20 μ A

Explanation: Using $\beta = I_C / I_B \rightarrow I_B = 4 \text{ mA} / 200 = 0.02$ mA = 20 μ A.

8. The majority charge carriers in the emitter of an NPN transistor are:

Options:

A. pentavalent atoms

B. electrons

C. trivalent atoms

D. holes

Correct option: B. electrons

Explanation: In an NPN transistor, the emitter is N-type semiconductor where electrons are the majority charge carriers.

9. The output of a NAND gate is 0 when:

Options:

A. A is '1' and B is '1'

B. A is '0' and B is '1'

C. both A and B are '0'

D. both A and B are '1'

Correct option: D. both A and B are '1'

Explanation: A NAND gate gives output 0 only when both inputs are 1.

10. If $X = A + B$, then X is 0 when:

Options:

A. both A and B are '0'

B. A or B is '0'

C. A is '0' and B is '1'

D. A is '1' and B is '0'

Correct option: A. both A and B are '0'

Explanation: $X = A + B$ represents an OR operation. The output is 0 only when both inputs are 0.

11. The output of a NOR gate is '1' when:

Options:

A. both of its inputs are '0'

B. both of its inputs are '1'

C. any of its inputs is '0'

D. any of its inputs is '1'

Correct option: A. both of its inputs are '0'

Explanation: A NOR gate produces output 1 only when all inputs are 0.

12. The logical operation performed by the given gate symbol is:

Options:

A. AND

B. NOR

C. NAND

D. OR

Q1

In a junction transistor, emitter current is 5.82 mA and base current is 120 μA . Calculate the collector current.

GIVEN:

- Emitter current (I_e) = 5.82 mA
- Base current (I_b) = 120 μA = 120×10^{-6} A

REQUIRED:

The relationship between emitter, base and collector current is:

$$I_e = I_b + I_c$$

$$I_c = I_e - I_b$$

$$I_c = 5.82 \times 10^{-3} - 120 \times 10^{-6} \text{ A}$$

$$I_c = 5.7 \text{ mA}$$

SOLUTION:

The relationship between emitter, base and collector current is:

$$I_e = I_b + I_c$$

$$- I_c = 5.82 \times 10^{-3} - 120 \times 10^{-6} \text{ A}$$

$$I_c = 5.7 \text{ mA}$$

ANSWER

Therefore,
Collector current will be 5.7 mA

Q2

For a $600 \mu\text{A}$ base current and 30 mA collector current, how much is the current gain (β)?

GIVEN:

- Base current (I_b) = $600 \mu\text{A}$
- Collector current (I_c) = 30 mA

REQUIRED:

Current gain (β) = ?

SOLUTION:

Formula:

$$\beta = \frac{I_c}{I_b}$$

$$\beta = \frac{30 \times 10^{-3} \text{ A}}{600 \times 10^{-6}} = 50$$

$$\beta = 50$$

SOLUTION:

The relationship between emitter, base and collector current is:

$$\beta = 50$$

ANSWER

Therefore,
Current gain (β) will be 50

Infobox:-

β is a unitless quantity because same units cancel each other.

Q3

Calculate the value of β gain if an emitter current is changed by 4 mA and the collector current is changed by 3.5 mA.

GIVEN:

- Emitter current (I_e) = 4 mA
- Collector current (I_c) = 3.5 mA

REQUIRED:

Current gain (β) = ?

SOLUTION:

First find Base current (I_b):

$$I_b = I_e - I_c$$

$$I_b = \frac{4 \text{ mA} - 3.5 \text{ mA}}{0.5 \text{ mA}}$$

Now, calculate β gain:

$$\beta = \frac{I_c}{I_b}$$

$$\beta = \frac{3.5 \text{ mA}}{0.5 \text{ mA}} = 7$$

ANSWER

Therefore,
 β gain will be 7

Example 18.1

When collector current in a junction transistor is 99.9 mA and base current is 0.1 mA, how much is the emitter current?

GIVEN:

- Collector current (I_c) = 99.9 mA
- Base current (I_b) = 0.1 mA

REQUIRED:

Emitter current (I_e) = ?

SOLUTION:

The relationship between emitter, base and collector current is:

$$I_e = I_b + I_c$$

$$I_e = 0.1 \text{ mA} + 99.9 \text{ mA}$$

$$I_e = 100 \text{ mA or } 0.1 \text{ A}$$

ANSWER

Therefore,

Emitter current will be 100 mA or 0.1 A

Example 18.2

Find the value of base current required to turn on the transistor for a collector current of 150 mA, for a transistor having current gain $\beta = 190$?

GIVEN:

- Collector current (I_c) = 150 mA
- Current gain (β) = 190

REQUIRED:

Base current (I_b) = ?

SOLUTION:

The relationship for current gain is:

$$\beta = \frac{I_c}{I_b}$$

$$I_b = \frac{I_c}{\beta} = \frac{150 \text{ mA}}{190}$$

$$I_b = 0.789 \text{ mA}$$

ANSWER

Therefore,
Base current to run transistor will be around 0.8 mA

Credit

Written by:

Muhammad Bilal Mazhar

Compiled by:

Muhammad Mueen

Muhammad Bilal Mazhar

Umasia Nawab

SRQS credit:

muhammad hussain arshi

Amna kareem

hiba naveed

Ayesha fahad

MCQs credit:

muhammad Ammar ajmal

Haram Jawad

Quick revision sheet credit :

Eman tahir

Maida kazmi

Muhammad Ammar ajmal

Ibrahim siddique

Amna kareem

Muhammad Rehan

Exercise short Questions:

Abu Zahra

Side boxes with numericals:

Muhammad Rehan

Inaya toufique

Exercise MCQs credit:

Muhammad Bilal Mazhar

Additional support:

Muhammad Bilal Mazhar

Inaya toufique

Reviewed by:

Muhammad Bilal Mazhar

Inaya toufique

Muhammad Mueen

Umasia Nawab

Mam irza maryam

Supervised by:

Sir MAK

Mam Irza Maryam

Uploaded by:

Sir Abdur Rehman